

# MIPS Assembly language summary

## MIPS operands

Name	Example	Comments
32 registers	\$s0-\$s7, \$t0-\$t9, \$zero, \$a0-\$a3, \$v0-\$v1, \$gp, \$fp, \$sp, \$ra, \$at	Fast locations for data. In MIPS, data must be in registers to perform arithmetic. MIPS register \$zero always equals 0. Register \$at is reserved for the assembler to handle large constants.
2 <sup>30</sup> memory words	Memory[0], Memory[4], ..., Memory[4294967292]	Accessed only by data transfer instructions. MIPS uses byte addresses, so sequential words differ by 4. Memory holds data structures, such as arrays, and spilled registers, such as those saved on procedure calls.

## MIPS assembly language


Category	Instruction	Example	Meaning	Comments
	add	add \$s1, \$s2, \$s3	\$s1 = \$s2 + \$s3	Three operands; data in registers
Arithmetic	subtract	sub \$s1, \$s2, \$s3	\$s1 = \$s2 - \$s3	Three operands; data in registers
	add immediate	addi \$s1, \$s2, 100	\$s1 = \$s2 + 100	Used to add constants
	load word	lw \$s1, 100(\$s2)	\$s1 = Memory[\$s2 + 100]	Word from memory to register
	store word	sw \$s1, 100(\$s2)	Memory[\$s2 + 100] = \$s1	Word from register to memory
Data transfer	load byte	lb \$s1, 100(\$s2)	\$s1 = Memory[\$s2 + 100]	Byte from memory to register
	store byte	sb \$s1, 100(\$s2)	Memory[\$s2 + 100] = \$s1	Byte from register to memory
	load upper immediate	lui \$s1, 100	\$s1 = 100 * 2 <sup>16</sup>	Loads constant in upper 16 bits
	branch on equal	beq \$s1, \$s2, 25	if (\$s1 == \$s2) go to PC + 4 + 100	Equal test; PC-relative branch
	branch on not equal	bne \$s1, \$s2, 25	if (\$s1 != \$s2) go to PC + 4 + 100	Not equal test; PC-relative
Conditional branch	set on less than	slt \$s1, \$s2, \$s3	if (\$s2 < \$s3) \$s1 = 1; else \$s1 = 0	Compare less than; for beq, bne
	set less than immediate	slti \$s1, \$s2, 100	if (\$s2 < 100) \$s1 = 1; else \$s1 = 0	Compare less than constant
	jump	j 2500	go to 10000	Jump to target address
Unconditional jump	jump register	jr \$ra	go to \$ra	For switch, procedure return
	jump and link	j al 2500	\$ra = PC + 4; go to 10000	For procedure call

# MIPS
 
## instructions


R-type

add Rd, Rs, Rt      # Rd=Rs+Rt  
 sub Rd, Rs, Rt      # Rd=Rs-Rt  
 and Rd, Rs, Rt      # Rd=Rs AND Rt  
 or Rd, Rs, Rt        # Rd=Rs OR Rt  
 xor Rd, Rs, Rt      # Rd=Rs XOR Rt  
 slt Rd, Rs, Rt      # if Rs<Rt Rd=1 else Rd=0  
 jr Rs                # PC= Rs (Rd=0)




I-type

 addi Rt, Rs, imm    # Rt=Rs+ imm  
 lw Rt, imm(Rs)      # Rt=M[Rs + imm]  
 sw Rt, imm(Rs)      # M[Rs + imm]=Rt  
 beq Rs, Rt, label    # if Rs==Rt, PC=PC+4+imm\*4  
                           # else        PC=PC+4  
 bne Rs, Rt, label    # same as beq with cond of Rs≠Rt  
 ori Rt, Rs, imm      # Rt=Rs OR imm  
 lui Rt, imm          # Rt= imm<<16



j-type

 j imm                # PC= imm\*4  
 jal imm             # PC= imm\*4, \$31=PC+4



# 1) Description of the Fetch unit

Here we design the Fetch Unit of a pipelined MIPS CPU.

 


Fig. 1 – The Fetch Unit

The Fetch Unit is the part of the CPU that fetches the instruction from the Instruction Memory (IMem) into the Instruction Register (IR\_reg). It also handles jumps and branches. The Fetch Unit's main components are the PC register (PC\_reg) and IMem. The PC\_reg is a 32 bit register that advances by 4 in every clock. Thus we should have also a 32 bit Adder that adds 4 to the current PC\_reg value. In order to jump or branch, we need to input the jump address or branch address to the PC register. Thus, we have a multiplexer at the input of the PC register. This is depicted in Fig.1 above

### a. Names & definition of signals inside the Fetch Unit

You must use these exact signal names in your design.

1. PC\_reg – a 32 bit register. When RESET is '1', the PC\_reg value becomes 0x400000.  
(All other registers and FFs will be cleared by RESET='1').
2. PC\_plus\_4 – a 32 bit signal that has the PC\_reg value + 4.
3. PC\_plus\_4\_pID – a registered version of the PC\_plus\_4 to be used in the ID phase. This is why we added \_pID at the end of that signal name.
4. branch\_adrs – a 32 bit signal which is made of PC\_plus\_4\_pID + sext(imm)<<2. This is the address to be loaded into the PC when a successful branch is performed. Imm signal is made of the lower 16 bits of IR\_reg (see IR\_reg in #8 below).
5. jump\_adrs – a 32 bit signal made of PC\_plus\_4\_pID[31:28] & IR[25:0] & b"00", i.e., the jump address in words multiplied by 4. This is the address to be loaded into the PC when a jump or a jal instruction is performed.
6. jr\_adrs – a 32 bit signal made of the Rs value in a JR instruction. Since we do not have a GPR file, we set the Rs value to x"00400004". In the complete CPU this will be the address to be loaded into the PC when a jr (jump register) instruction is performed.
7. PC\_source – a 2 bit signal. When "00", PC\_reg is loaded with PC\_plus\_4. When "01" it is loaded with branch\_adrs, when "10" with jr\_adrs (Rs value for jr instruction) and when "11", PC\_reg is loaded with the jump\_adrs.  
The PC\_source signal is created by a decoder looking at the opcode field of the instruction residing in the IR\_reg.
8. IR\_reg- a 32 bit register that has the instruction we read from the IMem. This register is part of the IMem (The IMem is an already designed component we use in the Fetch Unit).
9. imm – the 16 LSBs of IR\_reg
10. sext\_imm – sign extension of imm to 32 bits
11. opcode – the 6 MSBs of IR\_reg. We could determine the PC\_source value according to the instruction opcode (j,jal-11, beq,bne-01,jr -10, any other instruction-00).
12. HOLD – This signal is meant to freeze all registers when it is "1". It will be used later for running the design in a single clock mode. At that mode this signal will be "1" all the time except for the clock cycles in which we want to perform a single clock "step". This means that all of the registers should have a HOLD input. The IMem itself and its output register (the IR) already support that signal.

## 1) The Rtype only MIPS CPU and its main components

We would like to design part of the MIPS CPU which is capable of running simple programs with Rtype instructions only. There are 3 main parts involved. These are the Fetch Unit from HW2, the GPR File and the MIPS ALU.

In this homework/lab exercise we will design the GPR File and the MIPS ALU. In the next exercise we will tie the GPR File, the MIPS ALU and the Fetch unit together to form an Rtype MIPS CPU.

Below we see a simplified drawing of the Rtype MIPS CPU.

 


Fig. 1 – The Rtype only MIPS CPU – a simplified drawing

## 2) GPR – design & simulation

The inside of the GPR File is made of a dual port memory. That memory does not have a register at its output as we had in the IMem we used in the Fetch Unit of HW2. Only the writing process of the memory is triggered by the rising edge of the clock. When “wr\_en”=’1’ and there is a rising edge in “wr\_clk”, then the “wr\_data” is written into the “wr\_address” location of the memory. The reading from the dual port memory is a combinational process.

Note that “wr\_address” and “rd\_address” are integers, and if your address signals is a STD\_LOGIC\_VECTOR signal you need to use the function conv\_integer( your signal vector name) to convert the STD\_LOGIC\_VECTOR value to integer in order to set a value to the wr\_address or rd\_address.

We give you a vhd file called **single\_port\_memory.vhd** and you need to manipulate it to become a **dual\_port\_memory.vhd**. The skeleton of the **dual\_port\_memory.vhd** is given in the **dual\_port\_memory.empty** file so that you will use the signal names we decided on.

The outside to the GPR File is described in the skeleton file **GPR.empty**. In this file we implement the following:

2.1) Although the dual port memory we use has address 0 and so we can write data into that address and read data from that address, we will make sure that when we read from read\_reg1=0, we will get rd\_data1=x”00000000”.

2.2) Similarly, when reading from read\_reg2=0, we will get rd\_data2=x”00000000”.

2.3) We will add a GPR\_hold input to the GPR file. When this input is ‘1’ there should not be a write operation at the rising edge of the clock even if the RegWrite signal is ‘1’.

So you need to prepare the files:


- **dual\_port\_memory.vhd** – that describes the dual port memory in which only the writing is synchronous (activated by the rising edge of the clock)
- **GPR.vhd** – that “wraps” the dual\_port\_memory component of 32 addresses of 32 bits each and performs what was requested in 2.1 and 2.2 above

To ease the design for you the GPR.vhd content is depicted in Fig. 2 below.

Now you can run a simulation and check your design with the additional three files of:

- **SIM\_GPR\_TB.vhd** - the TestBench file we prepared for you ahead of time
- **SIM\_GPR\_TB\_data.dat** - the TestBench testing data file we prepared ahead of time
- **SIM\_HW3\_GPR\_filenames.vhd** – In this file we specify the path of the data files used in simulation

With these 5 files you need to run the simulation and verify your design works fine. Note that you need to update the **SIM\_HW3\_GPR\_filenames.vhd** with the actual path of the **SIM\_GPR\_TB\_data.dat** file.

 

**Fig. 2 – The inside of the GPR.vhd**

You should submit a zip file of the entire GPR\_File simulation project – see detailed instructions at section 4 of this document.

Also you need to attach a doc file with screen captures describing the simulation you made. All i/o signals of GPR entity should be presented in the screen capture. Show the 2<sup>nd</sup> session of writing into the GPR File (clock cycles 46 to 55 = 920ns to 1100ns) and make sure that the values of all signals are readable. Explain what is seen in the **rd\_data1** and **rd\_data2** outputs of the GPR\_File in these clock cycles.

### 3) MIPS ALU – design & simulation

The MIPS ALU is a combinational circuit. No FFs are involved. We “added” to the ALU also the ALU\_src\_B multiplexer and also the logic control that issues the ALU\_cmd signal. The ALU\_cmd is a 3 bit signal vector which determines what is the calculation done by the ALU.

If the ALU\_cmd is “010”, the ALU performs an addition. If ALU\_cmd is “110”, the ALU performs a subtraction. Here is the list of operation done by the ALU according to the ALU\_cmd bits:

- ALU\_cmd=“000” => A and B
- ALU\_cmd=“001” => A or B
- ALU\_cmd=“010” => A + B
- ALU\_cmd=“011” => A xor B
- ALU\_cmd=“100” => A nand B - not used
- ALU\_cmd=“101” => A nor B - not used
- ALU\_cmd=“110” => A - B
- ALU\_cmd=“111” => SLT. 1 if A<B, 0 if not. A & B are considered 2’s complement numbers

The logic that drives the ALU\_cmd gets the 2 bit signal vector called ALUOP. When ALUOP=“00”, the ALU performs addition. When ALUOP=“01”, the ALU performs subtraction. When ALUOP=“10”, the ALU operation is determined by the 6 bit vector called Funct (function) that comes from the 6 LSBs of the IR reg. Here is the list of the Funct codes:

- Funct=“100000” => ADD
- Funct=“100010” => SUB
- Funct=“100100” => AND
- Funct=“100101” => OR
- Funct=“100110” => XOR
- Funct=“101010” => SLT

In all other cases we request to perform ADD.

The ALU\_src\_B mux selects what will be fed into the B input of the ALU. If ALUsrcB=’0’, we input the B\_in data into the ALU B input. If ALUsrcB=’1’, we input the sext\_imm data into the ALU B input.

We prepared a **MIPS\_ALU.empty** file for your convenience.

You need to add all of the logic described above. When done, you should run a simulation using the **MIPS\_ALU.vhd** file and the additional three files of:

- **SIM\_MIPS\_ALU\_TB.vhd** - the TestBench file we prepared for you ahead of time
- **SIM\_MIPS\_ALU\_TB\_data.dat** - the TestBench Data file we prepared ahead of time
- **SIM\_HW3\_ALU\_filenames.vhd** – In this file we specify the path of the data files used in simulation

With these 4 files you need to run the simulation and verify your design works fine. Note that you need to update the **SIM\_HW3\_ALU\_filenames.vhd** with the actual path of the **SIM\_MIPS\_ALU\_TB\_data.dat** file.

You should submit a zip file of the entire MIPS\_ALU simulation project– see detailed instructions at section 4 of this document. Also you need to attach a doc file with screen captures describing



the entire simulation you made – till 1200 ns. All i/o signals of the MIPS\_ALU entity should be presented in the screen capture.

#### 4) **HW3 report**

You should submit a single zip file for the Simulation of both entities. It should have three directories/folders. The first is called **GPR\_File**, the 2<sup>nd</sup> is called **MIPS\_ALU**, the 3<sup>rd</sup> is called **Disassembly**.

In the **GPR\_File** directory you will have the following 3 sub-directories:

- **GPR\_File\_Src** - with all of your simulation sources
- **GPR\_File\_Sim** - with the simulation project
- **GPR\_File\_Docs** - Add a doc file with screen capture of the simulation showing the waveforms of the TB signal and the Console window. All i/o signals of GPR entity should be presented in the screen capture. Show the 2<sup>nd</sup> session of writing into the GPR File (clock cycles 46 to 55 = 920ns to 1100ns) and make sure that the values of all signals are readable. Explain in detail what do we see in rd\_data1 and rd\_data2 in these 10 clock cycles. The first few lines in the report will have your ID numbers (names are optional).

In the **MIPS\_ALU** directory you will have the following 3 sub-directories:

- **MIPS\_ALU\_Src** - with all of your simulation sources
- **MIPS\_ALU\_Sim** - with the simulation project
- **MIPS\_ALU\_Docs** - Add a doc file with screen capture of the simulation showing the waveforms of the TB signal and the Console window. The screen captures should have the entire simulation you made (from its start to its end – till 1200 ns), and all of the MIPS\_ALU i/o signals. No need to see the values of the signals, just the total picture and the console with a “Test Pass” message. The first few lines in the report will have your ID numbers (names are optional).

In the **Disassembly** directory you should have a doc file in which you disassemble a MIPS binary code and some explanations (answer questions).

See the questions in the file 18.1\_MIPS\_binary\_code\_for\_disassembly\_v4.docx

Note that the binary MIPS code you need to disassemble is the program we will be using in HW4. You need this disassembled code to understand what is done in HW3. That binary program to be disassembled appears in a Word file called 18.1\_MIPS\_binary\_code\_for\_disassembly\_v4.docx and also in a text file called 18.2\_MIPS\_binary\_code\_for\_disassembly\_v4.txt.

Use this file and add your disassembled code. See the appendix at the end of the document for MIPS instructions coding. Also explain in detail what is done by this code. Also explain how this code tests the GPR\_file and ALU parts of a MIPS CPU.

At the end of this assignment you will have the necessary building blocks for our next assignment, HW4 – the “Rtype” MIPS CPU.

**Enjoy the assignment !!**

## 5) Appendix A – MIPS instructions coding

### a. Codes of the Opcode fields - IR(31 downto 26)

sw	= [101011] = 43
lw	= [100011] = 35
lui	= [001111] = 15
ori	= [001101] = 13
addi	= [001000] = 8
beq	= [000100] = 4
bne	= [000101] = 5
j	= [000010] = 2
jal	= [000011] = 3
R-type	= [000000] = 0

### b. Function field codes for RType instructions – IR(5 downto 0)

add	= [100000] = 32
sub	= [100010] = 34
and	= [100100] = 36
or	= [100101] = 37
xor	= [100110] = 38
slt	= [101010] = 42
jr	= [001000] = 8

**Rs, Rt and Rd fields have a 5 bit binary number of the register (0-31)**

## 1) The Rtype MIPS CPU and its main components

In HW3 we stated that we want to design part of the MIPS CPU which is capable of running simple programs with Rtype instructions only. There are 3 main parts involved. These are the Fetch Unit from HW2, the GPR File and the MIPS ALU. We built the last two components in HW3.

In this homework/lab exercise we are going to tie the GPR File, the MIPS ALU and the Fetch unit together to form an Rtype MIPS CPU.

Below we see a simplified drawing of the Rtype MIPS CPU we used in HW3.

 


Fig. 1 – The Rtype only MIPS CPU – a simplified drawing

In HW3 we called this CPU the Rtype only MIPS. However, in the Fetch Unit we already have the ability to support jump and branch instructions. Supporting **beq** and **bne** instructions might require some minor additions. In order to make things more interesting, we will also support the **addi** instruction. Thus, this “Rtype” MIPS CPU will start running from address 400000h and preform **Rtype** instructions and also **j**, **beq**, **bne** and **addi** instructions.

Some changes in the Fetch Unit are necessary to “tailor” it into the Rtype MIPS CPU. Our design of the Rtype MIPS CPU resides in the **HW4\_top.vhd**.

A more accurate description appears in Figure 2 below.

 


Fig. 2 – The Rtype MIPS or HW4\_MIPS CPU

## 2) HW4 Rtype MIPS CPU – design & simulation

The HW4 Rtype MIPS CPU will have four phases.

- **IF** – Instruction Fetch, which is carried out inside the Fetch Unit producing the instruction in the IR\_reg at the rising edge of the clock which ends the IF phase and starts the ID phase.
- **ID** – Instruction Decode, which is the stage in which we do the following:
  - Decode the instruction residing now at the IR\_reg and decide what should be done.  
This means, we produce all control signals to be used by that instruction in all phases of this instruction – ID, ED and WB.
  - Read Rs into A\_reg and Rt into B\_reg

The rising edge of the clock sampling data into the A\_reg and B\_reg ends the ID phase and starts the EX phase.

- **EX** – Execute, which is the phase in which the ALU calculates the result of A op B (in **Rtype** instructions) or A+sext\_imm (in **addi** instructions). The result is sampled into the ALUout\_reg at the rising edge of the clock which ends the EX phase and starts the WB phase.  
In this phase we also select Rs or Rd as the GPR file destination register to be written into in the Write Back phase.
- **WB** – Write Back, which is the final phase of the instruction. If this is an **Rtype** or **addi** instruction, then we write the ALUout\_reg value into the GPR file. If this is a **j**, **beq** or **bne** instruction, we do nothing at that stage. The rising edge of the clock sampling data into the GPR File ends the WB phase and completes the instruction.

As explained above, the control signals are created by decoding the instruction residing in the IR\_reg at the ID phase. If the control signal is supposed to influence at the EX phase, it must be delayed by 1 clock cycle. If that control signal is supposed to influence at the WB phase, it must be delayed by 2 clock cycles. You will have to handle these timing issues in order to make your design function properly.

 


Fig. 2b – The Rtype MIPS control scheme

### a. Modifications required in the Fetch Unit

We do the following changes in the Fetch\_Unit entity so it will be possible to use it in the HW4\_TOPdesign. See Figure 3 on the next page.

We remove all rdbk0-15 output signals from the Fetch Unit. We hope we won't need them since the Fetch Unit is already debugged and the changes we introduce are minor.

Instead we add output signals coming out of the Fetch\_Unit that should be used by the rest of the CPU. These output signals are:

1. IR\_reg\_pID - This is a 32 bit signal of the IR\_reg (the instruction bits). We added pID to that signal name to indicate it is the IR\_reg value at the ID phase.
2. sext\_imm\_pID - Similarly, this is the 32 bit sext\_imm signal we calculate at the ID phase. It is outputted from the Fetch Unit to be used later in the EX phase.
3. PC\_reg\_pIF - this is the 32 bit PC\_reg we use during the IF phase for the Instruction Fetch, i.e., for reading from the IMem. It is outputted from the Fetch Unit to be used for verification purposes only (debugging).


These signals are used in the **HW4\_top** entity. They also allow us testing the IR\_reg and sext\_imm (and the PC\_reg) during simulation. Our Fetch\_Unit stays the same for simulation & implementation – no changes are required when going from the simulation phase to the implementation phase. Note that for TB purposes we output the CK\_out\_to\_TB, RESET\_out\_to\_TB, HOLD\_out\_to\_TB signals from the **HW4\_top\_4sim.vhd** which in HW4 is our top component. Therefore, when going from simulation to implementation, we will need to change the **HW4\_top** and remove these signals.

Now we add an input signal to the updated Fetch\_Unit.

1. We add the Rs\_equals\_Rt\_pID signal that tells us whether to branch in beq (if it is '1') or not (if it is '0'). This signal should come from comparing the two data outputs of the GPR File which resides outside the Fetch\_Unit. You should modify the PC\_source signal decoder so that the **beq** and **bne** instructions are properly performed. Make sure that the **addi** instruction is also supported.

The rest of the Fetch\_Unit signals are left unchanged. See Fig. 3 below for the updated Fetch\_Unit with the new signals in **RED**

When simulating our top file is **HW4\_top\_4sim.vhd**. In this entity we will use the **BYOC\_Host\_Intf\_4sim.vhd** as our Host Interface circuit having the pre-loaded IMem. For implementation our top vhd file will be renamed to **HW4\_top.vhd** and inside it, we will use the **BYOC\_Host\_Intf.ngc** file. The difference between the two Host\_Intf versions is that in the sim version the Host Interface has the program already loaded inside (actually it is loaded at the beginning of the simulation). The implementation version includes the real Host\_Intf mechanism allowing us to load a program from the PC, run the design in single clock mode and see the readback signals. The difference between the **HW4\_top\_4sim.vhd** and the **HW4\_top.vhd** will be minor - removal of TB signals.

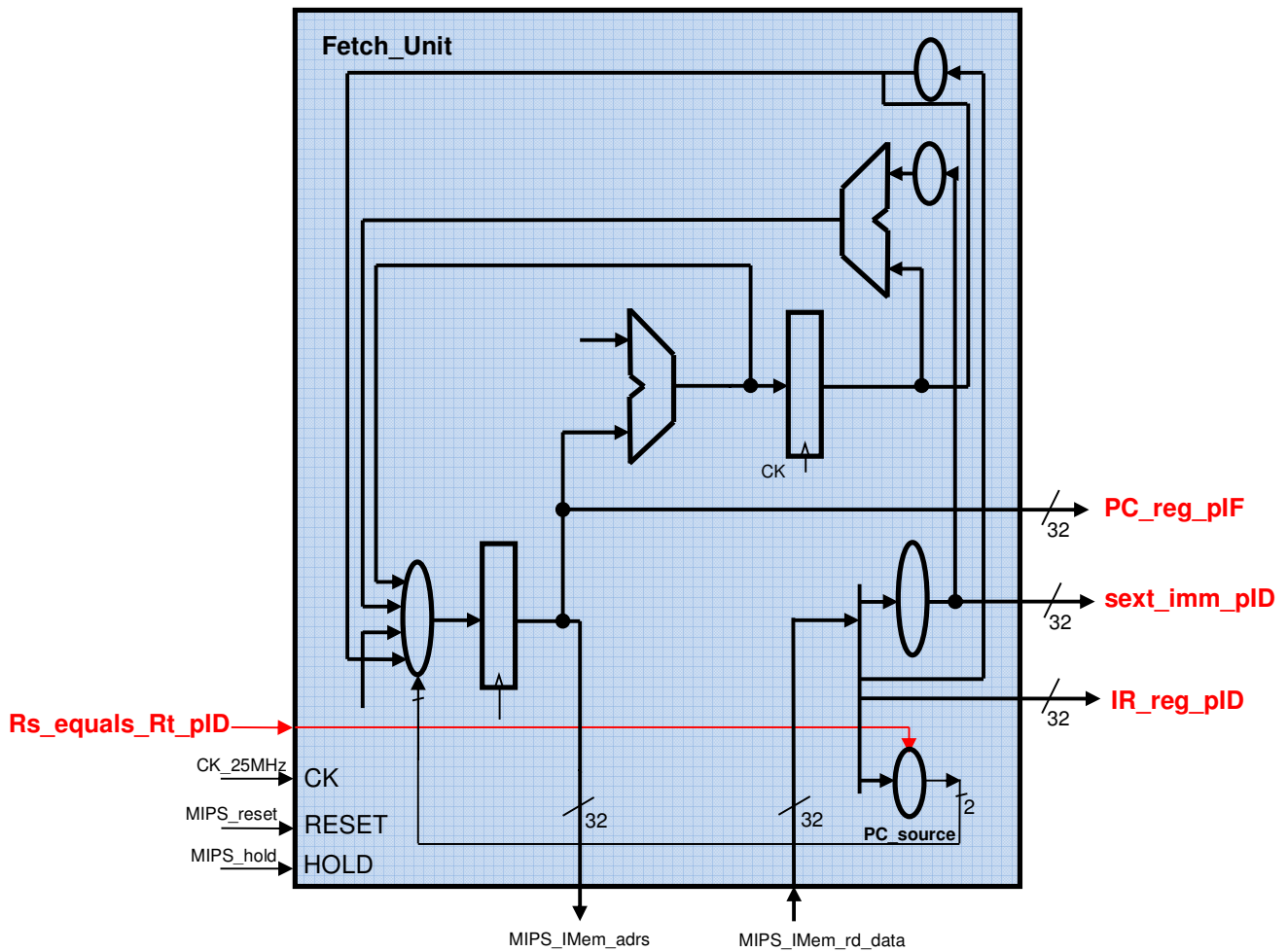

**Fig. 3 – The updated Fetch\_Unit (new signals – in red)**

Note that in the **HW4\_top\_4sim.empty** file we already connected all of the components (Fetch\_Unit, GPR, MIPA\_ALU, BYOC\_Host\_Intf – those are the blue, orange, green and pink parts of Fig. 2). We also defined all of the HW4\_top signals (see in section **b** below). Your job is therefore to rename it to **HW4\_top\_4sim.vhd** and build the missing “logic” in the **HW4\_top\_4sim.vhd** (which is the yellow part in Fig. 2). That “logic” is made of the registers, FFs and combinational logic forming the Rtype MIPS CPU.

# 1. The HW5 MIPS CPU and its main components

In this assignment we add lw and sw instructions to the Rtype MIPS CPU we designed in HW4. This means we have to add the Data Memory (DMem) to our design. Following this we will have an almost complete MIPS CPU capable of performing Rtype, addi, j, beq, bne, lw and sw instructions. In our next & final assignment we will complete the CPU by adding jal, jr, lui and ori instructions and add forwarding to enhance the CPU performance.

The DMem we add is located inside the BYOC\_Host\_Intf component that includes infrastructure allowing loading data into the IMem and DMem memories.

Below we see a simplified drawing of the HW5 MIPS CPU we are going to build in this assignment.

 


Fig. 1 – The HW5 MIPS CPU



A more accurate drawing includes the BYOC\_Host\_Intf part – as depicted in Fig.2 below:

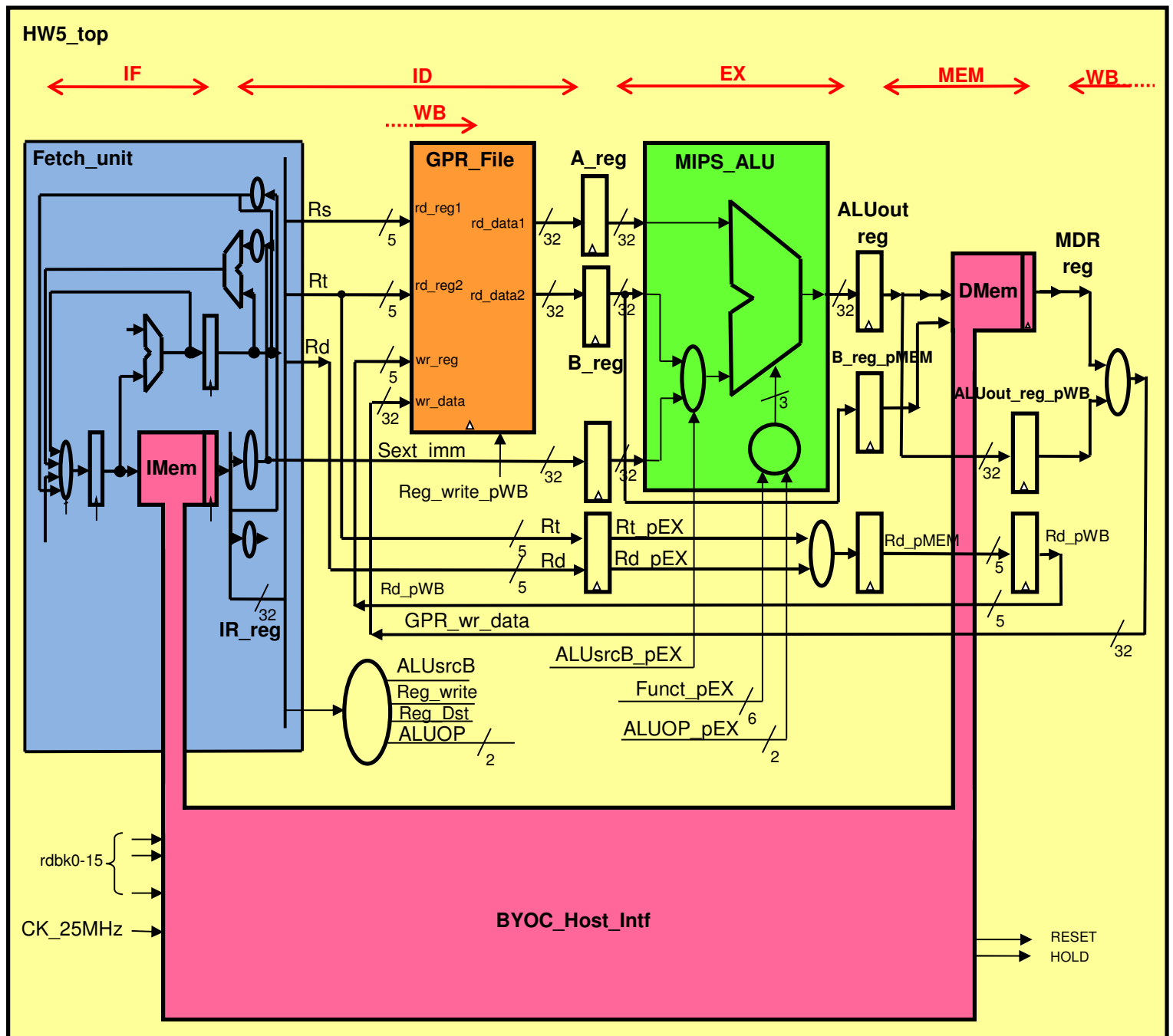


Fig. 2 – The HW5\_MIPS CPU with the Host\_Intf infrastructure

To your **HW5\_top** design, the only required connections to the **BYOC\_Host\_Intf** are the **RESET** & **HOLD** signals, the **IMem** connections and the **DMem** connections and the **rsdbk0-15** coming from the signals we want to check during implementation. These and the rest of the **BYOC\_Host\_Intf** connections are already given in the **HW5\_top\_4sim.empty** file.

You should rename that file to **HW5\_top\_4sim.vhd** and add the necessary equations – all based on HW4 design). Below we describe the actual work required.

### a. Connecting the DMem

The DMem signals are already connected in the **HW5\_top\_4sim.empty** file. There is no need to add any more DMem connections, but you need to understand these connections:

1. MIPS\_DMem\_adrs – a 32 bit address signal of DMem is connected to ALUout\_reg signal.
2. MIPS\_DMem\_rd\_data – the 32 bit data read from the DMem (we read from the address specified by MIPS\_DMem\_adrs). This is after a register. I.e., it is actually the MDR data. It is directly connected to the HW5\_top signal called MDR\_reg.
3. MIPS\_DMem\_wr\_data – 32 bit data to be written into the DMem to the address specified by MIPS\_DMem\_adrs at the rising edge of the CK if MIPS\_DMem\_we is '1'. It is connected to (i.e., driven by) the B\_reg\_pMEM signal of HW5\_top.
4. MIPS\_DMem\_we – a '1' means data will be written into the DMem at the rising edge of the CK. This is driven by the MemWrite\_pMEM signal of HW5\_top.

### b. Names & definition of signals inside the HW5\_top MIPS CPU

In your design, you should use the exact signal names as were used in the Rtype MIPS CPU of HW4 and **add** the following signals using the exact signal names shown below:

#### ID additional signals

5. MemWrite – '1' when this is a sw instruction and we write into the DMem, '0' otherwise.
6. MemToReg – '1' when we read from memory, i.e., in lw instruction.

#### EX phase signals


7. MemWrite\_pEX – MemWrite delayed by 1 clock cycle.
8. MemToReg\_pEX – MemToReg delayed by 1 clock cycle.

#### MEM phase signals.


9. B\_reg\_pMEM – a 32 bit register receiving the B\_reg signal (i.e., B\_reg delayed by 1 CK cycle). This register has the data to be written into the DMem in sw instruction.
10. Rd\_pMEM – the output of RegDest mux selecting to which register the CPU writes in the WB phase.
11. MemWrite\_pMEM - MemWrite\_pEX delayed by 1 clock cycle.
12. MemToReg\_pMEM – MemToReg\_pEX delayed by 1 clock cycle.
13. RegWrite\_pMEM – RegWrite\_pEX delayed by 1 clock cycle.

#### WB phase signals

14. MDR\_reg - a 32 bit register that has the data read from the memory. This is a rename of the DMem\_rd\_data signal coming out of the **BYOC\_Host\_Intf\_4sim** component.
15. ALUout\_reg\_pWB - a 32 bit register that has the ALUout\_reg data delayed by 1 CK cycle.
16. GPR\_wr\_data - a 32 bit signal that is the output of the MemToReg mux (selecting between MDR\_reg and ALUout\_reg\_pWB).
17. Rd\_pWB – Rd\_pMEM delayed by 1 clock cycle.
18. MemToReg\_pWB – MemToReg\_pMEM delayed by 1 clock cycle
19. RegWrite\_pWB – RegWrite\_pMEM delayed by 1 clock cycle.

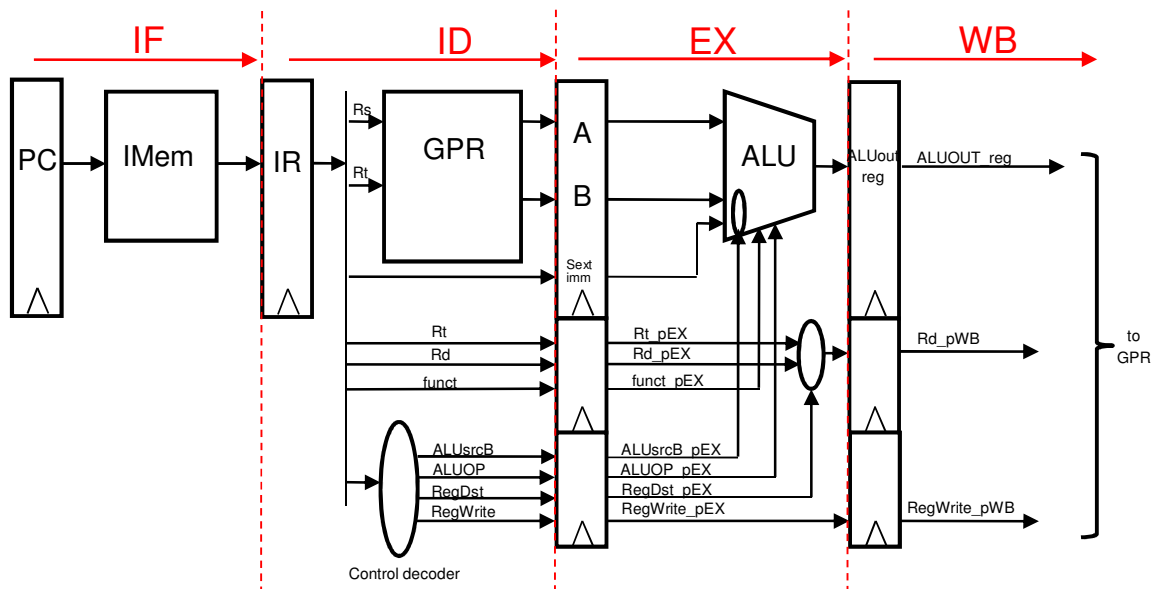

**Fig. 1 – HW4 control scheme**

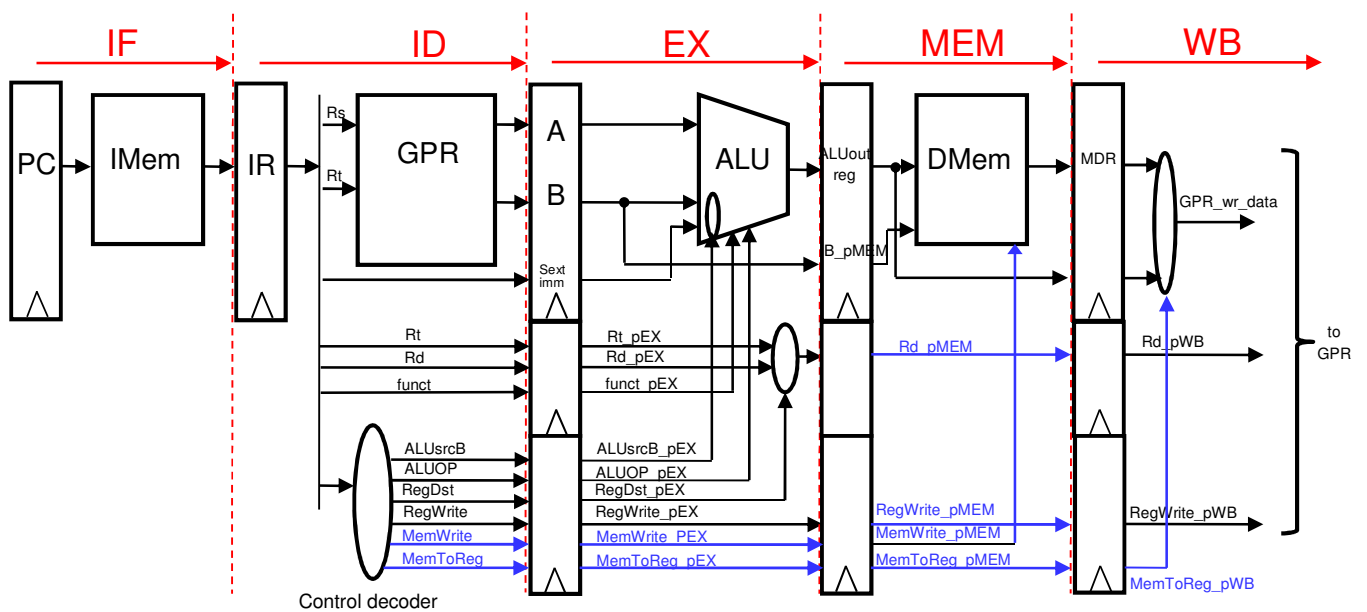

**Fig. 2 – HW5 control scheme**  
(Additions to HW4 control signals - in blue)

# 1. The HW6 MIPS CPU

In this assignment we add jal, jr, lui, ori instructions to the MIPS CPU we designed in HW5. Thus, we will have a CPU supporting Rtype (add, sub, and, or, xor, slt), addi, lui, ori, beq, bne, lw, sw, j, jal and jr instructions. Besides adding these instructions we would like to add a forwarding mechanism to enhance the CPU performance.

It is highly recommended to watch the lecture in: <http://youtu.be/Yu6FFVhI4D4> and the first 11 minutes of: [http://youtu.be/-fylybz8p\\_M](http://youtu.be/-fylybz8p_M)

Below we remind you of the HW5 MIPS CPU we designed in HW5. It is almost the same as the HW6 MIPS of this assignment

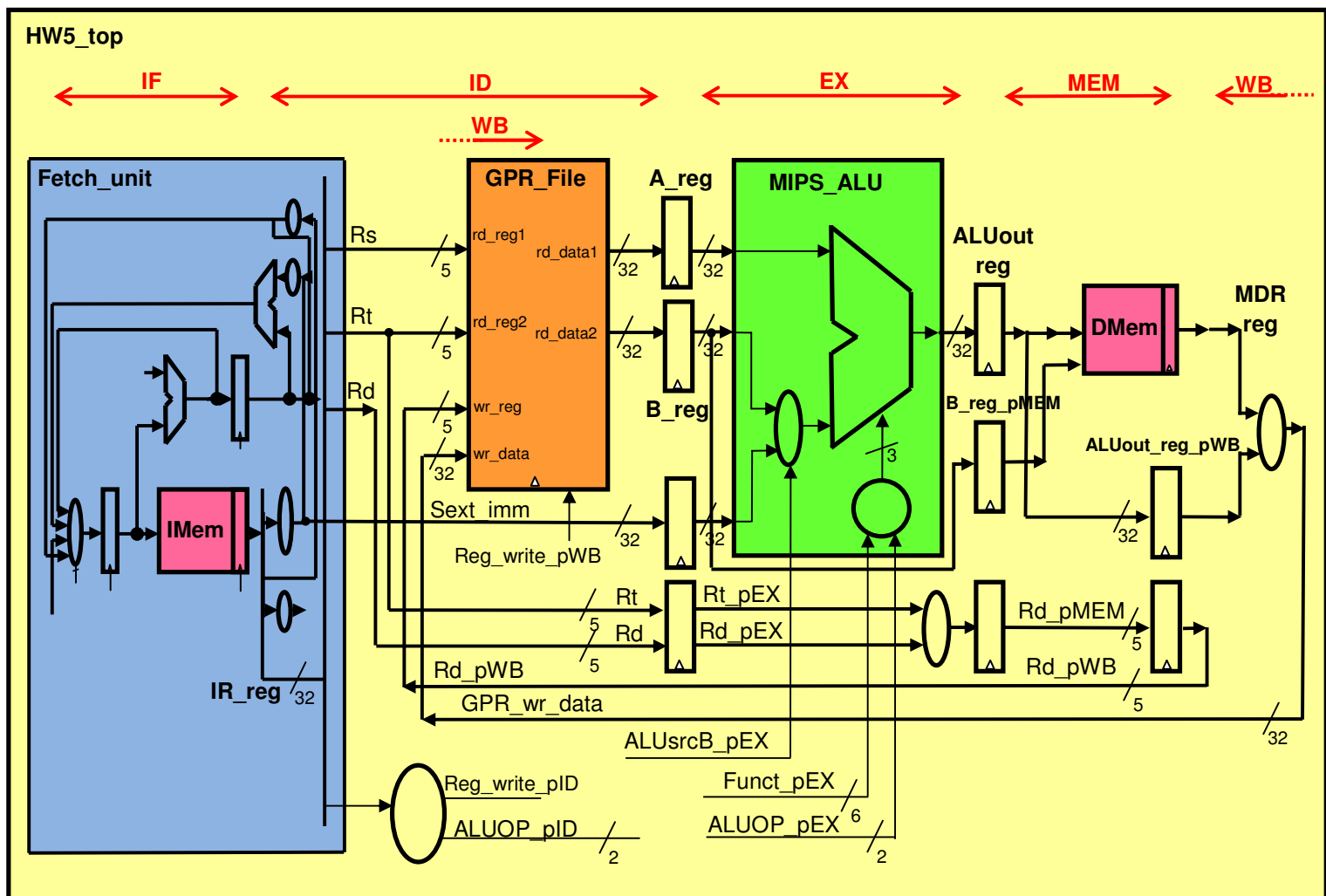


Fig. 1 – The HW5 MIPS CPU

## a. HW6 outline

This assignment has 3 parts. The first is to add the new instructions and it is described in section **b** below. It is recommended to fill up the table in **Appendix A** before starting to add the new instructions. We will not implement that design, just run the simulation. After a successful simulation of this part you should add the forwarding mechanism. This is done in two parts, data forwarding (which is described in section **c**) and branch forwarding (described in section **d**). Thus this HW has 3 parts: i) Add the new instructions ii) Add data forwarding iii) Add branch forwarding.

## b. PART I - Adding the new instructions

- i. LUI – The simplest way to add the lui instruction is to change the sign extension circuit so that when we have a lui instruction, it shifts the imm left for 16 times. We should make sure that the rest of the circuit will behave in a similar manner to addi instruction. For example, the ALU will add it's a input value to the sext\_imm\_reg value that appears in its B input. Thus, we should make sure that the A\_reg value is 0. This can be done in several ways. The simplest way is to make sure that the Assembler always translate lui instruction so that Rs=0. Another way is to force Rs to be 0 (b"00000") when we decode a lui instruction.
- ii. ORI – This instruction is almost the same as addi one. There are two differences. The first is that in ori instruction we should prevent sign extension of the imm. This is easily done by an additional change in the sign extension circuit. The other difference is forcing the ALU to perform a OR operation instead of an ADD one. The simplest way to do that is to use the 4<sup>th</sup> combination of the ALUOP vector signal. While b"00" means ADD, b"01" means SUB and b"10" means use the FUNCTION field to determine the ALU operation, we will add the combination b"11" and will change the MIPS\_ALU so that ALUOP="b11" will result with an OR operation.  
Thus for supporting ORI, we should fix the sext\_imm circuit, force ALUOP control signal to be b"11" and change the MIPS\_ALU to support this combination.  
[The expected behavior of the ALUOP signal is: "10" in Rtype instructions, "01" in beq & bne, "11" in ori, "00" in all other instructions]
- iii. JR – Supporting this instruction is pretty easy. We should direct the Rs content value (GPR\_rd\_data1) back into the Fetch\_Unit so that the jr\_adrs signal inside the Fetch Unit will get the GPR\_rd\_data1 instead of the constant x"00400004" we had so far.  
This means we need to add a input signal to the Fetch\_Unit entity. This new 32 bit input signal is called jr\_adrs\_in.
- iv. JAL – Supporting this instruction is a little more involved. The jal should behave exactly as the j instruction in the Fetch Unit so that when a j instruction or jal instruction appear in the IR\_reg, the PC\_source will be "11" and the PC\_reg will get the "jump\_adrs" signal at its input. This makes sure that we jump properly in both cases. In jal we should also write the PC\_plus\_4 of the instruction to \$ra, i.e., to register \$31 in the GPR File. How do we do that? We "propagate" the PC\_plus\_4 value till the WB phase and there, add it as an additional input to the MemToReg mux. We need to output the PC\_plus\_4\_pID from the Fetch\_Unit (this means a change in the i/o pins of the Fetch\_Unit). This signal needs to "propagate" till it becomes be PC\_plus\_4\_reg\_pWB. We need to make sure we issue RegWrite='1' in jal and we should force "Rd" to be 31. Since the rule for RegDst mux is


that RegDst='1' only in Rtype instructions, it means that in jal instruction it is '0' and the RegDst mux choose Rd\_pMEM to be Rt\_pEX, it means that in jal instruction we should force Rt to be 31 (b"11111").

To summarize, we need support jal in the Fetch Unit the same as we do for j instruction, we need to output PC\_plus\_4\_pID from the Fetch\_Unit and delay it till the WB phase, we need to issue a RegWrite='1', we need to expand the MemToReg mux to write the PC\_plus\_4 in the WB phase of jal instruction and we need to force Rt to be 31 in jal instruction.

See more in section e below.

### c. PART II - Data forwarding

In a pipelined implementation of a CPU we encounter an inherent latency problem. The result of an add instruction (we will use add instruction as an example, but the analysis is applicable also for all instructions writing back into the GPR File except lw and jal, i.e., Rtype, addi, lui and ori instructions) is available for a later instruction that uses it only after the WB phase of the add instruction is completed. The instruction using that result "reads" it from the GPR File in its' ID phase. Thus, we need to wait 3 time slots before "using" the add result in a new instruction. This is depicted in Fig. 2 below. The updated value of **\$3** is written into the GPR File in the rising edge of the clock ending the WB phase of the "add **\$3**, \$5, \$8" instruction (marked by the red line). Thus, the ID phase of the "add \$y, **\$3**, \$x" instruction which uses that value, can occur to the right of the red line. We see that the inherent 5 CKs latency of the pipelined implementation results with "wasted" time slots.

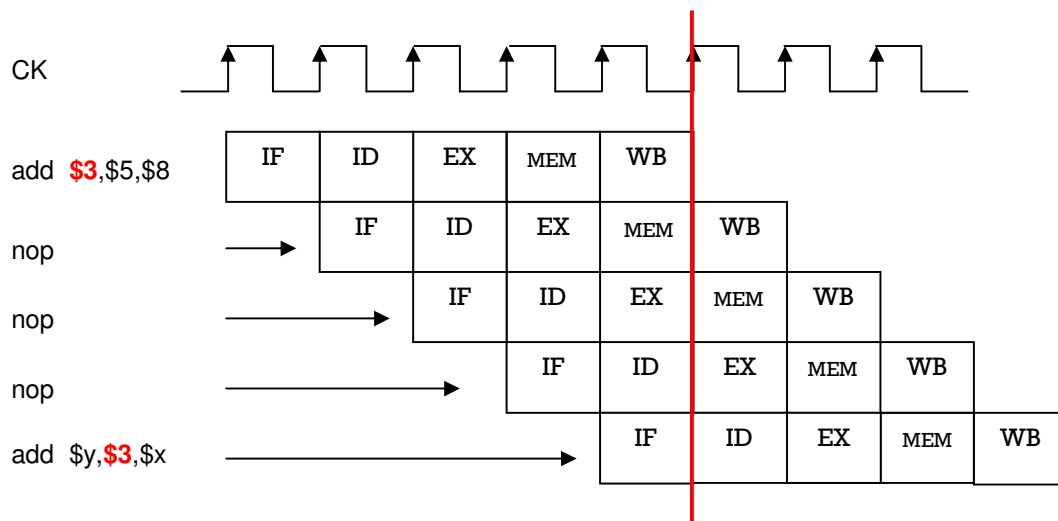

**Fig. 2 – The pipelined MIPS latency**

We can use these time slots for other instructions that do not write to \$3 or \$x (those who are used by the "add \$y, **\$3**, \$x" instruction). A smart C compiler can therefore improve the situation. However, it is easy to overcome this problem and improve the situation dramatically by "Data Forwarding".

Data Forwarding means using the updated value to be written into the GPR File even before it is written into the GPR File. This is possible since that data already exists inside the pipeline – in most cases. We read data from the GPR File in the ID phase of an instruction in order to use it in the EX phase of the instruction. This means that the forwarding should occur in the EX phase or before it, in the ID phase of the instruction we want to forward the data to.

We have 3 cases of Data Forwarding.

1. Case I: Forward data from previous instruction in the EX phase of the current instruction if the Rs or Rt of the current instruction is written into by the previous instruction.

I.e., if `RegWrite_pMEM='1'` and `Rd_pMEM=Rs_pEX`, we should use `ALUout_reg` value instead of `A_reg` value.

Similarly, if `RegWrite_pMEM='1'` and `Rd_pMEM=Rt_pEX`, we should use `ALUout_reg` value instead of `B_reg` value.

This is described by the arrow from the MEM phase of the 1<sup>st</sup> instruction (the top one) in Fig. 3, to the EX phase of the 2<sup>nd</sup> instruction.

2. Case II: Forward data from the instruction that was done 2 clocks ago in the EX phase of the current instruction if the Rs or Rt of the current instruction is written into by the instruction from 2 clocks ago.

I.e., if `RegWrite_pWB='1'` and `Rd_pWB=Rs_pEX`, we should use `MemToReg` mux output value instead of `A_reg` value.


Similarly, if `RegWrite_pWB='1'` and `Rd_pWB=Rt_pEX`, we should use `MemToReg` mux output value instead of `B_reg` value.

This is described by the arrow from the WB phase of the 1<sup>st</sup> instruction in Fig. 3, to the EX phase of the 3<sup>rd</sup> instruction.


3. Case III: Forward data from the instruction that was done 3 clocks ago. This is done in the ID phase of the current instruction (through a “transparent GPR”) if the Rs or Rt of the current instruction is written into by the instruction from 3 clocks ago.

This means that inside the GPR, if `rd_reg1=wr_reg` and `Reg_Write='1'`, then we should bypass the GPR file and output the `wr_data` instead of the “regular” `rd_data1`. Similarly to `rd_reg2` and `rd_data2`.

This is described by the arrow from the MEM phase of the 1<sup>st</sup> instruction in Fig. 3, to the ID phase of the 4<sup>th</sup> instruction.

 

**Fig. 3 – Data Forwarding timing diagram  
(from the 1<sup>st</sup> instruction to future instructions)**

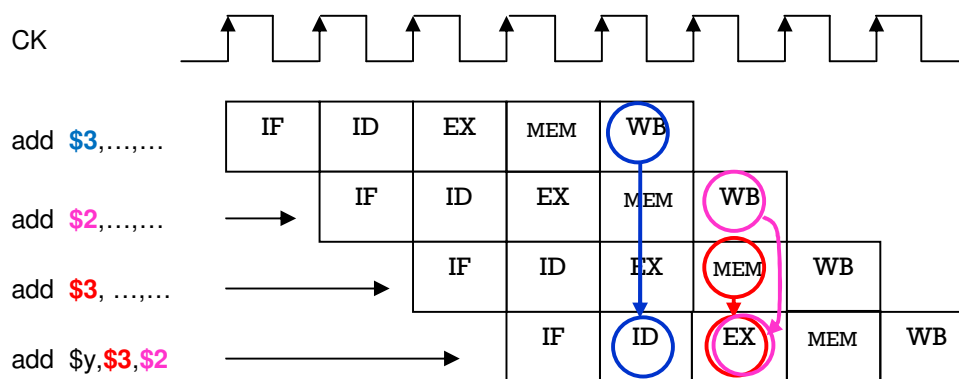

**Fig. 3B – The 3 Data Forwarding options to an instruction  
(to the 4<sup>th</sup> instruction from previous instructions)**

Fig. 3B shows we see that the 1<sup>st</sup> instruction writes to register \$3, the 2<sup>nd</sup> instruction writes to register \$2 and the 3<sup>rd</sup> instruction writes to register \$3. We see the 3 forwarding mechanisms working to supply updated data to the 4<sup>th</sup> instruction. In the ID phase of the 4<sup>th</sup> instruction we read the result of the 1<sup>st</sup> instruction via the “transparent GPR” mechanism supporting forwarding from 3 instructions ago. In the EX phase of the 4<sup>th</sup> instructions we see forwarding of Rs from the previous instruction (in red) and from 2 instructions ago (in magenta).

In Fig. 4 and Fig. 5 below we see the MIPS data path without and with Data Forwarding. The changes are drawn in red. The connections shown in the MIPS data path in Fig. 5 support forwarding from previous instruction (case I) and from instruction before the previous one (case II). The forwarding through “transparent” GPR File (case III) is not shown in Fig. 5. It is described in Fig. 6 further below with the changes inside the GPR File also drawn in red.



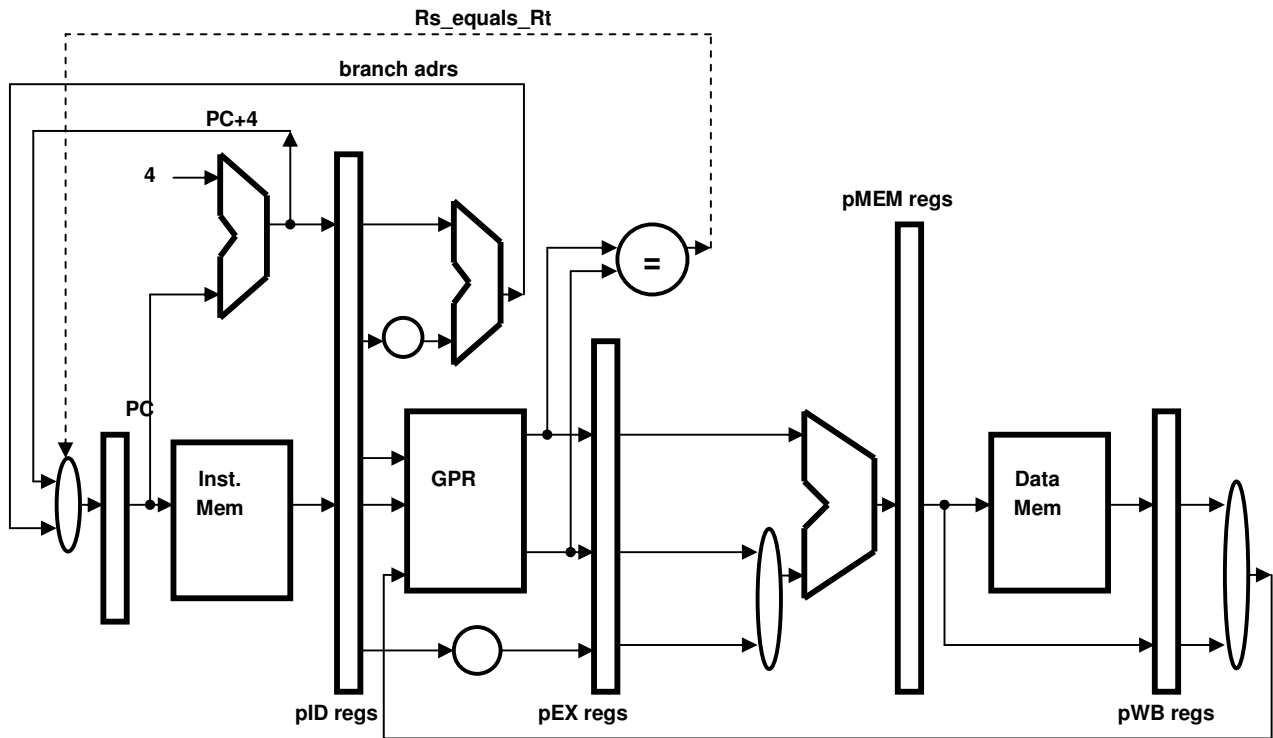


Fig. 4 – MIPS data path (part) with no forwarding

 


Fig. 5 – MIPS Data Path with Data Forwarding

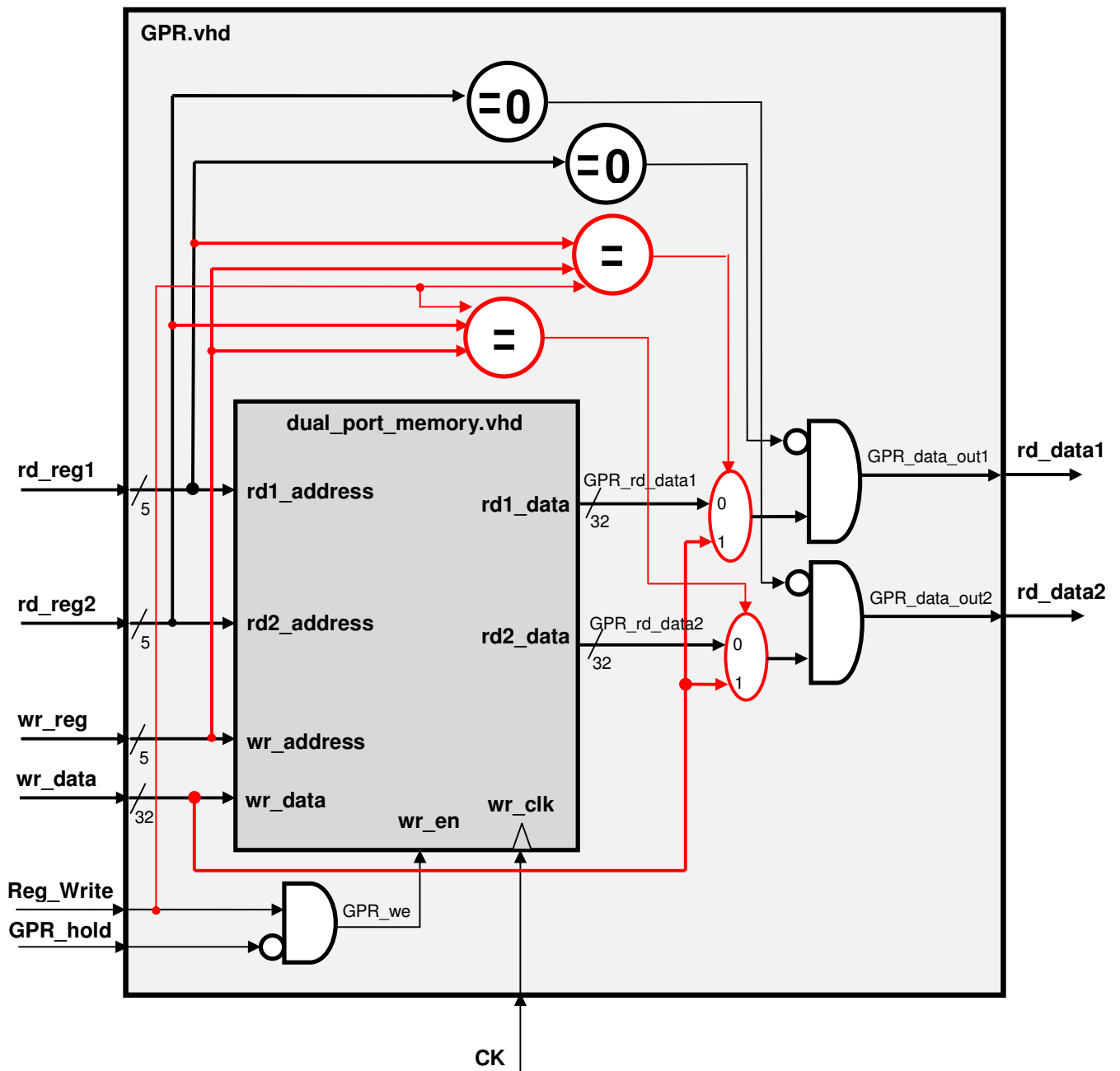


Fig. 6 – MIPS Data Path with Data Forwarding

The only two signals we added to the HW6 MIPS CPU to support Data Forwarding are A\_reg\_wt\_fwd and B\_reg\_wt\_fwd that are the outputs of two new muxes at the A and B inputs of the ALU. Actually we also need to keep the value of Rs till the EX phase so that we can use to check whether forwarding data to the A input of the ALU is required. Thus, we also added the RS\_pEX register.

Important notes:

- 1) No forwarding should be done if we read from register \$0 [see how it is handled in Fig. 6].
- 2) We need to make sure that we handle the situation properly also in cases where we have 2 or 3 previous instructions writing to the same register we are reading from in the current instruction.
- 3) We need to make sure that we use the correct data also in sw instruction.
- 4) This forwarding does not apply to lw instruction (if it is the previous instruction) since a lw instruction has valid write data only at the WB phase - after the MEM phase, while other instructions such as Rtype, addi, ori & lui that write to the GPR File have their valid data after the EX phase – from MEM phase and on.
- 5) Similarly, jal data path is different than the regular instructions and data is available for forwarding only at the WB of the jal instruction.

After adding the data forwarding muxes, we should use A\_reg\_wt\_fwd instead of A\_reg wherever the A\_reg data was used and similarly, use B\_reg\_wt\_fwd instead of B\_reg wherever the B\_reg data was used.

See more in section e below

#### d. PART III - Branch forwarding

In a similar manner, the pipeline inherent latency also creates problems when we perform a branch instruction. In order to decide whether to branch or not, we compared the data values read from both outputs of the GPR file. This means we have to wait until the data inside the GPR file is updated before we can branch. As in the data case, we would like to build a forwarding mechanism allowing us to compare the right values as soon they are available.


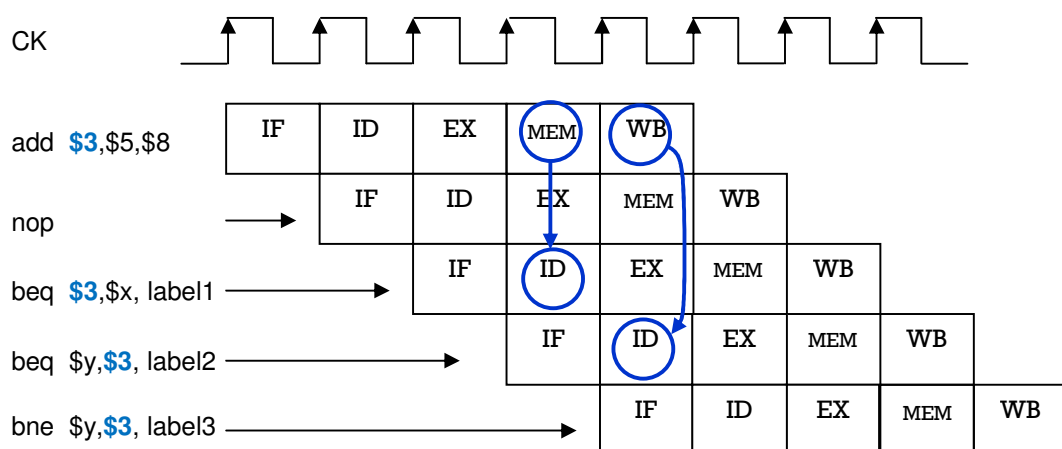


Fig. 7 – Branch Forwarding timing diagram

In Fig. 7 we see that an add instruction writes to register \$3. If we want to compare \$3 in our branch instruction, we must wait at least 1 time slot. This is so since the result of the add instruction is only available after the EX phase, i.e., from MEM phase and on. Since the branch comparison is done in its ID phase, the branch instruction's ID phase cannot be performed before the MEM phase of the add instruction. This is not enough. We need a Branch Forwarding mechanism that will bring the updated MEM phase value to the Rs\_equals\_Rt comparator. Usually this comparator compares GPR\_rd\_data1 to GPR\_rd\_data2. Only when we compare a register that was written into (actually, will be written into) by the instruction before the previous (2 instructions ago) we need to forward the MEM phase data (which is the ALUOUT\_reg data). Note that we do not need to handle Branch Forwarding from earlier instructions since from 3 instructions ago, the “transparent GPR” of the data forwarding does that for us, and from 4 instructions ago there is no forwarding problem since the GPR File is updated on time.

You should add this mechanism as depicted in Fig. 8 below.

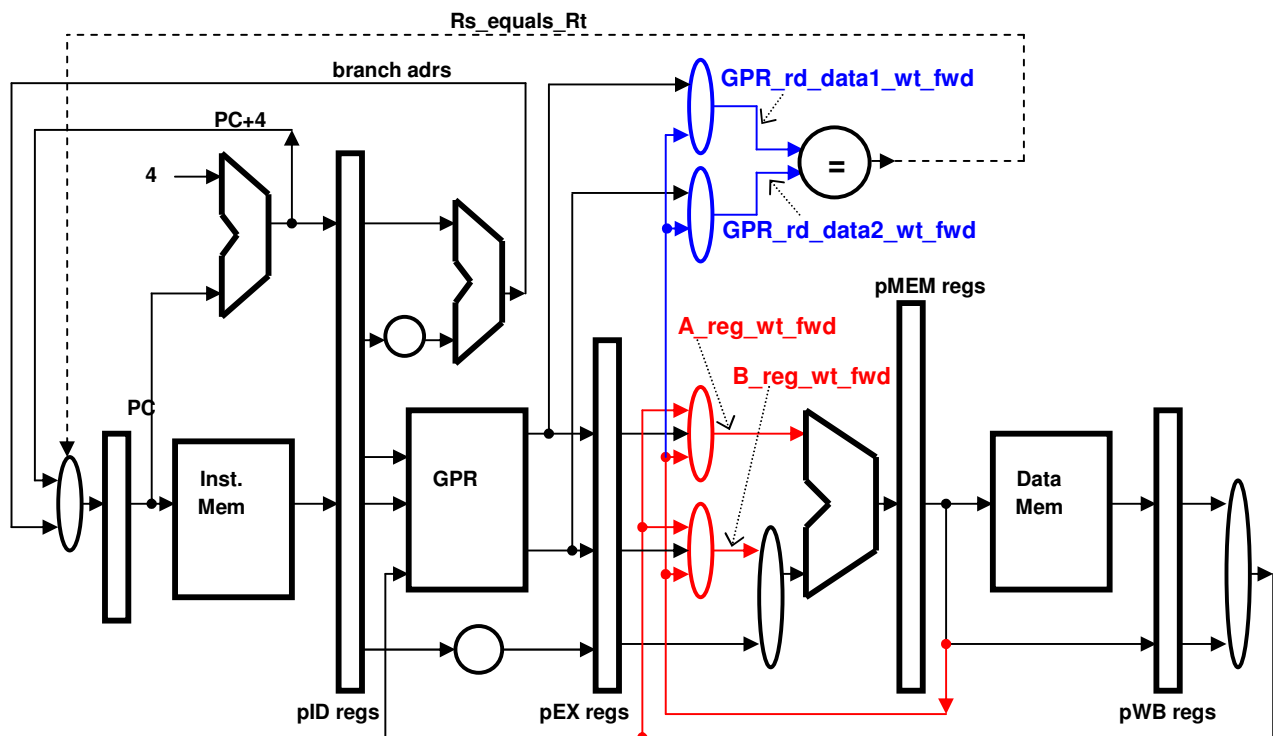

**Fig. 8 – MIPS Data Path with Data and Branch Forwarding**

The only two signals we added to the HW6 MIPS CPU to support Branch Forwarding are GPR\_rd\_data1\_wt\_fwd and GPR\_rd\_data2\_wt\_fwd that are the outputs of two new muxes at the inputs of the Rs\_equals\_Rt comparator.

Note that this mechanism should also be used by the jr instruction. In the jr instruction we have a similar latency issue. Instead of sending back the GPR\_rd\_data1 to the Fetch Unit, you need now to use the GPR\_rd\_data1\_wt\_fwd vector signal.

See more in section e below.

## Appendix A – IMem program for simulation – 2<sup>nd</sup> part

Address	label	Inst.	Rd/Rt	Rs	Rt	Imm/label	# remark	Inst. code
4001A8	cont:	addi	\$1	\$0		1000h	# prep4 sw/lw test	20011000
4001AC		nop						00000000
4001B0		addi	\$2	\$0		5555h		20025555
4001B4		addi	\$3	\$0		AAAAh		2003AAAA
4001B8		add	\$1	\$1	\$1		# 1 add once	00210820
4001BC		nop						00000000
4001C0		nop						00000000
4001C4		nop						00000000
4001C8		add	\$1	\$1	\$1		# 2 add for the 2nd time	00210820
4001CC		nop						00000000
4001D0		nop						00000000
4001D4		nop						00000000
4001D8		add	\$1	\$1	\$1		# 3	00210820
4001DC		nop						00000000
4001E0		nop						00000000
4001E4		nop						00000000
4001E8		add	\$1	\$1	\$1		# 4	00210820
4001EC		nop						00000000
4001F0		nop						00000000
4001F4		nop						00000000
4001F8		add	\$1	\$1	\$1		# 5	00210820
4001FC		nop						00000000
400200		nop						00000000
400204		nop						00000000
400208		add	\$1	\$1	\$1		# 6	00210820
40020C		nop						00000000
400210		nop						00000000
400214		nop						00000000
400218		add	\$1	\$1	\$1		# 7	00210820
40021C		nop						00000000
400220		nop						00000000
400224		nop						00000000
400228		add	\$1	\$1	\$1		# 8	00210820
40022C		nop						00000000
400230		nop						00000000
400234		nop						00000000
400238		add	\$1	\$1	\$1		# 9	00210820
40023C		nop						00000000
400240		nop						00000000

400244	nop						00000000
400248	add	\$1	\$1	\$1	# 10		00210820
40024C	nop						00000000
400250	nop						00000000
400254	nop						00000000
400258	add	\$1	\$1	\$1	# 11		00210820
40025C	nop						00000000
400260	nop						00000000
400264	nop						00000000
400268	add	\$1	\$1	\$1	# 12		00210820
40026C	nop						00000000
400270	nop						00000000
400274	nop						00000000
400278	add	\$1	\$1	\$1	# 13		00210820
40027C	nop						00000000
400280	nop						00000000
400284	nop						00000000
400288	add	\$1	\$1	\$1	# 14		00210820
40028C	nop						00000000
400290	nop						00000000
400294	nop						00000000
400298	add	\$1	\$1	\$1	# 15		00210820
40029C	nop						00000000
4002A0	nop						00000000
4002A4	nop						00000000
4002A8	add	\$1	\$1	\$1	# 16 - the 16th addition		00210820
4002AC	nop						00000000
4002B0	nop						00000000
4002B4	nop						00000000
4002B8	sw	\$2	\$1	0	# now \$1=???		AC220000
4002BC	sw	\$3	\$1	4			AC230004
4002C0	lw	\$4	\$1	0			8C240000
4002C4	lw	\$5	\$1	4			8C250004
4002C8	nop						00000000
4002CC	nop						00000000
4002D0	nop						00000000
4002D4	add	\$5	\$5	\$4			00A42820
4002D8	nop						00000000
4002DC	nop						00000000
4002E0	nop						00000000
4002E4	addi	\$5	\$5	1			20A50001
4002E8	nop						00000000
4002EC	nop						00000000

4002F0	nop				00000000
4002F4	bne	\$5	\$0	errlp	14A00007
4002F8	nop				00000000
4002FC	nop				00000000
400300	nop				00000000
400304	endlp: j			endlp	081000C1
400308	nop				00000000
40030C	nop				00000000
400310	nop				00000000
400314	errlp: j			errlp	081000C5
400318	nop				00000000
40031C	nop				00000000
400320	nop			end of errlop	00000000
400324	endlp2: j			endlp2	081000C9
400328	nop				00000000
40032C	nop				00000000
400330	nop			end of program	00000000

## **Appendix B – Rect4 - IMem program for implementation**

Address in Hex	label	instruction	Rd/ Rt	Rs/ Rt	Rt	Imm/ label	remark	MIPS Hex ode
400000	main	addi	\$1	\$0		64		20010040
400004		addi	\$2	\$0		2000h		20022000
400008		addi	\$4	\$0		16		20040010
40000C		nop						00000000
400010		nop						00000000
400014	shft_lp	add	\$2	\$2	\$2			00421020
400018		addi	\$4	\$4		-1		2084FFFF
40001C		nop						00000000
400020		nop						00000000
400024		nop						00000000
400028		bne	\$4	\$0		shft_lp		1480FFFA
40002C		nop						00000000
400030		addi	\$2	\$2		18h		20420018
400034		addi	\$3	\$0		-1		2003FFFF
400038		nop						00000000
40003C		nop						00000000
400040		nop						00000000
400044	drawlp	sw	\$3	\$2		0		AC430000
400048		addi	\$1	\$1		-1		2021FFFF
40004C		addi	\$2	\$2		52		20420034
400050		nop						00000000
400054		nop						00000000
400058		bne	\$1	\$0		drawlp		1420FFFA
40005C		nop						00000000
400060	end	j				end		08100018
400064		nop						00000000



```

1 -----
2 --
3 --
4 -- This module is the HW6_top entity for simulation      see --@@HW6 for HW6 related changes
5 --
6 --
7 -- It supports Rtype instructions of: add, sub, and, or, xor, slt
8 -- It also supports addi, beq, bne, lw & sw instructions
9 -- It also supports lui, ori, jr & jal instructions
10 --
11 -- There are 5 phases in HW6 MIPS CPU: IF, ID, EX, MEM, WB
12 --
13 --
14 -----
15 library IEEE;
16 use IEEE.STD_LOGIC_1164.ALL;
17 use IEEE.STD_LOGIC_UNSIGNED.ALL;
18 use IEEE.STD_LOGIC_ARITH.ALL;
19
20 -- *****
21 -- *****
22
23 entity HW6_top is
24 Port (
25 --- Infrastructure signals [To be used by PC via RS232 or from Nexys2 board switches & pushbuttons and VGA signals to the screen]
26 --- Host intf signals
27 RS232_Rx      : in   STD_LOGIC;
28 RS232_Tx      : out  STD_LOGIC;
29 --- VGA signals
30 VGA_h_sync    : out   STD_LOGIC;
31 VGA_v_sync    : out   STD_LOGIC;
32 VGA_red0      : out   STD_LOGIC;
33 VGA_red1      : out   STD_LOGIC;
34 VGA_red2      : out   STD_LOGIC;
35 VGA_grn0      : out   STD_LOGIC;
36 VGA_grn1      : out   STD_LOGIC;
37 VGA_grn2      : out   STD_LOGIC;
38 VGA_blu1      : out   STD_LOGIC;
39 VGA_blu2      : out   STD_LOGIC;
40 ---Flash Mem signals
41 MT_ce_n       : out   STD_LOGIC; -- '0' when accessing MOBILE SDRAM mem
42 Flash_adrs    : out   STD_LOGIC_VECTOR (23 downto 1); -- Flash read/write address
43 Flash_ce_n    : out   STD_LOGIC; -- '0' when accessing Flash mem
44 Flash_we_n    : out   STD_LOGIC; -- '0' when writing to Flash mem
45 Flash_oe_n    : out   STD_LOGIC; -- '0' when reading from Flash mem
46 Flash_rp_n    : out   STD_LOGIC; -- '0' when resetting Flash mem
47 Flash_sts     : in    STD_LOGIC; -- '1' when Flash mem FSM is done
48 Flash_data    : inout  STD_LOGIC_VECTOR (15 downto 0); -- Date read from Imem or Dmem to be written to Flash mem or data read from Flash mem to be written to :
49 ---KBD signals
50 PS2C          : in    STD_LOGIC; -- PS2 keyboard clock
51 PS2D          : in    STD_LOGIC; -- PS2 keyboard data
52 ---general signals
53 leds_out      : out   STD_LOGIC_VECTOR (7 downto 0); -- 7=Flash_sts, 6=MIPS_ck, 5=0=Host_intf version
54 CK_50MHz      : in    STD_LOGIC;
55 buttons_in    : in    STD_LOGIC_VECTOR(3 downto 0); -- btn0 is single clock (manual clock), btn3 is manual reset
56 switches_in   : in    STD_LOGIC_VECTOR (7 downto 0); -- 4-0 to select which part to be displayed on the 7Segnets LEDs
57 sevenseg_out  : out   STD_LOGIC_VECTOR (6 downto 0); -- to the 7 seg LEDs
58 anodes_out    : out   STD_LOGIC_VECTOR (3 downto 0); -- to the 7 seg LEDs
59
60 );
61 end HW6_top;
62
63 architecture Behavioral of HW6_top is
64
65 -- *****
66 -- *****
67
68
69 -- constants
70 constant MIPS_data_width : INTEGER :=32; -- data width in bits
71 constant MIPS_adrs_width : INTEGER :=32; -- Full address width of MIPS CPU
72
73
74
75 -- Put here all the components used: Clock_Driver, BYOC_Host_intf, your components
76 -- *****
77
78 -- *****
79 COMPONENT Clock_Driver is
80 port
81 (
82   CK_50MHz_IN      : in  std_logic;
83   CK_25MHz_OUT     : out std_logic
84 );
85 END COMPONENT;
86
87
88 -- *****
89 -- *****
90 COMPONENT BYOC_Host_intf is
91 Port (
92 ---*****The student's part*****
93 --- MIPS signals [to be used by students]
94 MIPS_reset      : out   STD_LOGIC; -- output to the Student's design
95 MIPS_hold       : out   STD_LOGIC; -- output to the Student's design
96 --- MIPS IMem signals
97 MIPS_IMem_adrs  : in    STD_LOGIC_VECTOR (31 downto 0); -- MIPS IMem read address
98 MIPS_IMem_rd_data : out  STD_LOGIC_VECTOR (31 downto 0); -- read data (sync read - at the rising edge of MIPS_ck, all the time)
99 --- MIPS DMem signals
100 MIPS_DMem_we    : in    STD_LOGIC; -- '1' when the CPU writes to MIPD_DMem (MIPS_DMem_wr_data is written to MIPS_DMem_adrs at the rising edge of MIPS_ck),
101 MIPS_DMem_adrs  : in    STD_LOGIC_VECTOR (31 downto 0); -- MIPS DMem read/write address
102 MIPS_DMem_wr_data : in   STD_LOGIC_VECTOR (31 downto 0); -- write data (sync write - at the rising edge of MIPS_ck, if MIPS_DMem_we='1')
103 MIPS_DMem_rd_data : out  STD_LOGIC_VECTOR (31 downto 0); -- read data (sync read - at the rising edge of MIPS_ck, all the time)
104

```

```

105 -----Other signals to be directed to i/o pins-----
106 --Flash Mem signals
107 Flash_adrs      :      out      STD_LOGIC_VECTOR (23 downto 1);-- Flash read/write address
108 Flash_ce_n      :      out      STD_LOGIC;-- '1' when accessing Flash mem
109 Flash_we_n      :      out      STD_LOGIC;-- '1' when writing to Flash mem
110 Flash_oe_n      :      out      STD_LOGIC;-- '1' when reding from Flash mem
111 Flash_rp_n      :      out      STD_LOGIC;-- '0' when resetting Flash mem
112 Flash_sts       :      in       STD_LOGIC;-- '1' when Flash mem FSM is done
113 Flash_rd_data   :      in       STD_LOGIC_VECTOR (15 downto 0);-- data read from Flash mem to be written to Imem or Dmem
114 Flash_wr_data   :      out      STD_LOGIC_VECTOR (15 downto 0);-- Date read from Imem or Dmem to be written to Flash
115 --
116 -- Infrastructure signals [To be used by PC via RS232 or from Nexys2 board switches & pushbuttons, and VGA signals to the screen],
117 -- Host intf signals
118 RS232_Rx        :      in       STD_LOGIC;
119 RS232_Tx        :      out      STD_LOGIC;
120 -- VGA signals
121 VGA_h_sync      :      out      STD_LOGIC;
122 VGA_v_sync      :      out      STD_LOGIC;
123 VGA_red0        :      out      STD_LOGIC;
124 VGA_red1        :      out      STD_LOGIC;
125 VGA_red2        :      out      STD_LOGIC;
126 VGA_grn0        :      out      STD_LOGIC;
127 VGA_grn1        :      out      STD_LOGIC;
128 VGA_grn2        :      out      STD_LOGIC;
129 VGA_blu1        :      out      STD_LOGIC;
130 VGA_blu2        :      out      STD_LOGIC;
131 --PS2 kbd signals
132 PS2_kbd_ck      :      in       STD_LOGIC;
133 PS2_kbd_data    :      in       STD_LOGIC;
134 --
135 --general signals
136 CK_25MHz        :      in       STD_LOGIC; -- main clock input to the Host interface. From this clock we create all other clock signals in the design
137 buttons_in      :      in       STD_LOGIC_VECTOR(3 downto 0);-- btn0 is single clock (manual clock), btn3 is manual reset
138 switches_in     :      in       STD_LOGIC_VECTOR (7 downto 0);-- 4-0 to select which part to be displayed on the 7Segnets LEDs
139 sevenseg_out    :      out      STD_LOGIC_VECTOR (6 downto 0);-- to the 7 seg LEDs
140 anodes_out      :      out      STD_LOGIC_VECTOR (3 downto 0);-- to the 7 seg LEDs
141 leds_out        :      out      STD_LOGIC_VECTOR (7 downto 0);-- to 8 LEDs (Leftmost = Flash status, next = MIPS_ck, 6 right ones = version number)
142 --
143 ----- additional part for the student -----
144 -- RDBK signals
145 rdbk0           :      in       STD_LOGIC_VECTOR (31 downto 0);
146 rdbk1           :      in       STD_LOGIC_VECTOR (31 downto 0);
147 rdbk2           :      in       STD_LOGIC_VECTOR (31 downto 0);
148 rdbk3           :      in       STD_LOGIC_VECTOR (31 downto 0);
149 rdbk4           :      in       STD_LOGIC_VECTOR (31 downto 0);
150 rdbk5           :      in       STD_LOGIC_VECTOR (31 downto 0);
151 rdbk6           :      in       STD_LOGIC_VECTOR (31 downto 0);
152 rdbk7           :      in       STD_LOGIC_VECTOR (31 downto 0);
153 rdbk8           :      in       STD_LOGIC_VECTOR (31 downto 0);
154 rdbk9           :      in       STD_LOGIC_VECTOR (31 downto 0);
155 rdbk10          :      in       STD_LOGIC_VECTOR (31 downto 0);
156 rdbk11          :      in       STD_LOGIC_VECTOR (31 downto 0);
157 rdbk12          :      in       STD_LOGIC_VECTOR (31 downto 0);
158 rdbk13          :      in       STD_LOGIC_VECTOR (31 downto 0);
159 rdbk14          :      in       STD_LOGIC_VECTOR (31 downto 0);
160 rdbk15          :      in       STD_LOGIC_VECTOR (31 downto 0);
161 );
162 END COMPONENT;
163
164
165 -- *****
166 -- put your components declarations here
167
168 -- *****
169 COMPONENT Fetch_Unit is
170 Port (
171 -- general input signals
172 CK_25MHz        :      in       STD_LOGIC;
173 RESET_in        :      in       STD_LOGIC;
174 HOLD_in         :      in       STD_LOGIC;
175 -- MIPS signals
176 IR_reg_pID      :      out      STD_LOGIC_VECTOR (31 downto 0);-- The IR_reg (instruction) to be used in ID
177 sext_imm_pID    :      out      STD_LOGIC_VECTOR (31 downto 0);-- The sext_imm to be used in ID
178 PC_reg_pIF      :      out      STD_LOGIC_VECTOR (31 downto 0);-- The PC_reg value in IF. To be read by TB in simulation and rdbk in implementation - for verifi
179 PC_plus_4_pID_out :      out      STD_LOGIC_VECTOR (31 downto 0);-- The PC_plus_4 value in ID --@@@HW6 JAL support - this is the address to be written to $ra ($31) in the
180 Rs_equals_Rt_pID :      in       STD_LOGIC; -- '1' if value read from Rs equals the value read from Rt, '0' otherwise. Used in branch instructions.
181 jr_adrs_in      :      in       STD_LOGIC_VECTOR (31 downto 0);-- @@@HW6 JR support -- the value to be load into the PC in jr instruction --@@@HW6 add JR support
182 -- IMem signals
183 MIPS_IMem_adrs  :      out      STD_LOGIC_VECTOR (31 downto 0);
184 MIPS_IMem_rd_data :      in      STD_LOGIC_VECTOR (31 downto 0)
185 );
186 END COMPONENT;
187
188
189 -- *****
190 COMPONENT GPR is
191 Port (
192 -- RST
193 CK              :      in       STD_LOGIC;
194 rd_reg1         :      in       STD_LOGIC_VECTOR (4 downto 0); -- Rs
195 rd_reg2         :      in       STD_LOGIC_VECTOR (4 downto 0); -- Rt
196 wr_reg         :      in       STD_LOGIC_VECTOR (4 downto 0); -- Rd (in R-Type instruction, Rt in LW)
197 rd_data1        :      out      STD_LOGIC_VECTOR (31 downto 0); -- Rs contents
198 rd_data2        :      out      STD_LOGIC_VECTOR (31 downto 0); -- Rt contents
199 wr_data         :      in       STD_LOGIC_VECTOR (31 downto 0); -- contents to be written into Rd (or Rt)
200 Reg_Write       :      in       STD_LOGIC; -- "0" means no register is written into
201 GPR_hold        :      in       STD_LOGIC -- "1" means no register is written into
202 );
203 end COMPONENT;
204
205
206 -- *****
207 COMPONENT MIPS_ALU is
208 Port (
209 -- ALU operation control inputs

```

```

210 ALUOP      : in STD_LOGIC_VECTOR(1 downto 0); -- 00=add, 01=sub, 10=by Function
211 Funct      : in STD_LOGIC_VECTOR(5 downto 0); -- 32=ADD, 34=sub, 36=AND, 37=OR, 38=XOR, 42=SLT
212 -- data inputs & data control inputs
213 A_in       : in STD_LOGIC_VECTOR(31 downto 0);
214 B_in       : in STD_LOGIC_VECTOR(31 downto 0);
215 sext_imm   : in STD_LOGIC_VECTOR(31 downto 0);
216 ALUSrcB    : in STD_LOGIC;
217 -- data output
218 ALU_out     : out STD_LOGIC_VECTOR(31 downto 0)
219 );
220 end COMPONENT;
221
222
223
224
225
226
227 -- *****
228 -- *****
229
230 -- signals connecting the components, inputs & external logic
231 -- =====
232 -- Reset and CK signals
233 signal CK : STD_LOGIC := '0';
234 signal RESET : STD_LOGIC := '0'; -- The main RESET signal combined from switches in & MIPS_reset
235 signal HOLD : STD_LOGIC := '0'; -- The main RESET signal combined from switches in & MIPS_reset
236 signal RESET_from_Host_Intf : STD_LOGIC; -- is coming from the BYOC_Host_intf
237
238
239 -- Flash data bus signals (used to connect to the Flash_data "inout" pin)
240 signal data_from_Flash : STD_LOGIC_VECTOR (15 downto 0);
241 signal data_to_Flash : STD_LOGIC_VECTOR (15 downto 0);
242 -- Flash control signals
243 signal Flash_ce_n_line : STD_LOGIC;
244 signal Flash_we_n_line : STD_LOGIC;
245 signal Flash_oe_n_line : STD_LOGIC;
246
247 signal Flash_rp_n_in_BYOC : STD_LOGIC; -- '0' when resetting Flash mem
248 signal Flash_sts_in_BYOC : STD_LOGIC; -- '1' when Flash mem FSM is done
249
250 signal leds_out_from_host_intf : STD_LOGIC_VECTOR (7 downto 0); -- 7=Flash_stts, 6=MIPS_ck, 5=Host_intf version
251
252
253
254
255 -- =====
256 -- Your design signals
257 -- =====
258
259
260 -- ===== MIPS signals =====
261 -- =====
262
263 -- ===== IF phase =====
264 -- =====
265 -- almost all signals are inside the Fetch Unit
266
267 -- except IMem signals:
268 signal IMem_adrs : STD_LOGIC_VECTOR (31 downto 0);
269 signal IMem_rd_data : STD_LOGIC_VECTOR (31 downto 0);
270
271 -- and we have the PC_reg (PC_reg_pIF) coming out of the Fetch_Unit for rdbk to Host_Intf & TB
272 signal PC_reg : STD_LOGIC_VECTOR (31 downto 0);
273
274 signal PC_plus_4_pID : STD_LOGIC_VECTOR (31 downto 0); -- @@@HW6 changes to support JAL instruction
275
276
277 -- ===== ID phase =====
278 -- =====
279 -- ID phase (a register with valid value along the ID phase)
280 signal IR_reg : STD_LOGIC_VECTOR (31 downto 0);
281 -- IR reg signals (valid in ID phase)
282 signal Opcode : STD_LOGIC_VECTOR (5 downto 0); -- IR[5:0]
283 signal Rs : STD_LOGIC_VECTOR (4 downto 0); -- IR[25:21]
284 signal Rt : STD_LOGIC_VECTOR (4 downto 0); -- IR[20:16]
285 signal Rd : STD_LOGIC_VECTOR (4 downto 0); -- IR[15:11]
286 signal Funct : STD_LOGIC_VECTOR (5 downto 0); -- IR[5:0]
287
288 signal rt_tmp : STD_LOGIC_VECTOR(4 downto 0);
289
290 -- other signals active in ID phase
291 signal sext_imm : STD_LOGIC_VECTOR (31 downto 0);
292 signal GPR_rd_data1 : STD_LOGIC_VECTOR (31 downto 0);
293 signal GPR_rd_data2 : STD_LOGIC_VECTOR (31 downto 0);
294 signal Rs_equals_Rt : STD_LOGIC; -- '1' if contents of Rs equals the contents of Rt, '0' if not.
295
296 --@@@HW6 - add JR support
297 signal jr_address : STD_LOGIC_VECTOR (31 downto 0); --the Rs value (usually from GPR_rd_data1) to be loaded into the PC in jr instruction
298
299 --@@@HW6 - adding branch forwarding
300 signal GPR_rd_data1_wt_fwd : STD_LOGIC_VECTOR (31 downto 0); --@@@HW6 adding branch forwarding
301 signal GPR_rd_data2_wt_fwd : STD_LOGIC_VECTOR (31 downto 0); --@@@HW6 adding branch forwarding
302
303
304 -- MIPS control signals - created at the ID phase
305 -----
306 -- Decoded signals for EX phase
307 signal ALUSrcB : STD_LOGIC; -- '0' selects A_reg, '1' selects sext sext_imm
308 signal ALUOP : STD_LOGIC_VECTOR (1 downto 0); -- 00=add, 01=sub, 10=by Function --@@@HW6 11=or to support ORI instruction
309 signal RegDst : STD_LOGIC; -- '0' selects Rt, '1' selects Rd
310 -- Decoded signals for MEM phase
311 signal MemWrite : STD_LOGIC; -- '1' for writing to the DMem
312 -- Decoded signals for WB phase
313 signal RegWrite : STD_LOGIC; -- '1' for writing to the GPR file
314 signal MemToReg : STD_LOGIC; -- '1' for writing MDR data to the GPR file, '0' for writing ALUout_reg_pWB data to the GPR file

```

```

315
316 signal    JAL          : STD_LOGIC;-- '1' in JAL instruction -- @@@HW6 - adding JAL instruction
317
318
319
320 ----- EX phase -----
321 -----
322 --Registerd valid in EX phase
323 signal A_reg      : STD_LOGIC_VECTOR (31 downto 0);
324 signal B_reg      : STD_LOGIC_VECTOR (31 downto 0);
325 signal sext_imm_reg : STD_LOGIC_VECTOR (31 downto 0);
326 signal Rt_pEX     : STD_LOGIC_VECTOR (4 downto 0);
327 signal Rd_pEX     : STD_LOGIC_VECTOR (4 downto 0);
328 signal ALU_output  : STD_LOGIC_VECTOR (31 downto 0);
329
330 signal PC_plus_4_pEX : STD_LOGIC_VECTOR (31 downto 0); --@@@HW6 - adding JAL instruction
331
332 signal A_reg_wt_fwd  : STD_LOGIC_VECTOR (31 downto 0); --@@@HW6 - adding data forwarding
333 signal B_reg_wt_fwd  : STD_LOGIC_VECTOR (31 downto 0); --@@@HW6 - adding data forwarding
334 signal Rs_pEX       : STD_LOGIC_VECTOR (4 downto 0); --@@@HW6 - adding data forwarding
335
336
337
338 -- MIPS control signals - created at the ID phase - delayed to EX phase
339 -----
340 -- Decoded signals for EX phase
341 signal ALUSrcB_pEX   : STD_LOGIC;
342 signal Funct_pEX     : STD_LOGIC_VECTOR (5 downto 0);--IR[5:0]
343 signal ALUOp_pEX     : STD_LOGIC_VECTOR (1 downto 0);
344 signal RegDst_pEX    : STD_LOGIC;
345 signal RegWrite_pEX  : STD_LOGIC;
346 signal MemWrite_pEX  : STD_LOGIC;
347 signal MemToReg_pEX  : STD_LOGIC;
348
349 signal JAL_pEX       : STD_LOGIC;--@@@HW6 adding JAL instruction
350
351
352
353 ----- MEM phase -----
354 -----
355 --Registerd valid in EX phase
356 signal B_reg_pMEM    : STD_LOGIC_VECTOR (31 downto 0);
357 signal Rd_pMEM       : STD_LOGIC_VECTOR (4 downto 0);
358 signal ALUout_reg    : STD_LOGIC_VECTOR (31 downto 0);
359
360 signal PC_plus_4_pMEM : STD_LOGIC_VECTOR (31 downto 0); --@@@HW6 - adding JAL instruction
361
362
363 -- MIPS control signals - created at the ID phase - delayed to EX phase
364 -----
365 -- Decoded signals for MEM phase
366 signal RegWrite_pMEM : STD_LOGIC;
367 signal MemWrite_pMEM : STD_LOGIC;
368 signal MemToReg_pMEM : STD_LOGIC;
369
370 signal JAL_pMEM       : STD_LOGIC;--@@@HW6 adding JAL instruction
371
372
373
374
375 ----- WB phase -----
376 -----
377 --Registers valid in WB phase
378 signal MDR_reg      : STD_LOGIC_VECTOR (31 downto 0); -- renaming of the MIPS_DMem_rd_data signal
379 signal ALUout_reg_pWB : STD_LOGIC_VECTOR (31 downto 0);
380 signal GPR_wr_data   : STD_LOGIC_VECTOR (31 downto 0);
381 signal Rd_pWB       : STD_LOGIC_VECTOR (4 downto 0);
382
383 signal PC_plus_4_pWB : STD_LOGIC_VECTOR (31 downto 0); --@@@HW6 adding JAL instruction
384
385
386 -- signals valid in WB phase
387 -- MIPS control signals - created at the ID phase - delayed to WB phase
388 -----
389 -- Decoded signals for WB phase
390 signal RegWrite_pWB : STD_LOGIC;
391 signal MemToReg_pWB : STD_LOGIC;
392
393 signal JAL_pWB       : STD_LOGIC;--@@@HW6 adding JAL instruction
394
395
396
397 --- ===== End of MIPS signals =====
398 --- =====
399
400
401
402 -- *****
403 -- Host Intf signals
404
405 signal rdbk3_vec : STD_LOGIC_VECTOR(31 downto 0);
406 signal rdbk4_vec : STD_LOGIC_VECTOR(31 downto 0);
407 signal rdbk5_vec : STD_LOGIC_VECTOR(31 downto 0);
408 signal rdbk12_vec : STD_LOGIC_VECTOR(31 downto 0);
409
410
411
412
413 -- *****
414
415
416
417
418
419 begin

```

```

420
421
422 -- *****
423 -- Component connections
424 -- =====
425 -- Connect all components used: Clock_Driver, BYOC_Host_intf, your components ...
426 -- =====
427
428 -- Connecting the Clock_Driver
429 -- =====
430 clock_divider : Clock_Driver
431 port map
432 (
433   CK_50MHz_IN    =>    CK_50MHz, -- directly form the HW_MIPS i/o pin
434   CK_25MHz_OUT   =>    CK      -- the CK signal to the entire HW4_MIPS design
435 );
436
437 -- Connecting the HW4_Host_intf
438 -- =====
439 host_intf : BYOC_Host_intf
440 Port Map(
441   ----- The student's part -----
442   -- MIPS signals [to be used by students]
443   MIPS_reset      =>    RESET_from_host_intf, -- The Host_intf drives the RESET signal
444   MIPS_hold       =>    HOLD,                -- The Host_intf also drives the HOLD signal
445   -- MIPS IMem signals
446   MIPS_IMem_adrs  =>    IMem_adrs,           -- driven by the Fetch_Unit
447   MIPS_IMem_rd_data =>    IMem_rd_data,       -- driven by the Host_intf and sent to the Fetch_Unit
448   -- MIPS DMem signals
449   MIPS_DMem_we    =>    MemWrite_pMEM, -- '1' if we want to write into DMem at the next rising edge of the MIPS_ck (for sw instruction)
450   MIPS_DMem_adrs  =>    ALUout_reg,        -- driven by the ALUout_reg = The address to DMem
451   MIPS_DMem_wr_data =>    B_reg_pMEM,      -- The data to be written into DMem_adrs in sw instruction
452   MIPS_DMem_rd_data =>    MDR_reg,         -- The data read from DMem_adrs in lw instruction. It is registered, i.e.= the MDR data
453   --
454   ----- Other signals to be directed to i/o pins -----
455   -- Flash Mem signals
456   Flash_adrs      =>    Flash_adrs,
457   Flash_ce_n      =>    Flash_ce_n_line,
458   Flash_we_n      =>    Flash_we_n_line,
459   Flash_oe_n      =>    Flash_oe_n_line,
460   Flash_rp_n      =>    Flash_rp_n_in_BYOC,
461   Flash_sts       =>    Flash_sts,
462   Flash_rd_data   =>    data_from_Flash,
463   Flash_wr_data   =>    data_to_Flash,
464   --
465   -- Infrastructure signals [To be used by PC via RS232 or from Nexys2 board switches & pushbuttons, and VGA signals to the screen],
466   -- Host intf signals
467   RS232_Rx        =>    RS232_Rx,
468   RS232_Tx        =>    RS232_Tx,
469   -- VGA signals
470   VGA_h_sync      =>    VGA_h_sync,
471   VGA_v_sync      =>    VGA_v_sync,
472   VGA_red0        =>    VGA_red0,
473   VGA_red1        =>    VGA_red1,
474   VGA_red2        =>    VGA_red2,
475   VGA_grn0        =>    VGA_grn0,
476   VGA_grn1        =>    VGA_grn1,
477   VGA_grn2        =>    VGA_grn2,
478   VGA_blu1        =>    VGA_blu1,
479   VGA_blu2        =>    VGA_blu2,
480   --PS2 kbd signals
481   PS2_kbd_ck      =>    PS2C,
482   PS2_kbd_data    =>    PS2D,
483   --
484   --general signals
485   CK_25MHz        =>    CK, -- CK_25MHz from the Clock_Driver
486   buttons_in      =>    buttons_in,
487   switches_in     =>    switches_in,
488   sevenseg_out    =>    sevenseg_out,
489   anodes_out      =>    anodes_out,
490   leds_out        =>    leds_out_from_host_intf,
491   --
492   ----- additional part for student -----
493   -- RDBK signals
494   rdbk0           =>    PC_reg,
495   rdbk1           =>    IR_reg,
496   rdbk2           =>    sext_imm,
497   rdbk3           =>    rdbk3_vec,
498   rdbk4           =>    rdbk4_vec,
499   rdbk5           =>    rdbk5_vec,
500   rdbk6           =>    A_reg,
501   rdbk7           =>    B_reg,
502   rdbk8           =>    sext_imm_reg,
503   rdbk9           =>    ALU_output,
504   rdbk10          =>    ALUout_reg,
505   rdbk11          =>    B_reg_pMEM,
506   rdbk12          =>    rdbk12_vec,
507   rdbk13          =>    MDR_reg,
508   rdbk14          =>    ALUout_reg_pWB,
509   rdbk15          =>    GPR_wr_data
510 );
511
512
513 -- *****
514 -- Connecting the Fetch_Unit
515 -- =====
516 fetch_unit_imp : Fetch_Unit
517 Port map (
518   -- general input signals
519   CK_25MHz        =>    CK,
520   RESET_in        =>    RESET,
521   HOLD_in         =>    HOLD,
522   -- MIPS signals
523   IR_reg_pID      =>    IR_reg, -- connecting IR_reg_pID to the signal called IR_reg
524   sext_imm_pID    =>    sext_imm, -- same for the signal called sext_imm

```

```

525 PC_reg_pIF      =>      PC_reg,
526 PC_plus_4_pID_out =>      PC_plus_4_pID, --@@@HW6 for JR support
527 Rs_equals_Rt_pID =>      Rs_equals_Rt,
528 jr_adrs_in       =>      jr_address, --@@@HW6 for JR support
529 -- IMem signals
530 MIPS_IMem_adrs   =>      IMem_adrs,
531 MIPS_IMem_rd_data =>      IMem_rd_data
532 );
533
534
535
536 -- Connecting the GPR file
537 -- =====
538 GPR_file : GPR
539 Port map (
540 --RST      =>      not connected
541 CK         =>      CK,
542 rd_reg1    =>      Rs,
543 rd_reg2    =>      Rt,
544 wr_reg     =>      Rd_pWB,
545 rd_data1   =>      GPR_rd_data1,
546 rd_data2   =>      GPR_rd_data2,
547 wr_data    =>      GPR_wr_data,
548 Reg_Write  =>      RegWrite_pWB,
549 GPR_hold   =>      HOLD -- ,
550 );
551
552
553 -- Connecting the MIPS_ALU
554 -- =====
555 ALU : MIPS_ALU
556 Port map (
557 -- ALU operation control inputs
558 ALUOP      =>      ALUOP_pEX,
559 Funct      =>      Funct_pEX,
560 -- data inputs & data control inputs
561 A_in       =>      A_reg_wt_fwd, -- @@@HW6 should be A_reg_wt_fwd for adding data forwarding in EX phase
562 B_in       =>      B_reg_wt_fwd, -- @@@HW6 should be B_reg_wt_fwd for adding data forwarding in EX phase
563 sext_imm   =>      sext_imm_reg,
564 ALUsrcB    =>      ALUsrcB_pEX,
565 -- data output
566 ALU_out    =>      ALU_output
567 );
568
569
570
571 -- all signal equations
572
573
574 -- Signals to external components
575 -- =====
576 -- disconnecting the Mobile SRAM
577 MT_ce_n    <= '1' ; -- making sure that the SRAM is not active
578
579 -- connecting Flash_data bidir signal
580 data_from_Flash    <= Flash_data;
581 Flash_data    <= data_to_Flash when (Flash_oe_n_line = '1' and Flash_ce_n_line = '0') else (others => 'Z');
582
583 -- connecting other Flash signals
584 Flash_ce_n    <= Flash_ce_n_line;
585 Flash_oe_n    <= Flash_oe_n_line;
586 Flash_we_n    <= Flash_we_n_line;
587
588 Flash_rp_n    <= Flash_rp_n_in_BYOC and ( not switches_in(4) );
589 Flash_sts_in_BYOC    <= Flash_sts;
590
591 -- leds_out(7) <= Flash_sts_in_BYOC ;
592 leds_out      <= Flash_sts_in_BYOC & leds_out_from_host_intf(6 downto 0); -- 7=Flash_stts, 6=MIPS_ck, 5=0=Host_intf version
593
594
595 -- General signals
596 -- =====
597 RESET    <= switches_in(6) or RESET_from_Host_Intf;
598
599
600 -- Here is your part, i.e., your equations
601
602 -- ===== IF phase processes =====
603 -- =====
604 -- no such processes. They are all inside the Fetch Unit
605
606 -- ===== ID phase processes =====
607 -- =====
608 -- IR fields signals
609 Opcode    <= IR_reg(31 downto 26);
610 --Rs      <= IR_reg(25 downto 21);
611 -----
612 --Rt      <= IR_reg(20 downto 16); --@@@HW6 a change is required here to support JAL
613 -----
614 Rd        <= IR_reg(15 downto 11);
615 Funct     <= IR_reg(5 downto 0);
616
617 --beq & bne & jr forwarding --@@@HW6 adding branch & JR forwarding
618 --A mux of the Rs_equal_Rt comparator (beq/bne forwarding)
619 process (RegWrite_pMEM, Rd_pMEM, Rs, GPR_rd_data1, ALUout_reg)
620 begin
621     if RegWrite_pMEM = '1' and Rd_pMEM = Rs and Rs /= b"00000" then
622         GPR_rd_data1_wt_fwd <= ALUout_reg;
623     else
624         GPR_rd_data1_wt_fwd <= GPR_rd_data1;
625     end if;
626 end process;
627
628 --B mux of the Rs_equal_Rt comparator (beq/bne forwarding) --@@@HW6 adding branch & JR forwarding
629 process (RegWrite_pMEM, Rd_pMEM, Rt, GPR_rd_data2, ALUout_reg)

```

```

630 begin
631   if RegWrite_pMEM = '1' and Rd_pMEM = Rt and Rt /= b"00000" then
632     GPR_rd_data2_wt_fwd <= ALUout_reg;
633   else
634     GPR_rd_data2_wt_fwd <= GPR_rd_data2;
635   end if;
636 end process;
637
638 --beq/bne comparator      --@@@HW6 adding branch forwarding means a change here
639 process (GPR_rd_data1_wt_fwd, GPR_rd_data2_wt_fwd)
640 begin
641   if GPR_rd_data1_wt_fwd = GPR_rd_data2_wt_fwd then
642     Rs_equals_Rt <= '1';
643   else
644     Rs_equals_Rt <= '0';
645   end if;
646 end process;
647
648 ---@@@HW6 add JR support    -- HW6 adding JR forwarding means a change here
649 jr_address <= GPR_rd_data1_wt_fwd;
650
651
652
653
654
655 -- Control decoder - calculates the signals in ID phase
656 -- creates the following signals according to the opcode:
657 --      ALUSrcB      '0' - selects B_reg, '1' - selects sext_imm_reg
658 --      ALUOP        b"00" - add, b"01" - sub, b"10" - the Function field determines the ALU operation, b"11" - or --@@@HW6 adding ORI support
659 --      RegDst       '1' - "Rd"=Rd (write to Rd - in Rtype inst. only), '0' - "Rd"=Rt (write to Rt - in all other instructions)
660 --      MemWrite     '1' - write to DMem
661 --      MemToReg     '0' - write ALUout_reg data (to "Rd"), '1' - write MDR_reg data (to "Rd")
662 --      RegWrite     '1' - write to GPR file (to "Rd")
663 --      JAL         '1' - wrhen we are in jal instruction --@@@HW6 adding JAL support
664 process (Opcode, IR_reg)
665 begin
666   if Opcode = 8 or Opcode = 13 or Opcode = 15 or Opcode = 35 or Opcode = 43 then --addi or ori or Lui or Lw or sw
667     ALUSrcB <= '1';
668   else
669     ALUSrcB <= '0';
670   end if;
671
672   if Opcode = 0 then --rtype
673     ALUOP <= b"10";
674   elsif Opcode = 4 or Opcode = 5 then --beq and bne
675     ALUOP <= b"01";
676   elsif Opcode = 13 then -- ori
677     ALUOP <= b"11";
678   else
679     ALUOP <= b"00";
680   end if;
681
682   if Opcode = 0 then --rtype
683     RegDst <= '1';
684   else
685     RegDst <= '0';
686   end if;
687
688   if Opcode = 43 then --sw
689     MemWrite <= '1';
690   else
691     MemWrite <= '0';
692   end if;
693
694   if Opcode = 35 then --Lw
695     MemToReg <= '1';
696   else
697     MemToReg <= '0';
698   end if;
699
700
701   if Opcode = 0 or Opcode = 8 or Opcode = 13 or Opcode = 15 or Opcode = 3 or Opcode = 35 then --rtype or addi or ori or Lui or jal or Lw
702     RegWrite <= '1';
703   else
704     RegWrite <= '0';
705   end if;
706
707   if Opcode = 3 then --jal
708     JAL <= '1';
709     Rt <= b"11111";
710   else
711     JAL <= '0';
712     Rt <= IR_reg(20 downto 16);
713   end if;
714
715   if Opcode = 15 then --Lui
716     Rs <= b"00000";
717   else
718     Rs <= IR_reg(25 downto 21);
719   end if;
720
721 end process;
722
723
724 -- ===== EX phase processes =====
725 -- =====
726 -- A & B registers
727 process (RESET, CK)
728 begin
729   if RESET='1' then
730     A_reg <= x"00000000";
731   elsif CK'event and CK='1' and HOLD='0' then
732     A_reg <= GPR_rd_data1;
733   end if;
734 end process;

```

```

735
736 process (RESET, CK)
737 begin
738     if RESET='1' then
739         B_reg <= x"00000000";
740     elsif CK'event and CK='1' and HOLD = '0' then
741         B_reg <= GPR_rd_data2;
742     end if;
743 end process;
744
745 -- with forwarding
746 -- src_A mux (forwarding)
747 process (RegWrite_pMEM, Rd_pMEM, Rs_pEX, RegWrite_pWB, Rd_pWB, JAL_pMEM, GPR_wr_data, ALUout_reg, A_reg)
748 begin
749     if RegWrite_pMEM = '1' and Rd_pMEM = Rs_pEX and Rs_pEX /= b"00000" and JAL_pMEM = '0' then
750         A_reg_wt_fwd <= ALUout_reg;
751     elsif RegWrite_pWB = '1' and Rd_pWB = Rs_pEX and Rs_pEX /= b"00000" then
752         A_reg_wt_fwd <= GPR_wr_data;
753     else
754         A_reg_wt_fwd <= A_reg;
755     end if;
756 end process;
757
758 -- src B mux (forwarding part)
759 process (RegWrite_pMEM, Rd_pMEM, Rt_pEX, RegWrite_pWB, Rd_pWB, JAL_pMEM, GPR_wr_data, ALUout_reg, B_reg)
760 begin
761     if RegWrite_pMEM = '1' and Rd_pMEM = Rt_pEX and Rt_pEX /= b"00000" and JAL_pMEM = '0' then
762         B_reg_wt_fwd <= ALUout_reg;
763     elsif RegWrite_pWB = '1' and Rd_pWB = Rt_pEX and Rt_pEX /= b"00000" then
764         B_reg_wt_fwd <= GPR_wr_data;
765     else
766         B_reg_wt_fwd <= B_reg;
767     end if;
768 end process;
769
770
771 -- sext_imm register
772 process (RESET, CK)
773 begin
774     if RESET='1' then
775         sext_imm_reg <= x"00000000";
776     elsif CK'event and CK='1' and HOLD = '0' then
777         sext_imm_reg <= sext_imm;
778     end if;
779 end process;
780
781 -- Rs register --@@@HW6 added for data forwarding support
782 process (RESET, CK)
783 begin
784     if RESET='1' then
785         Rs_pEX <= b"00000";
786     elsif CK'event and CK='1' and HOLD = '0' then
787         Rs_pEX <= Rs;
788     end if;
789 end process;
790
791 -- Rt register
792 process (RESET, CK)
793 begin
794     if RESET='1' then
795         Rt_pEX <= b"00000";
796     elsif CK'event and CK='1' and HOLD = '0' then
797         Rt_pEX <= Rt;
798     end if;
799 end process;
800
801 -- Rd register
802 process (RESET, CK)
803 begin
804     if RESET='1' then
805         Rd_pEX <= b"00000";
806     elsif CK'event and CK='1' and HOLD = '0' then
807         Rd_pEX <= Rd;
808     end if;
809 end process;
810
811 -- PC_plus_4_pEX --@@@HW6 added to support JAL instruction
812 process (RESET, CK)
813 begin
814     if RESET='1' then
815         PC_plus_4_pEX <= x"00000000";
816     elsif CK'event and CK='1' and HOLD = '0' then
817         PC_plus_4_pEX <= PC_plus_4_pID;
818     end if;
819 end process;
820
821 -- control signals regs --@@@HW6 add JAL support here to
822 process (RESET, CK)
823 begin
824     if RESET='1' then
825         ALUsrcB_pEX <= '0';
826         Funct_pEX <= b"000000";
827         ALUOP_pEX <= b"00";
828         RegDst_pEX <= '0';
829         RegWrite_pEX <= '0';
830         MemWrite_pEX <= '0';
831         MemToReg_pEX <= '0';
832         JAL_pEX <= '0';
833     elsif CK'event and CK='1' and HOLD = '0' then
834         ALUsrcB_pEX <= ALUsrcB;
835         Funct_pEX <= Funct;
836         ALUOP_pEX <= ALUOP;
837         RegDst_pEX <= RegDst;
838         RegWrite_pEX <= RegWrite;
839         MemWrite_pEX <= MemWrite;

```



```

840     MemToReg_pEX <= MemToReg;
841     JAL_pEX <= JAL;
842 end if;
843 end process;
844
845 -- RegWrite_pEX, MemToReg_pEX, MemWrite_pEX FFs
846
847
848
849 -- ===== MEM phase processes =====
850 -- =====
851 -- ALUOUT register
852 process (RESET, CK)
853 begin
854     if RESET='1' then
855         ALUout_reg <= x"00000000";
856     elsif CK'event and CK='1' and HOLD='0' then
857         ALUout_reg <= ALU_output;
858     end if;
859 end process;
860
861 -- B delayed reg --@@@HW6 need a change for data forwarding support
862 process (RESET, CK) -----
863 begin
864     if RESET='1' then
865         B_reg_pMEM <= x"00000000";
866     elsif CK'event and CK='1' and HOLD='0' then
867         if RegWrite_pMEM = '1' and Rd_pMEM = Rt_pEX and Rt_pEX /= b"00000" and JAL_pMEM = '0' then
868             B_reg_pMEM <= B_reg_wt_fwd;
869         elsif RegWrite_pWB = '1' and Rd_pWB = Rt_pEX and Rt_pEX /= b"00000" then
870             B_reg_pMEM <= B_reg_wt_fwd;
871         else
872             B_reg_pMEM <= B_reg;
873         end if;
874     end if;
875 end process;
876
877 -- RegDst mux and Rd_pMEM register
878 process (RESET, CK, RegDst_pEX, Rt_pEX, Rd_pEX)
879 begin
880     if RESET='1' then
881         Rd_pMEM <= b"00000";
882     elsif CK'event and CK='1' and HOLD='0' then
883         if RegDst_pEX = '0' then
884             Rd_pMEM <= Rt_pEX;
885         else
886             Rd_pMEM <= Rd_pEX;
887         end if;
888     end if;
889 end process;
890
891 -- PC_plus_4_pMEM reg --@@@HW6 added to support JAL instruction
892 process (RESET, CK)
893 begin
894     if RESET='1' then
895         PC_plus_4_pMEM <= x"00000000";
896     elsif CK'event and CK='1' and HOLD='0' then
897         PC_plus_4_pMEM <= PC_plus_4_pEX;
898     end if;
899 end process;
900
901 -- control signals FFs
902 -- RegWrite_pMEM, MemToReg_pMEM, MemWrite_pEX FFs --@@@HW6 add JAL_pMEM to support JAL
903 process (RESET, CK)
904 begin
905     if RESET='1' then
906         RegWrite_pMEM <= '0';
907         MemToReg_pMEM <= '0';
908         MemWrite_pMEM <= '0';
909         JAL_pMEM <= '0';
910     elsif CK'event and CK='1' and HOLD='0' then
911         RegWrite_pMEM <= RegWrite_pEX;
912         MemToReg_pMEM <= MemToReg_pEX;
913         MemWrite_pMEM <= MemWrite_pEX;
914         JAL_pMEM <= JAL_pEX;
915     end if;
916 end process;
917
918 -- ===== WB phase processes =====
919 -- =====
920 -- MDR_reg - no need to define -- connected directly from BYOC_Host_intf - resides inside the DMem
921
922 --ALUout_pWB register
923 process (RESET, CK)
924 begin
925     if RESET='1' then
926         ALUout_reg_pWB <= x"00000000";
927     elsif CK'event and CK='1' and HOLD='0' then
928         ALUout_reg_pWB <= ALUout_reg;
929     end if;
930 end process;
931
932 -- MemToReg mux --@@@HW6 requires changes to support JAL instruction
933 process (MemToReg_pWB, MDR_reg, ALUout_reg_pWB, PC_plus_4_pWB, JAL_pWB)
934 begin
935     if JAL_pWB = '1' then
936         GPR_wr_data <= PC_plus_4_pWB;
937     elsif MemToReg_pWB = '1' then
938         GPR_wr_data <= MDR_reg;
939     else
940         GPR_wr_data <= ALUout_reg_pWB;
941     end if;
942 end process;
943
944 -- Rd_pWB register

```

```

945 process (RESET, CK)
946 begin
947     if RESET='1' then
948         Rd_pWB <= b"00000";
949     elsif CK'event and CK='1' and HOLD='0' then
950         Rd_pWB <= Rd_pMEM;
951     end if;
952 end process;
953
954 -- PC_plus_4_pWB --@@@HW6 added to support JAL instruction
955 process (RESET, CK)
956 begin
957     if RESET='1' then
958         PC_plus_4_pWB <= x"00000000";
959     elsif CK'event and CK='1' and HOLD='0' then
960         PC_plus_4_pWB <= PC_plus_4_pMEM;
961     end if;
962 end process;
963
964 -- control signals FFs
965 -- RegWrite_pWB, MemToReg_pWB FFs --@@@HW6 added JAL_pWB FF to support JAL instruction
966 process (RESET, CK)
967 begin
968     if RESET='1' then
969         RegWrite_pWB <= '0';
970         MemToReg_pWB <= '0';
971         JAL_pWB <= '0';
972     elsif CK'event and CK='1' and HOLD='0' then
973         RegWrite_pWB <= RegWrite_pMEM;
974         MemToReg_pWB <= MemToReg_pMEM;
975         JAL_pWB <= JAL_pMEM;
976     end if;
977 end process;
978
979 -- *****
980 --build special rdbk signals
981 rdbk3_vec <= b"000" & Rs & b"000" & Rt & b"000" & Rd & b"00" & Funct;
982 rdbk4_vec <= b"000" & RegWrite & b"0000" & b"00000000" & b"00000000" & b"0000" & b"000" & Rs_equals_Rt;
983 rdbk5_vec <= b"000" & ALUSrcB_pEX & b"0000" & b"00000000" & b"0000" & b"00" & ALUOP_pEX & "00" & Funct_pEX;
984 rdbk12_vec <= MemWrite_pMem & b"00" & MemToReg_pMEM & b"000" & RegWrite_pMEM & b"000" & Rd_pMEM & b"000" & MemToReg_pWB & b"000" & RegWrite_pWB & b"000" & Rd_pWB
985
986
987
988
989 -- *****
990
991
992
993 end Behavioral;
994
995 -- *****
996 -- *****

```

```

1  --
2  --
3  -- This module is the Fetch Unit
4  --
5  --
6  --
7  --
8  --
9  -----
10 library IEEE ;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.STD_LOGIC_ARITH.ALL;
13 use IEEE.STD_LOGIC_UNSIGNED.ALL;
14
15 -- *****
16 -- *****
17
18 entity Fetch_Unit is
19 Port (
20 --
21 CK_25MHz          : in STD_LOGIC;
22 RESET_in          : in STD_LOGIC;
23 HOLD_in           : in STD_LOGIC;
24 -- IMem signals
25 MIPS_IMem_adrs    : out STD_LOGIC_VECTOR (31 downto 0);
26 MIPS_IMem_rd_data : in STD_LOGIC_VECTOR (31 downto 0);
27 IR_reg_pID        : out STD_LOGIC_VECTOR (31 downto 0);
28 sext_imm_pID      : out STD_LOGIC_VECTOR (31 downto 0);
29 PC_reg_pIF        : out STD_LOGIC_VECTOR (31 downto 0);
30 Rs_equals_Rt_pID  : in STD_LOGIC;
31 jr_adrs_in        : in STD_LOGIC_VECTOR (31 downto 0); --@@@HW6
32 PC_plus_4_pID_out : out STD_LOGIC_VECTOR (31 downto 0); --@@@HW6
33 );
34 end Fetch_Unit;
35
36
37 architecture Behavioral of Fetch_Unit is
38
39 -- *****
40 -- *****
41
42
43 --- ===== Host intf signals =====
44 -----
45 signal RESET          : STD_LOGIC; -- is coming directly from the Fetch_Unit_Host_intf
46 signal CK              : STD_LOGIC; -- is coming directly from the Fetch_Unit_Host_intf
47 signal HOLD           : STD_LOGIC; -- is coming directly from the Fetch_Unit_Host_intf
48 signal IMem_adrs      : STD_LOGIC_VECTOR(31 downto 0);
49 signal IMem_rd_data   : STD_LOGIC_VECTOR(31 downto 0);
50
51
52 -- ===== MIPS signals =====
53 -----
54
55 -- ===== IF phase =====
56 -----
57 --- IR & related signals
58 signal IR_reg          : STD_LOGIC_VECTOR (31 downto 0) := x"00000000";
59 signal imm             : STD_LOGIC_VECTOR (15 downto 0);
60 signal sext_imm        : STD_LOGIC_VECTOR (31 downto 0);
61 signal opcode          : STD_LOGIC_VECTOR (5 downto 0);
62 signal funct           : STD_LOGIC_VECTOR (5 downto 0);
63
64 -- PC
65 signal PC_reg          : STD_LOGIC_VECTOR (31 downto 0) := x"00000000";
66
67 -- PC_mux
68 -- control signal of PC_mux
69 signal PC_Source       : STD_LOGIC_VECTOR (1 downto 0); -- 0=PC+4, 1=BRANCH, 2=JR, 3=JUMP

```

```

70 -- input signals to PC_mux
71 signal PC_plus_4          : STD_LOGIC_VECTOR (31 downto 0);
72 signal jump_adrs         : STD_LOGIC_VECTOR (31 downto 0);
73 signal branch_adrs       : STD_LOGIC_VECTOR (31 downto 0);
74 signal jr_adrs           : STD_LOGIC_VECTOR (31 downto 0);
75 -- output
76 signal PC_mux_out        : STD_LOGIC_VECTOR (31 downto 0);
77
78
79 signal PC_plus_4_pID      : STD_LOGIC_VECTOR (31 downto 0);
80
81
82
83 ===== End of MIPS signals =====
84 =====
85
86
87 -- additional "complex" rdbk signals
88 signal rdbk_vec1         : STD_LOGIC_VECTOR (31 downto 0);
89 signal rdbk_vec2         : STD_LOGIC_VECTOR (31 downto 0);
90
91
92
93
94 -- *****
95
96
97 begin
98
99 -- Connecting the Fetch_Unit pins to inner signals
100 -- =====
101 -- MIPS signals [to be used by students]
102 CK              <=      CK_25MHz;
103 RESET           <=      RESET_in;
104 HOLD            <=      HOLD_in;
105 MIPS_IMem_adrs  <=      IMem_adrs;
106 IMem_rd_data    <=      MIPS_IMem_rd_data;
107 -- RDBK signals [to be used by students]
108
109 --
110 IR_reg_pID <= MIPS_IMem_rd_data;
111 sext_imm_pID <= sext_imm;
112 PC_reg_pIF <= PC_reg;
113
114
115
116 -- @@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@
117 -- your Fetch_Unit code starts here <<< @@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@
118 -- @@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@
119
120 -- ===== IF phase processes =====
121 -- =====
122 -- PC register
123 process (RESET, CK, opcode)
124 begin
125     if RESET='1' then
126         PC_reg <= x"00400000";
127     elsif CK'event and CK='1' and HOLD='0' then
128         if opcode = 2 or opcode = 3 then
129             PC_reg <= jump_adrs; --@@@HW6
130         else
131             PC_reg <= PC_mux_out;
132         end if ;
133     end if;
134 end process;
135
136 IMem_adrs <= PC_reg; -- connect PC_reg to IMem_adrs
137
138 -- PC source mux
139 process (PC Source, PC plus 4, branch adrs, jr adrs, jump adrs)

```

```

140 begin
141   if PC_Source = b"00" then --PC_plus_4
142     PC_mux_out <= PC_plus_4;
143   elsif PC_Source = b"01" then --branch_adrs
144     PC_mux_out <= branch_adrs;
145   elsif PC_Source = b"10" then --jr_instruction
146     PC_mux_out <= jr_adrs;
147   elsif PC_Source = b"11" then --jump_adrs
148     PC_mux_out <= jump_adrs;
149   end if;
150 end process;
151
152 -- PC Adder - incrementing PC by 4   (create the PC_plus_4 signal)
153 PC_plus_4 <= PC_reg + 4;
154
155
156 -- IR_reg   (rename of the IMem_rd_data signal)
157 IR_reg <= IMem_rd_data;
158
159 imm <= IR_reg(15 downto 0);
160
161
162 -- imm sign extension   (create the sext_imm signal)
163 process (imm, opcode)
164 begin
165   if opcode = 15 then -- Lui
166     sext_imm <= imm & x"0000"; --@@@HW6
167   elsif opcode /= 13 then -- @@@HW6 not ori
168     if imm(15) = '0' then
169       sext_imm <= x"0000" & imm;
170     elsif imm(15) = '1' then
171       sext_imm <= x"FFFF" & imm;
172     end if;
173   else
174     sext_imm <= x"0000" & imm;
175   end if;
176 end process;
177
178 -- BRANCH address   (create the branch_adrs signal)
179 branch_adrs <= (sext_imm(29 downto 0) & b"00") + PC_plus_4_pID;
180
181 -- JUMP address     (create the jump_adrs signal)
182 jump_adrs <= PC_plus_4_pID(31 downto 28) & IR_reg(25 downto 0) & b"00";
183
184 -- JR address       (create the jr_adrs signal)
185 jr_adrs <= jr_adrs_in; --@@@HW6
186 PC_plus_4_pID_out <= PC_plus_4_pID; --@@@HW6
187
188 -- PC_plus_4_pID register   (create the PC_plus_4_pID signal)
189 process (RESET, CK)
190 begin
191   if RESET='1' then
192     PC_plus_4_pID <= x"00000000";
193   elsif CK'event and CK='1' and HOLD='0' then
194     PC_plus_4_pID <= PC_plus_4;
195   end if;
196 end process;
197
198 -- instruction decoder
199 opcode <= IR_reg (31 downto 26);
200 funct <= IR_reg (5 downto 0);
201
202
203 -- PC_source decoder   (create the PC_source signal)
204 process (opcode, funct, Rs_equals_Rt_pID)
205 begin
206   if opcode = b"000010" or opcode = b"000011" then --j or jal
207     PC_source <= b"11"; --jump_adrs
208   elsif opcode = b"000100" and Rs_equals_Rt_pID = '1' then -- beq
209     PC_source <= b"01"; --branch_adrs

```

```

210     elsif opcode = b"000101" and Rs_equals_Rt_pID = '0' then -- bne
211         PC_source <= b"01"; --branch_adrs
212     elsif opcode = b"000000" and funct = b"001000" then -- jr
213         PC_source <= b"10"; --jr_instruction
214     else --any other
215         PC_source <= b"00"; --PC_plus_4
216     end if;
217 end process;
218
219
220 -- @@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@
221 -- your Fetch_Unit code ends here <<<@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@
222 -- @@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@@
223
224
225
226 -- rdbk signals
227 rdbk_vec1 <= x"0000000" & b"00" & PC_source; -- add Leading zeros to create 32 bit vec
228
229
230
231
232
233
234 end Behavioral;
235
236 -- *****
237 -- *****

```

```

1 -- This module is the MIPS General Purpose Register (GPR) file implementation for HW3
2 --
3 --
4 --
5 -----
6 library IEEE;
7 use IEEE.STD_LOGIC_1164.ALL;
8 use IEEE.STD_LOGIC_ARITH.ALL;
9 use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11
12 entity GPR is
13 Port(
14
15 CK          :    in      STD_LOGIC;
16 rd_reg1     :    in      STD_LOGIC_VECTOR (4 downto 0);-- Rs
17 rd_reg2     :    in      STD_LOGIC_VECTOR (4 downto 0);-- Rt
18 wr_reg      :    in      STD_LOGIC_VECTOR (4 downto 0);-- Rd (in R-Type instruction, Rt in LW)
19 rd_data1    :    out     STD_LOGIC_VECTOR (31 downto 0);-- Rs contents
20 rd_data2    :    out     STD_LOGIC_VECTOR (31 downto 0);-- Rt contents
21 wr_data     :    in      STD_LOGIC_VECTOR (31 downto 0);-- contents to be written into Rd (or Rt)
22 Reg_Write   :    in      STD_LOGIC;-- "0" means no register is written into
23 GPR_hold    :    in      STD_LOGIC-- "1" means no register is written into
24
25 );
26 end GPR;
27
28
29 architecture Behavioral of GPR is
30
31 --signals used
32 signal Equal      : STD_LOGIC;
33 signal GPR_rd_data1 : STD_LOGIC_VECTOR (31 downto 0);-- Rt contents
34 signal GPR_rd_data2 : STD_LOGIC_VECTOR (31 downto 0);-- Rt contents
35 signal GPR_data_out1 : STD_LOGIC_VECTOR (31 downto 0);-- Rt contents
36 signal GPR_data_out2 : STD_LOGIC_VECTOR (31 downto 0);-- Rt contents
37 signal GPR_wr_data  : STD_LOGIC_VECTOR (31 downto 0);-- Rt contents
38
39 signal GPR_we      : STD_LOGIC;-- the we signal to the memory. made of (Reg_Write and (not GPR_hold))
40
41
42 -- components used
43 COMPONENT dual_port_memory_no_CLK_read IS
44 GENERIC(
45     width : integer :=32;
46     depth : integer :=32
47 );
48 PORT (
49     wr_address : in integer range depth-1 downto 0;
50     wr_data    : in std_logic_vector(width-1 downto 0);
51     wr_clk     : in std_logic;
52     wr_en      : in std_logic;
53     rd1_address : in integer range depth-1 downto 0;
54     rd1_data    : out std_logic_vector(width-1 downto 0);
55     rd2_address : in integer range depth-1 downto 0;
56     rd2_data    : out std_logic_vector(width-1 downto 0)
57 );
58 END COMPONENT;
59
60
61
62 begin
63
64 GPR_wr_data <= wr_data;
65
66
67 -- produce rd_data1:
68 -- Here we ensure that reg 0 is always zero
69 process(rd_reg1, GPR_rd_data1, wr_reg, GPR_wr_data, Reg_Write)
70 begin
71     if rd_reg1 = b"00000" then

```

```

72     GPR_data_out1 <= x"00000000";
73     elsif rd_reg1 = wr_reg and Reg_Write = '1' then
74         GPR_data_out1 <= GPR_wr_data;
75     else
76         GPR_data_out1 <= GPR_rd_data1;
77     end if;
78 end process;
79
80 rd_data1 <= GPR_data_out1;
81
82 --process (rd_reg1, wr_reg, Reg_Write) --@@@HW6
83 --begin
84 --     if rd_reg1 = wr_reg and Reg_Write = '1' then
85 --         rd_data1 <= wr_data;
86 --     else
87 --         rd_data1 <= GPR_data_out1;
88 --     end if ;
89 --end process;
90
91
92 -- produce rd_data2:
93 -- Here we ensure that reg 0 is always zero
94 process(rd_reg2, GPR_rd_data2, wr_reg, GPR_wr_data, Reg_Write)
95 begin
96     if rd_reg2 = b"00000" then
97         GPR_data_out2 <= x"00000000";
98     elsif rd_reg2 = wr_reg and Reg_Write = '1' then
99         GPR_data_out2 <= GPR_wr_data;
100    else
101        GPR_data_out2 <= GPR_rd_data2;
102    end if;
103 end process;
104
105 rd_data2 <= GPR_data_out2;
106
107 --process (rd_reg2, wr_reg, Reg_Write) --@@@HW6
108 --begin
109 --     if rd_reg2 = wr_reg and Reg_Write = '1' then
110 --         rd_data2 <= wr_data;
111 --     else
112 --         rd_data2 <= GPR_data_out2;
113 --     end if ;
114 --end process;
115
116
117 GPR_we <= Reg_Write and (not GPR_hold);
118
119 -- connecting the GPR memory
120 GPR_file : dual_port_memory_no_CLK_read
121 generic map (32, 32)
122 port map(
123     wr_address    =>    conv_integer(wr_reg),
124     wr_data        =>    GPR_wr_data,
125     wr_clk         =>    CK,
126     wr_en          =>    GPR_we,
127     rd1_address    =>    conv_integer(rd_reg1),
128     rd1_data       =>    GPR_rd_data1,
129     rd2_address    =>    conv_integer(rd_reg2),
130     rd2_data       =>    GPR_rd_data2
131 );
132
133
134 end Behavioral;

```



```

1 --
2 --
3 -- This module is the MIPS ALU for HW3
4 --
5 --
6 --
7 --
8 -----
9 library IEEE;
10 use IEEE.STD_LOGIC_1164.ALL;
11 use IEEE.STD_LOGIC_ARITH.ALL;
12 use IEEE.STD_LOGIC_UNSIGNED.ALL;
13
14 -- *****
15 -- *****
16
17 entity MIPS_ALU is
18 Port (
19 -- ALU operation control inputs
20 ALUOP      : in STD_LOGIC_VECTOR(1 downto 0);-- 00=add, 01=sub, 10=by Function
21 Funct      : in STD_LOGIC_VECTOR(5 downto 0);-- 32=ADD, 34=sub, 36=AND, 37=OR, 38=XOR, 42=SLT
22 -- data inputs & data control inputs
23 A_in       : in STD_LOGIC_VECTOR(31 downto 0);
24 B_in       : in STD_LOGIC_VECTOR(31 downto 0);
25 sext_imm   : in STD_LOGIC_VECTOR(31 downto 0);
26 ALUSrcB    : in STD_LOGIC;
27 -- data output
28 ALU_out     : out STD_LOGIC_VECTOR(31 downto 0)
29 );
30 end MIPS_ALU;
31
32
33 architecture Behavioral of MIPS_ALU is
34
35 -- *****
36 -- *****
37
38 -- inner signals
39 -- =====
40
41 signal ALU_cmd : STD_LOGIC_VECTOR (2 downto 0);-- 000=AND, 001=OR, 010=ADD, 011=XOR, 110=sub, 111=slt, 100,101= not used for now
42 signal ALU_A_in : STD_LOGIC_VECTOR (31 downto 0);
43 signal ALU_B_in : STD_LOGIC_VECTOR (31 downto 0);
44 signal ALU_output : STD_LOGIC_VECTOR (31 downto 0);
45
46 signal sub_rslt : STD_LOGIC_VECTOR (32 downto 0);-- use this for creating the sign of sub in SLT instruction
47 signal sign_of_sub : STD_LOGIC;
48
49 -- Decoded signals for ID phase
50 signal LUI : STD_LOGIC;-- '1' when we decode a LUI instruction
51 signal ORI : STD_LOGIC;-- '1' when we decode an ORI instruction
52 signal JAL : STD_LOGIC;-- '1' when we decode a JAL instruction
53
54
55 begin
56
57 --ORI <= '0';
58
59
60 -- ALU
61 process(ALUOP, Funct, ORI)
62 begin
63     if ALUOP = b"00" then
64         ALU_cmd <= b"010"; -- ADD
65     elsif ALUOP= b"01" then
66         ALU_cmd <= b"110";-- SUB
67     elsif ALUOP = b"11" then -- @@@ Ori HW6
68         ALU_cmd <= b"001";
69
70     else
71         if Funct = b"100000" then
72             ALU_cmd <= b"010"; -- FUNCT=ADD
73         elsif Funct = b"100010" then
74             ALU_cmd <= b"110"; -- FUNCT=SUB
75         elsif Funct = b"100100" then
76             ALU_cmd <= b"000"; -- FUNCT=AND
77         elsif Funct = b"100101" then
78             ALU_cmd <= b"001"; -- FUNCT=OR
79         elsif Funct = b"100110" then
80             ALU_cmd <= b"011"; -- FUNCT=XOR
81         elsif Funct = b"101010" then

```

```

82         ALU_cmd <= b"111"; -- FUNCT=SLT
83     else
84         ALU_cmd <= b"010"; -- ADD
85     end if;
86 end if;
87 end process;
88 --
89
90
91 --- before forwarding
92 process(ALUsrcB, sext_imm, B_in)
93 begin
94     if ALUsrcB='0' then
95         ALU_B_in <= B_in;
96     else
97         ALU_B_in <= sext_imm;
98     end if;
99 end process;
100 ALU_A_in <= A_in;
101
102
103
104 -- if we consider both inputs as 2's comp numbers then
105 sub_rslt <= (ALU_A_in(31) & ALU_A_in) - (ALU_B_in(31) & ALU_B_in);
106 sign_of_sub <= sub_rslt(32);
107
108
109 process(ALU_A_in, ALU_B_in, ALU_cmd, sign_of_sub)
110     begin
111         case ALU_cmd is
112             when b"000" => ALU_output <= ALU_A_in and ALU_B_in;-- AND
113             when b"001" => ALU_output <= ALU_A_in or ALU_B_in; -- OR
114             when b"010" => ALU_output <= ALU_A_in + ALU_B_in; -- ADD
115             when b"011" => ALU_output <= ALU_A_in xor ALU_B_in; -- XOR
116             when b"100" => ALU_output <= not(ALU_A_in and ALU_B_in); -- NAND
117             when b"101" => ALU_output <= not(ALU_A_in or ALU_B_in); -- NOR
118             when b"110" => ALU_output <= ALU_A_in - ALU_B_in; -- SUB
119             when others => ALU_output <= x"0000000" & b"000" & sign_of_sub;-- SLT
120         end case;
121     end process;
122
123
124 ALU_out <= ALU_output;
125
126
127 end Behavioral;
128
129 -- *****
130 -- *****

```

```

1  --
2  -- dual_port_memory no CK for read for HW3
3  --
4  -- Created:
5  --         by - Danny Seidner, 31/8/2013
6  --
7  --
8
9  LIBRARY ieee;
10 USE ieee.std_logic_1164.all;
11 USE ieee.std_logic_arith.all;
12
13 ENTITY dual_port_memory_no_CK_read IS
14   GENERIC(
15     width : integer :=32;
16     depth : integer :=32
17   );
18   PORT (
19     wr_address   : in integer range depth-1 downto 0;
20     wr_data      : in std_logic_vector(width-1 downto 0);
21     wr_clk       : in std_logic;
22     wr_en        : in std_logic;
23     rd1_address  : in integer range depth-1 downto 0;
24     rd1_data     : out std_logic_vector(width-1 downto 0);
25     rd2_address  : in integer range depth-1 downto 0;
26     rd2_data     : out std_logic_vector(width-1 downto 0)
27   );
28 END ENTITY dual_port_memory_no_CK_read;
29
30 --
31 ARCHITECTURE dual_port_memory OF dual_port_memory_no_CK_read IS
32   type Memory_Type is array ((depth-1) downto 0) of std_logic_vector((width-1) downto 0);
33   shared variable Memory_array : Memory_Type := (others => (others => '0')); -- reset initial value to be 0
34
35
36 BEGIN
37
38
39   Memory_wrdata: PROCESS (wr_clk)
40   begin
41     if wr_clk'event and wr_clk = '1' then
42       if wr_en = '1' then
43         Memory_array(wr_address) := wr_data;
44       end if;
45     end if ;
46   end process Memory_wrdata;
47
48
49   Memory_rddata1 : PROCESS (rd1_address,wr_clk) -- need to add wr_clk, otherwise
50   -- if we leave rd1_address constant,
51   -- we won't see changes in rd data even
52   -- we write new data (in simulation)
53   begin
54     rd1_data <= Memory_array(rd1_address);
55   end process Memory_rddata1;
56
57
58
59   Memory_rddata2 : PROCESS (rd2_address,wr_clk) -- need to add wr_clk, see Memory_rddata1 above
60   begin
61     rd2_data <= Memory_array(rd2_address);
62   end process Memory_rddata2;
63
64
65
66 END ARCHITECTURE dual_port_memory;
67
68

```