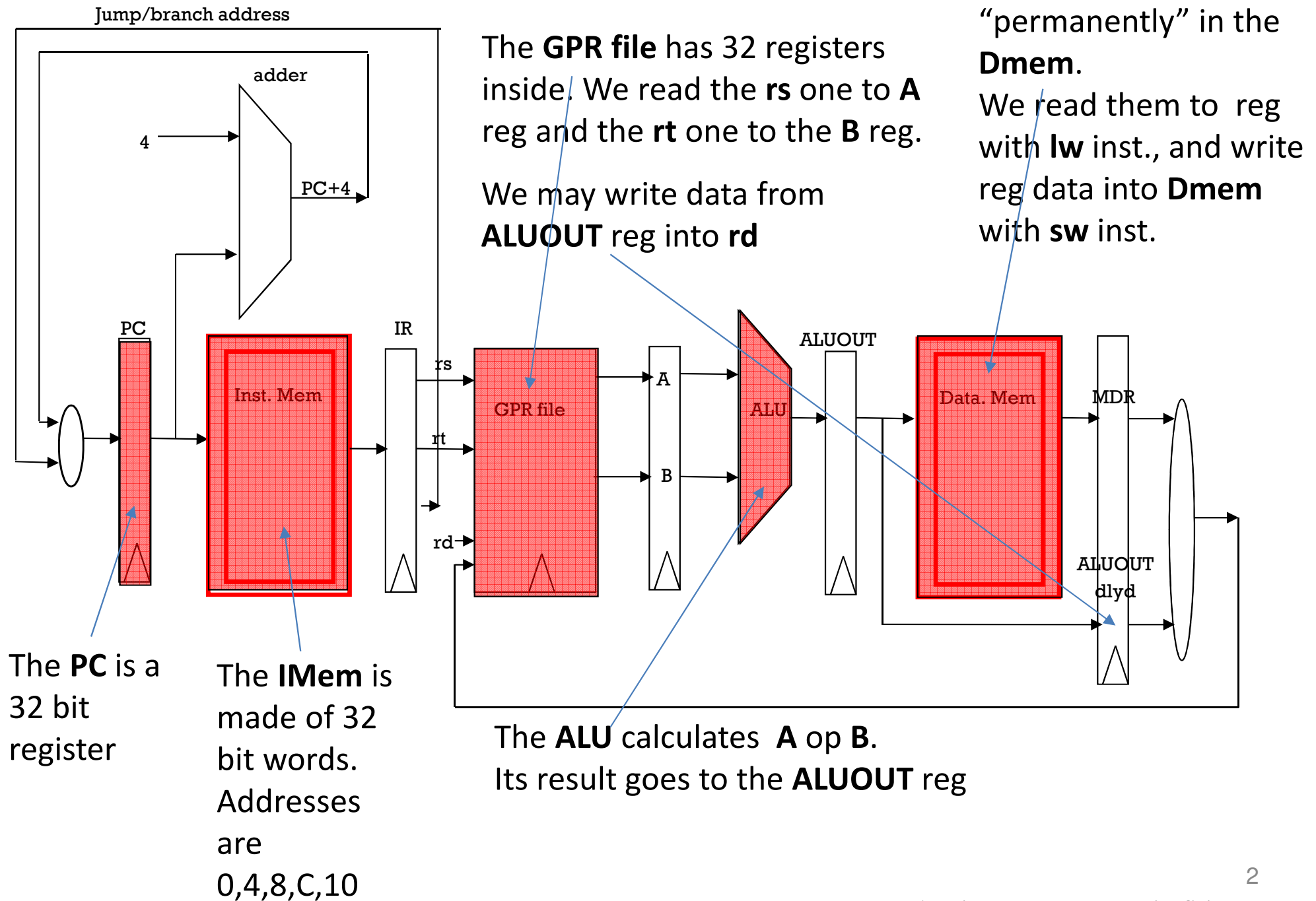


Pipelined MIPS

The pipelined MIPS



MIPS instruction set


R-type

add Rd, Rs, Rt # Rd=Rs+Rt
 sub Rd, Rs, Rt # Rd=Rs-Rt
 and Rd, Rs, Rt # Rd=Rs AND Rt
 or Rd, Rs, Rt # Rd=Rs OR Rt
 xor Rd, Rs, Rt # Rd=Rs XOR Rt
 slt Rd, Rs, Rt # if Rs<Rt Rd=1 else Rd=0
 jr Rs # PC=Rs (note that Rd=0)



I-type

 addi Rt, Rs, imm # Rt=Rs+ sext(imm)
 lw Rt, imm(Rs) # Rt=M[Rs + sext(imm)]
 sw Rt, imm(Rs) # M[Rs + sext(imm)]=Rt
 beq Rs, Rt, label # if Rs==Rt, PC=PC+4+ sext(imm)*4
 # else PC=PC+4
 bne Rs, Rt, label # same as beq with cond of Rs≠Rt
 ori Rt, Rs, imm # Rt=Rs OR imm (no sext)
 lui Rt, imm # Rt= imm<<16 (no sext)



j-type

j imm # PC= imm*4 (no sext)
 jal imm # PC= imm*4, \$31=PC+4 (no sext)



MIPS instructions

R-type instructions: add, sub, slt ,and, or, xor (& jr)

```
sub  rd, rs, rt      # rd = rs - rt
```

means subtract the contents of **rt** from the contents of **rs** and store the result into **rd**

The R-type instructions we use are:

add rd, rs, rt # $rd = rs + rt$

sub rd, rs, rt **# rd = rs – rt**

and rd, rs, rt # rd = rs AND rt

or rd, rs, rt # rd = rs OR rt


xor rd, rs, rt # rd = rs XOR rt

slt rd, rs, rt **# rd =1 if rs < rt, 0 otherwise** **[=set less than]**

The last R-type instruction is:

jr rs **# PC = rs**

 The R-type instruction binary representation is:



MIPS instructions

I-type instructions: addi, ori, beq, bne , lui, lw, sw

addi rt, rs, imm # rt = rs + sext(imm) [imm is 16 bit 2's comp]

means add imm to the contents of **rs** and put the result in **rt**

ori rt, rs, imm # rt = rs OR imm [imm is 16 bits –no sext]

means OR imm with the contents of **rs** and put the result in **rt** (16 MSBs will not change)

```
lui rt, imm           # rt = imm << 16           [imm is 16 bits –no sext]
```

means shift imm left by 16 and put the result in **rt** (16 LSBs will be '0'-s)

beq rt, rs, imm # if rs == rt PC = PC + 4 + 4*sext(imm) [imm is 16 bit 2's comp]

```
# else      PC = PC +4
```

means if the contents of **rs** equals the contents of **rt**, jump imm+1 instructions forward

bne - same, but checks if not equal

lw rt, (imm) rs **# rt = M[rs + sext(imm)]** **[imm is 16 bit 2's comp]**

Calc. address by adding imm to the contents of **rs**, read from the D.Mem and copy into **rt**

sw rt, (imm) rs # M[rs + sext(imm)]= rt [imm is 16 bit 2's comp]

Calc. address by adding imm to the contents of **rs**, write **rt** into that address in the D.Mem

The I-type instruction binary representation is:

6	5	5	16
OPCODE	Rs	Rt	imm

MIPS instructions

J-type instructions: j, jal

j imm26 # PC = PC[31:28] || 4*imm26 [imm26 = 26 bits]

means jump to the word specified by the 26 bit imm in the instruction

```
jal imm26 # PC = PC[31:28] || 4*imm26 [imm26 = 26 bits]
# $31= PC+4
```


means jump to the word specified by the 26 bit imm in the instruction, and also keep the address of the next instructions in register \$31

The J-type instruction binary representation is:




Rtype instructions

Performing Rtype inst.

 

Performing Rtype inst.

 


IF – Inst. Fetch

$IR = Imem[PC]$

$PC = PC+4$

Performing Rtype inst.

 


ID – Inst. Decode

A = rs , B = rt

(& decode
control signals)


Performing Rtype inst.

 

EX– Execute

ALUOUT = A op B


Performing Rtype inst.

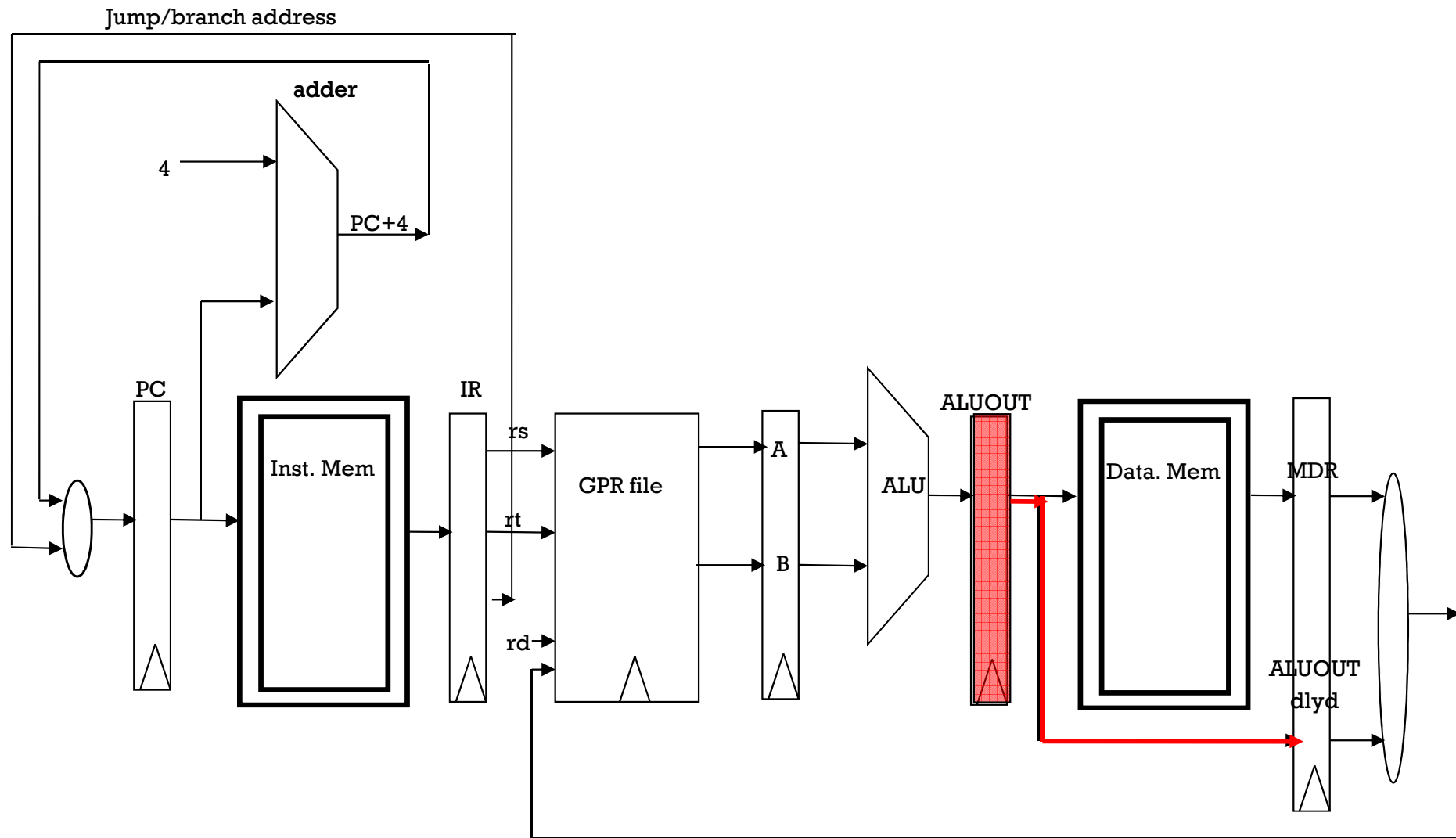

MEM – Memory

In Rtype – wait 1 ck

Performing Rtype inst.

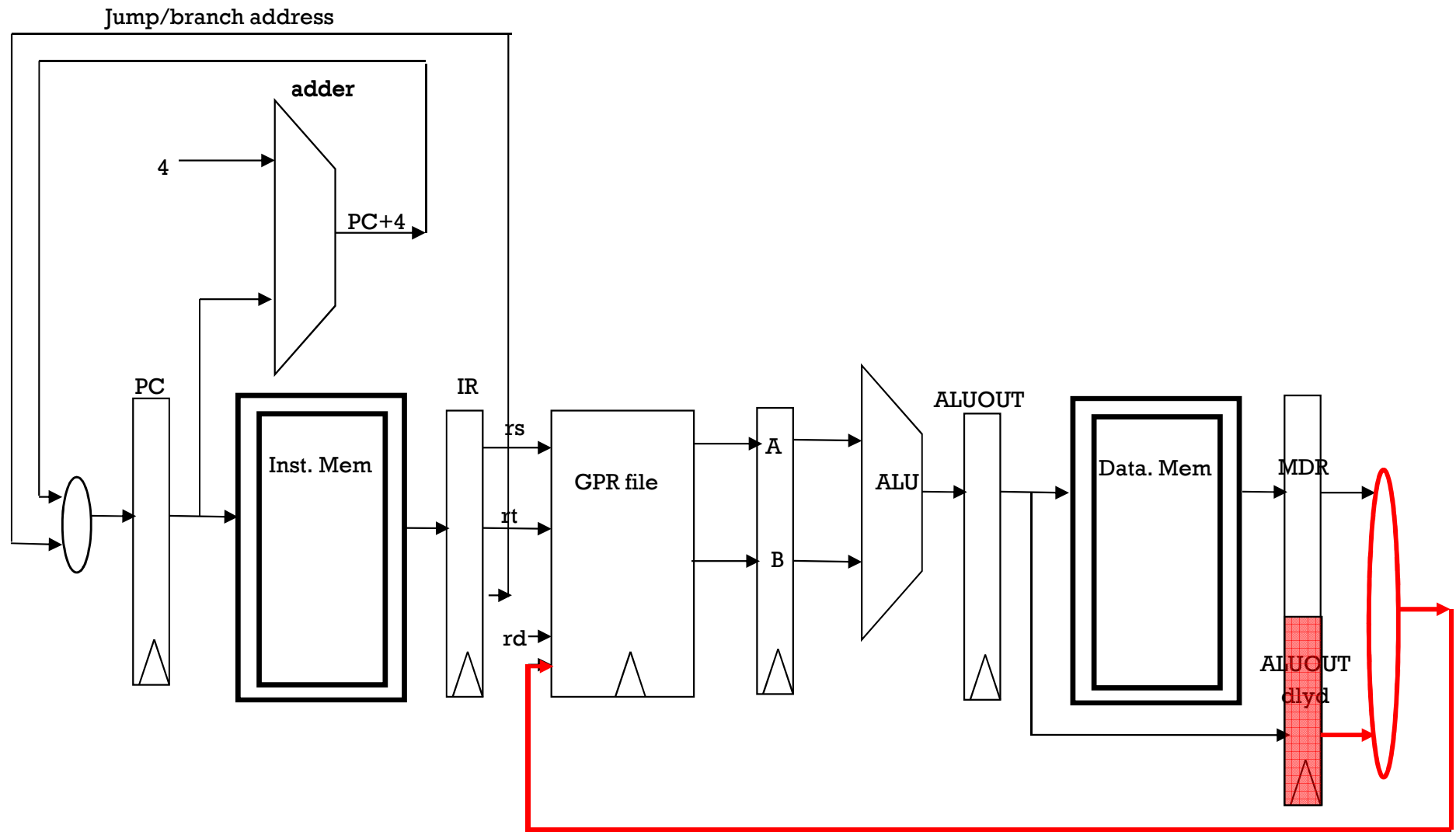


WB – write back


Rd = ALUOUT

lw instruction

Performing lw inst.

 

Performing lw inst.

 


IF – Inst. Fetch

$IR = Imem[PC]$

$PC = PC+4$

Performing lw inst.

 


ID – Inst. Decode

A = rs , B = rt

(& decode
control signals)


Performing lw inst.

 

EX– Execute

$$ALUOUT = A + sext(imm)$$

Performing lw inst.

 


MEM – Memory

In lw:

$\text{MDR} = \text{M}[\text{ALUOUT}]$

Performing lw inst.

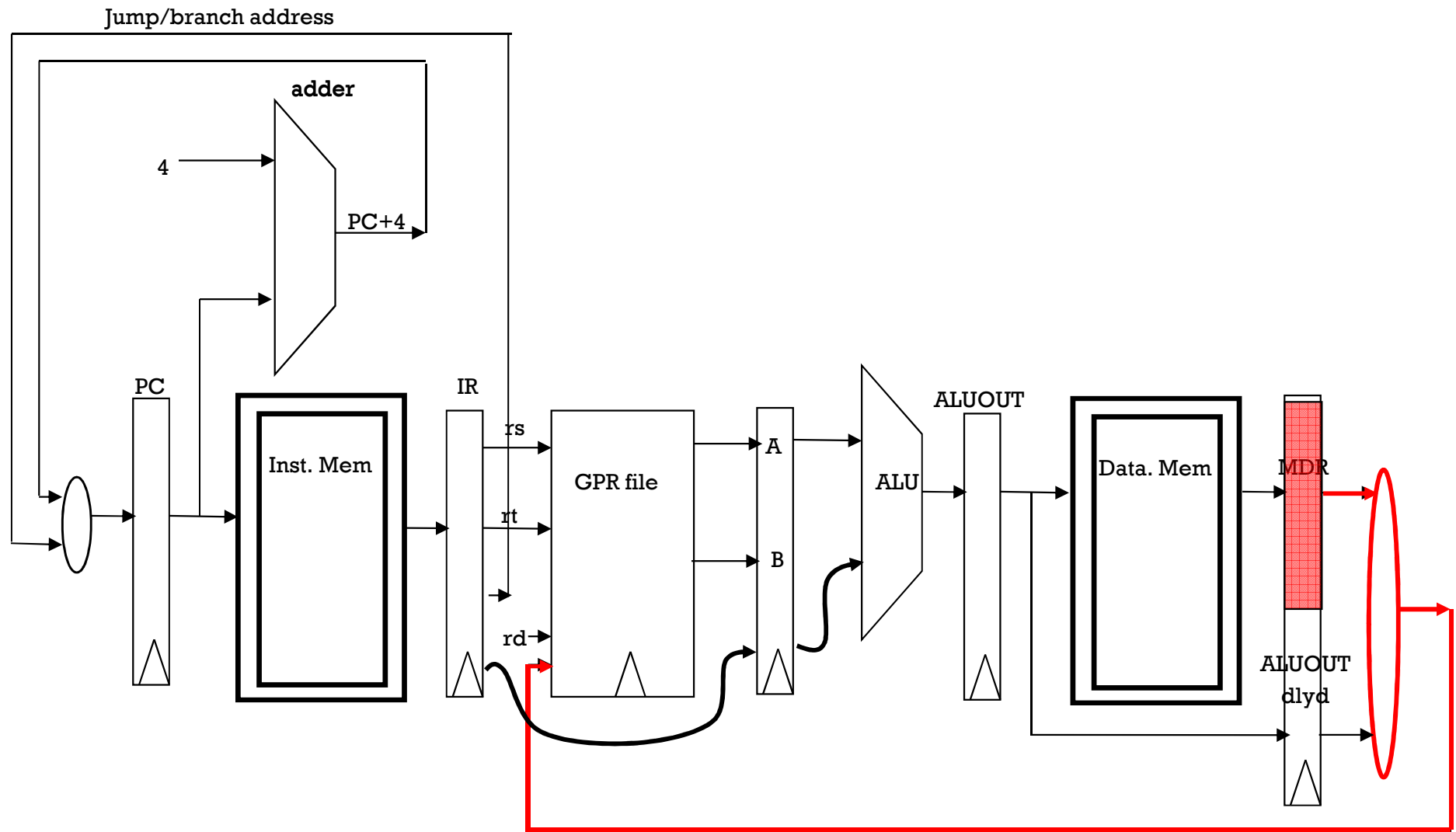


WB – write back


Rt = MDR

sw instruction

Performing sw inst.

 

Performing sw inst.

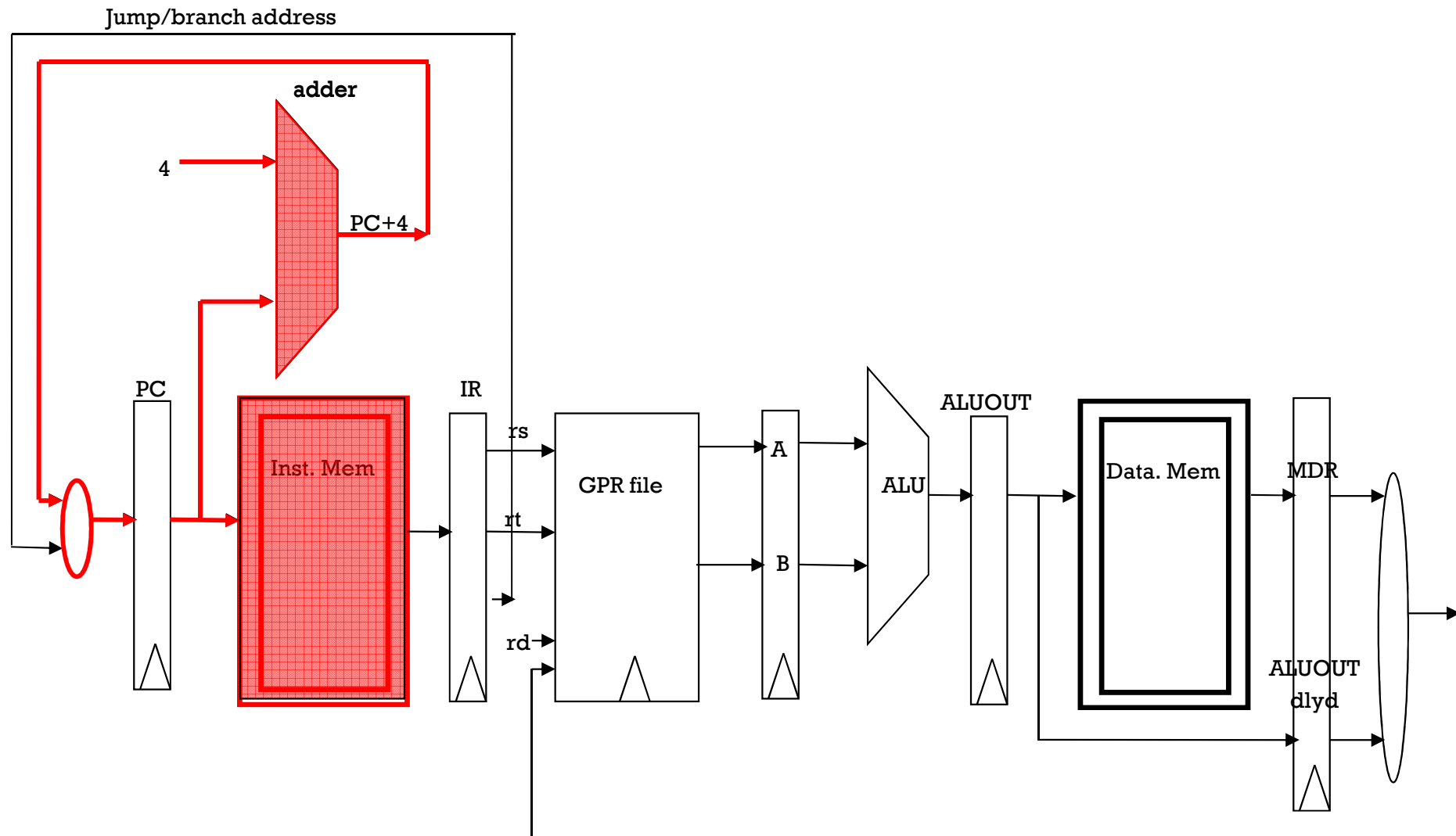


IF – Inst. Fetch

$IR = Imem[PC]$

$PC = PC+4$

Performing sw inst.

 


ID – Inst. Decode

A = rs , B = rt

(& decode
control signals)


Performing sw inst.

 

EX– Execute

$$\text{ALUOUT} = A + \text{sext}(\text{imm})$$

Performing sw inst.

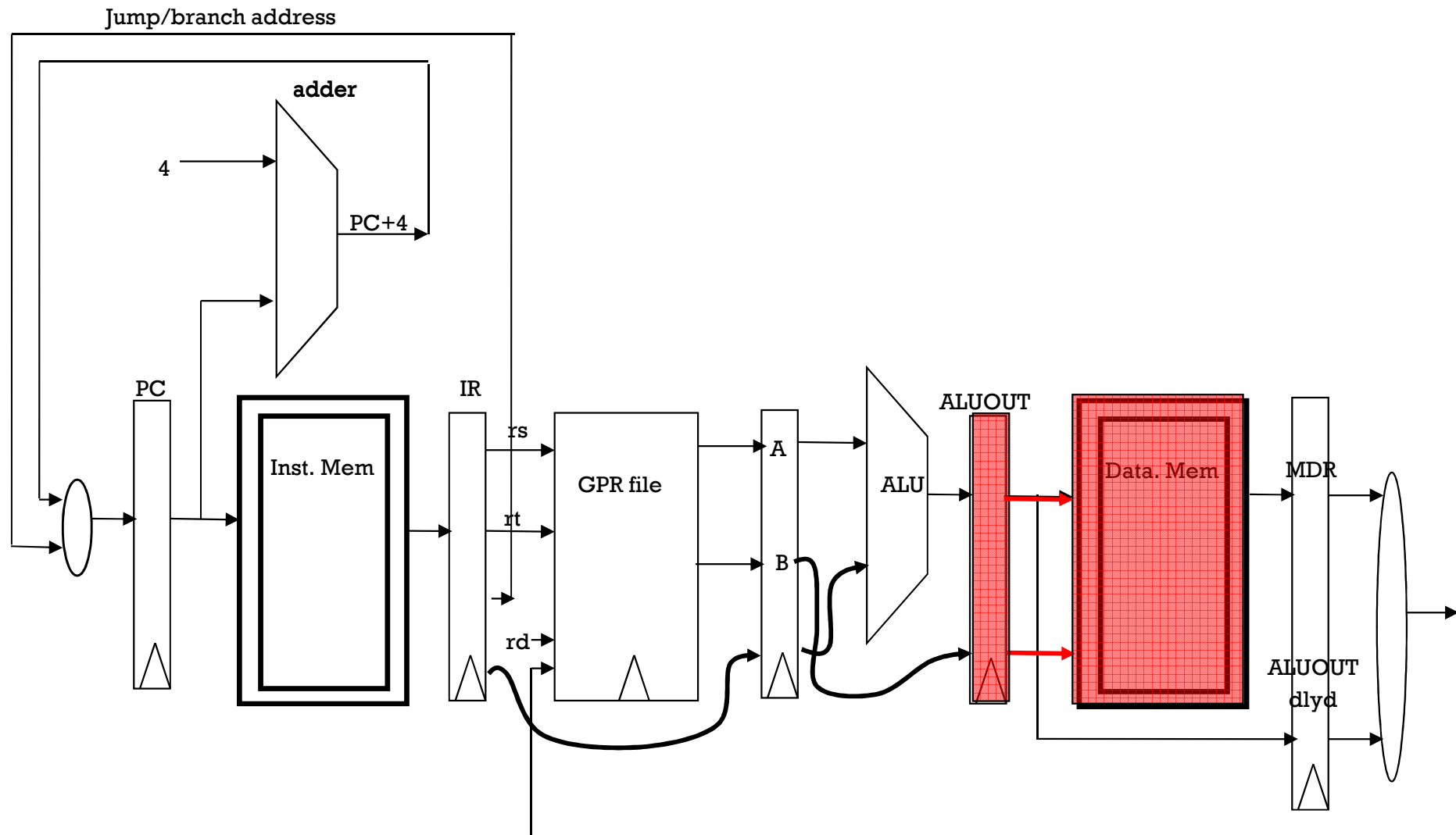


MEM – Memory

In sw:

$M[ALUOUT] = B \text{ dlyd}$

Performing lw inst.

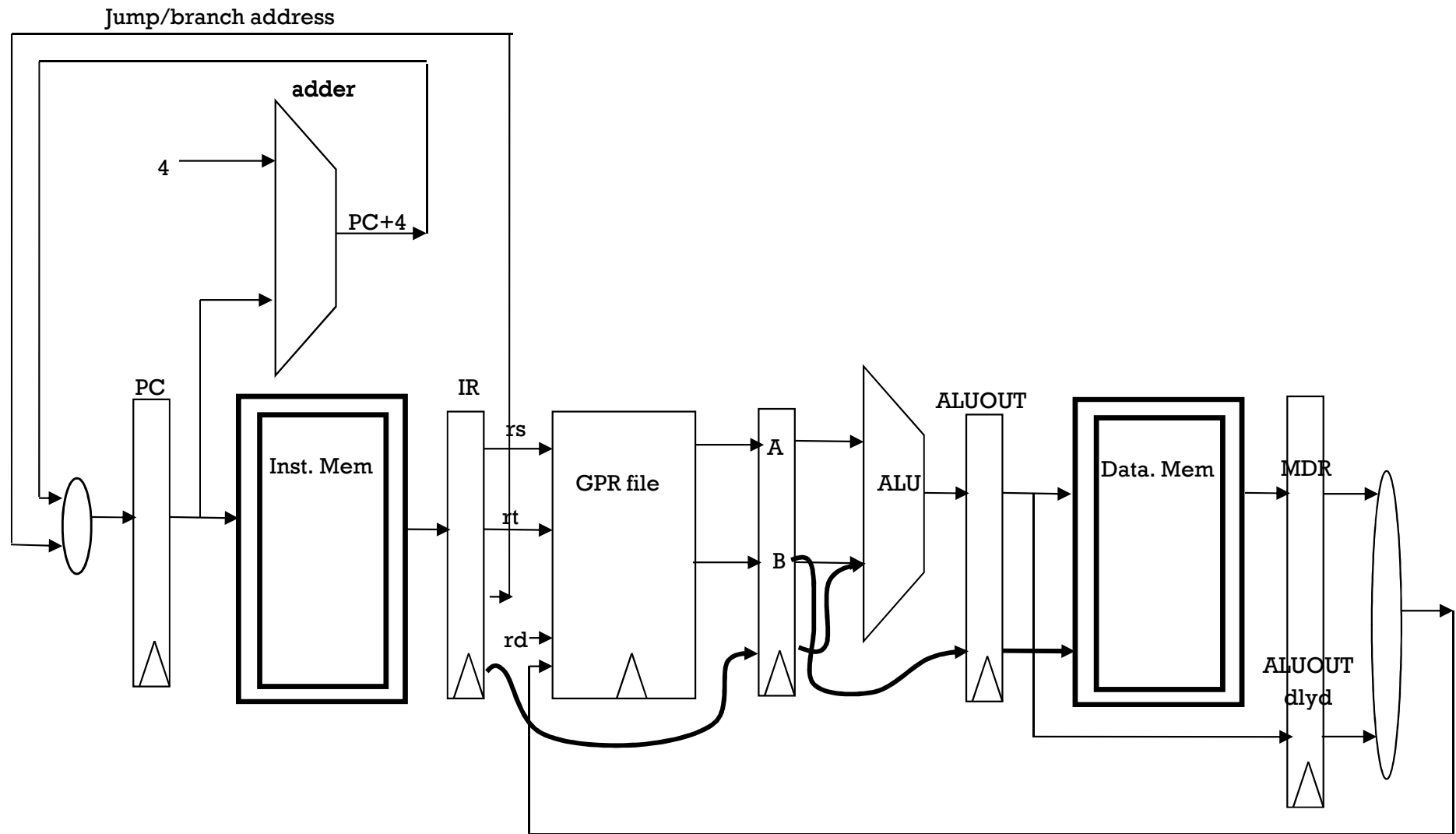


WB – write back


Do nothing

j or beq instructions

Performing jump or branch inst.

 

Performing jump or branch inst.

 


IF – Inst. Fetch

$IR = Imem[PC]$

$PC = PC+4$

Performing jump or branch inst.

 


ID – Inst. Decode

In jump:

PC = jump adrs

Performing jump or branch inst.

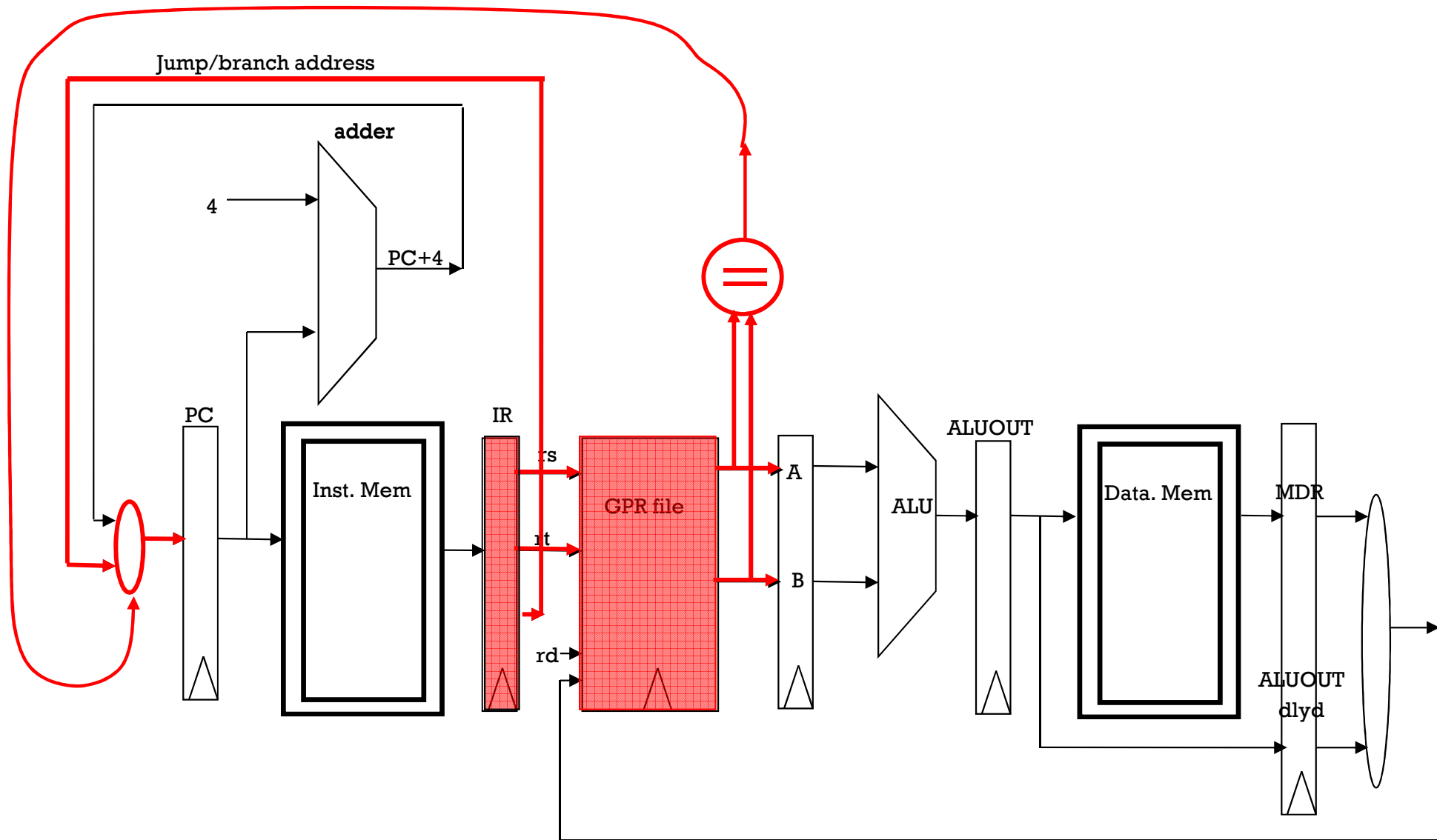

ID – Inst. Decode


In jump:

PC = branch adrs


if $rs == rt$

Pipelined operation

Performing Rtype inst.

 

Performing Rtype inst.

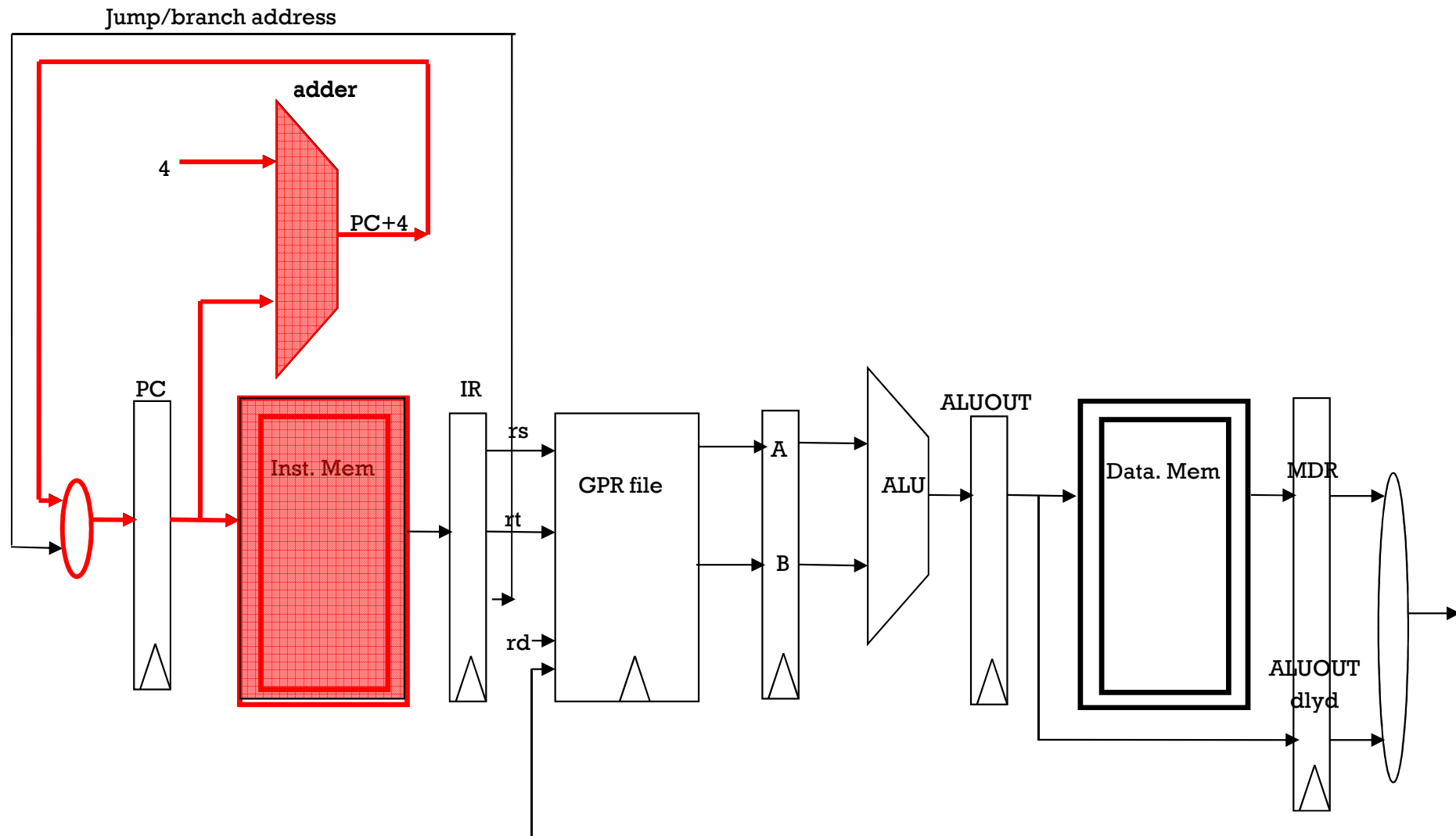


IF – Inst. Fetch

$IR = Imem[PC]$

$PC = PC+4$

Performing Rtype inst.

 

IF – Inst. Fetch


**IR = Imem[PC]
PC = PC+4**

ID – Inst. Decode

A = rs , B = rt

(& decode
control signals)

Performing Rtype inst.

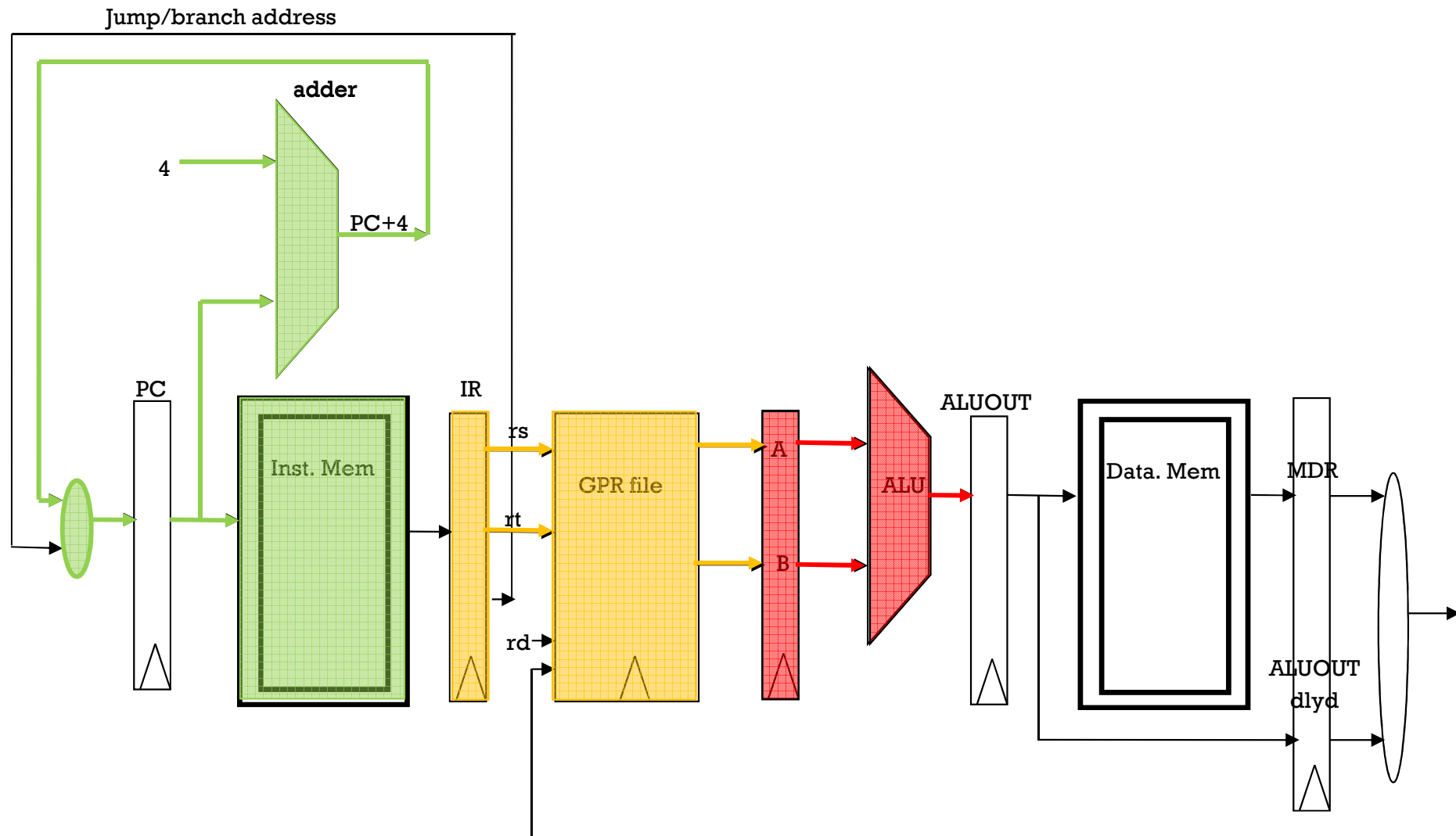

IF – Inst. Fetch

**IR = Imem[PC]
PC = PC+4**


ID – Inst. Dec.
A = rs , B = rt

(& decode
control signals)

EX– Execute

ALUOUT = A op B

Performing Rtype inst.

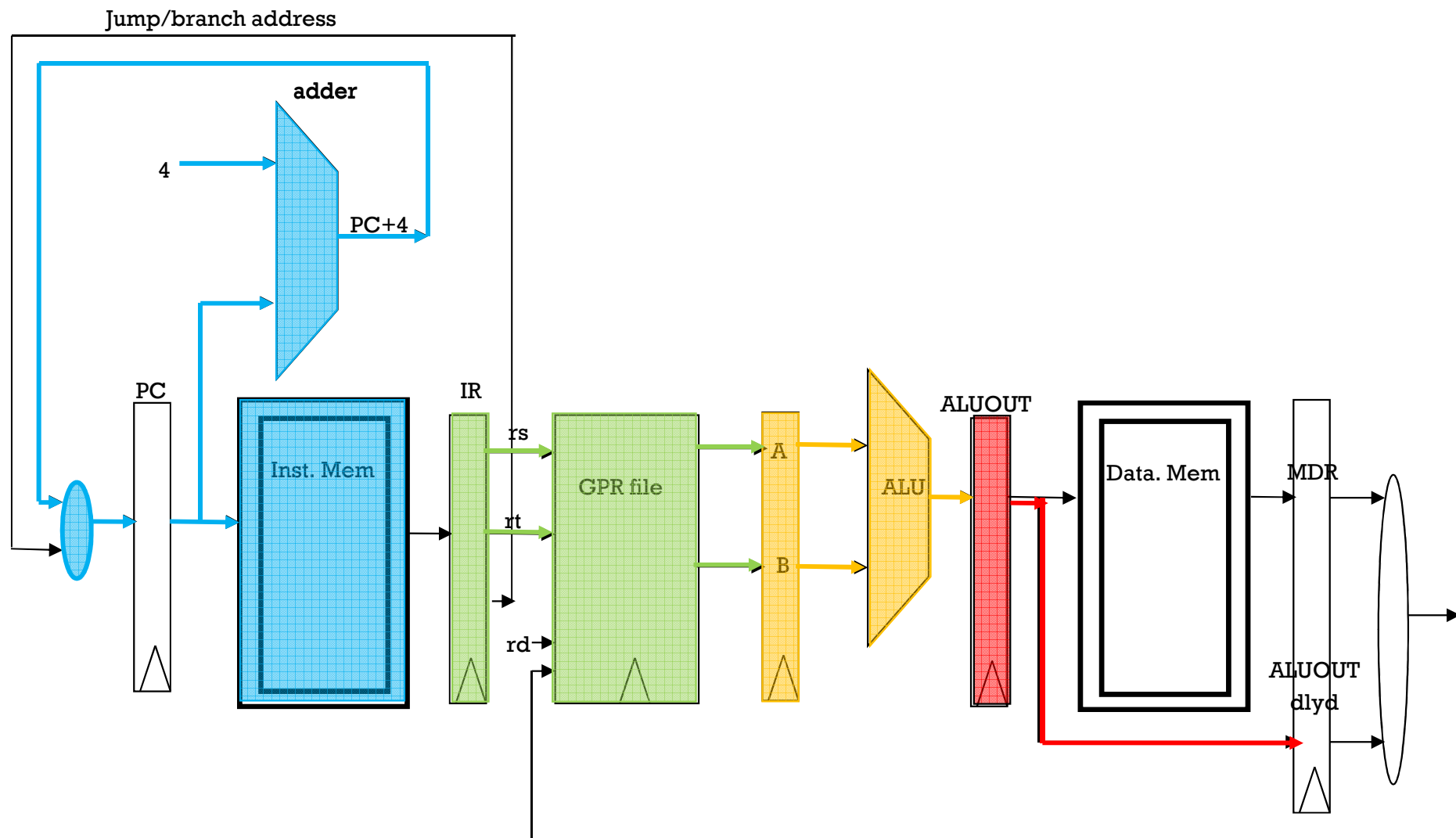

IF – Inst. Fetch

**IR = Imem[PC]
PC = PC+4**

ID – Inst. Dec.

A = rs , B = rt

(& decode
control signals)


EX– Execute

ALUOUT = A op B

MEM

**In Rtype –
wait 1 ck**

Performing Rtype inst.

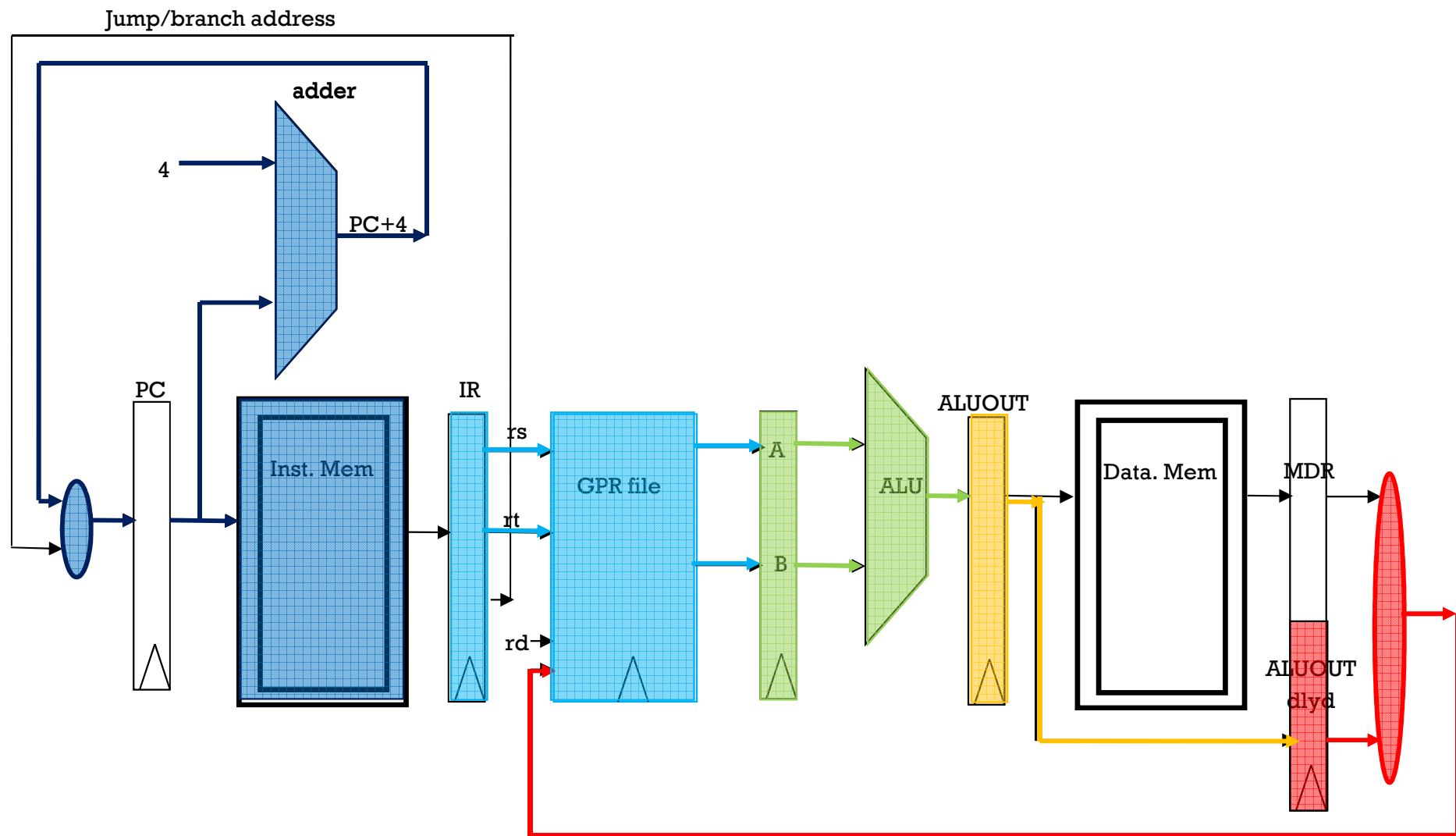

IF – Inst. Fetch

**IR = Imem[PC]
PC = PC+4**

ID – Inst. Dec.

A = rs , B = rt

(& decode
control signals)

EX– Execute

ALUOUT = A op B


MEM

**In Rtype –
wait 1 ck**

WB – write back


Rd = ALUOUT

Performing Rtype inst.

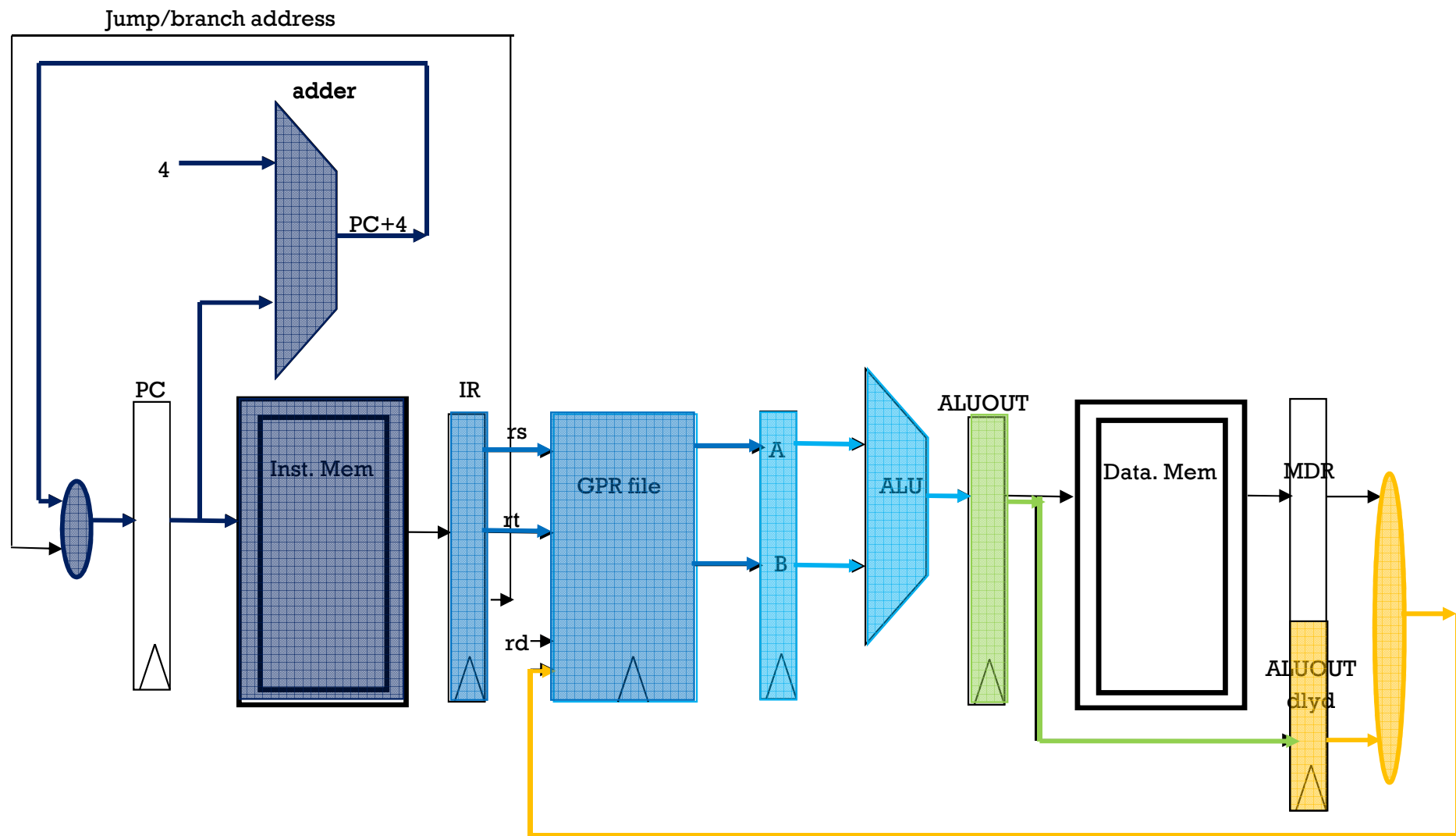

IF – Inst. Fetch	ID – Inst. Dec. A = rs , B = rt (& decode control signals)	EX– Execute ALUOUT = A op B	MEM In Rtype – wait 1 ck	WB – write back Rd = ALUOUT
IR = Imem[PC] PC = PC+4				

Performing Rtype inst.

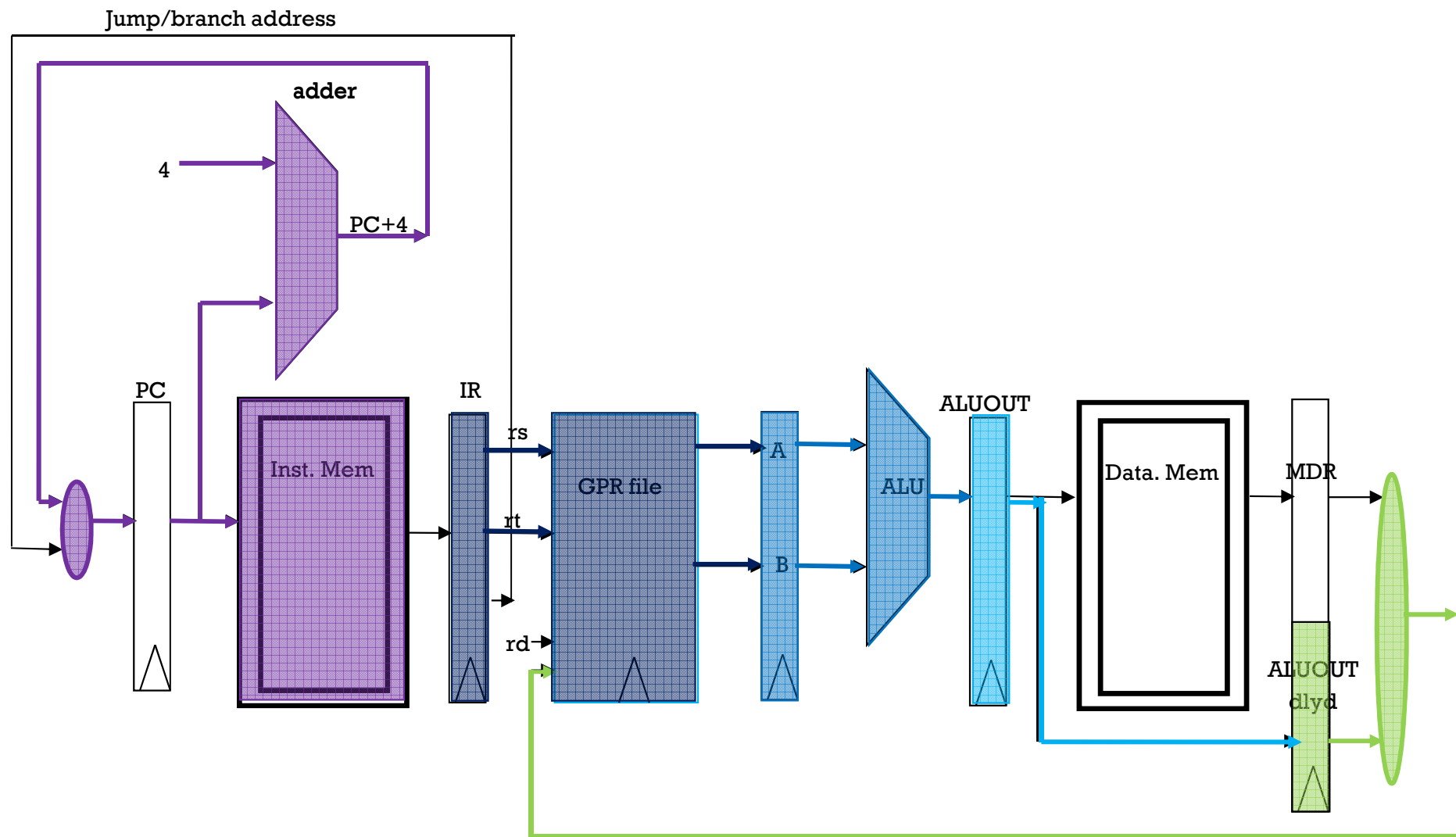

IF – Inst. Fetch

**IR = Imem[PC]
PC = PC+4**

ID – Inst. Dec.

A = rs , B = rt
(& decode control signals)

EX– Execute

ALUOUT = A op B


MEM

**In Rtype –
wait 1 ck**

WB – write back

Rd = ALUOUT

Performing Rtype inst.

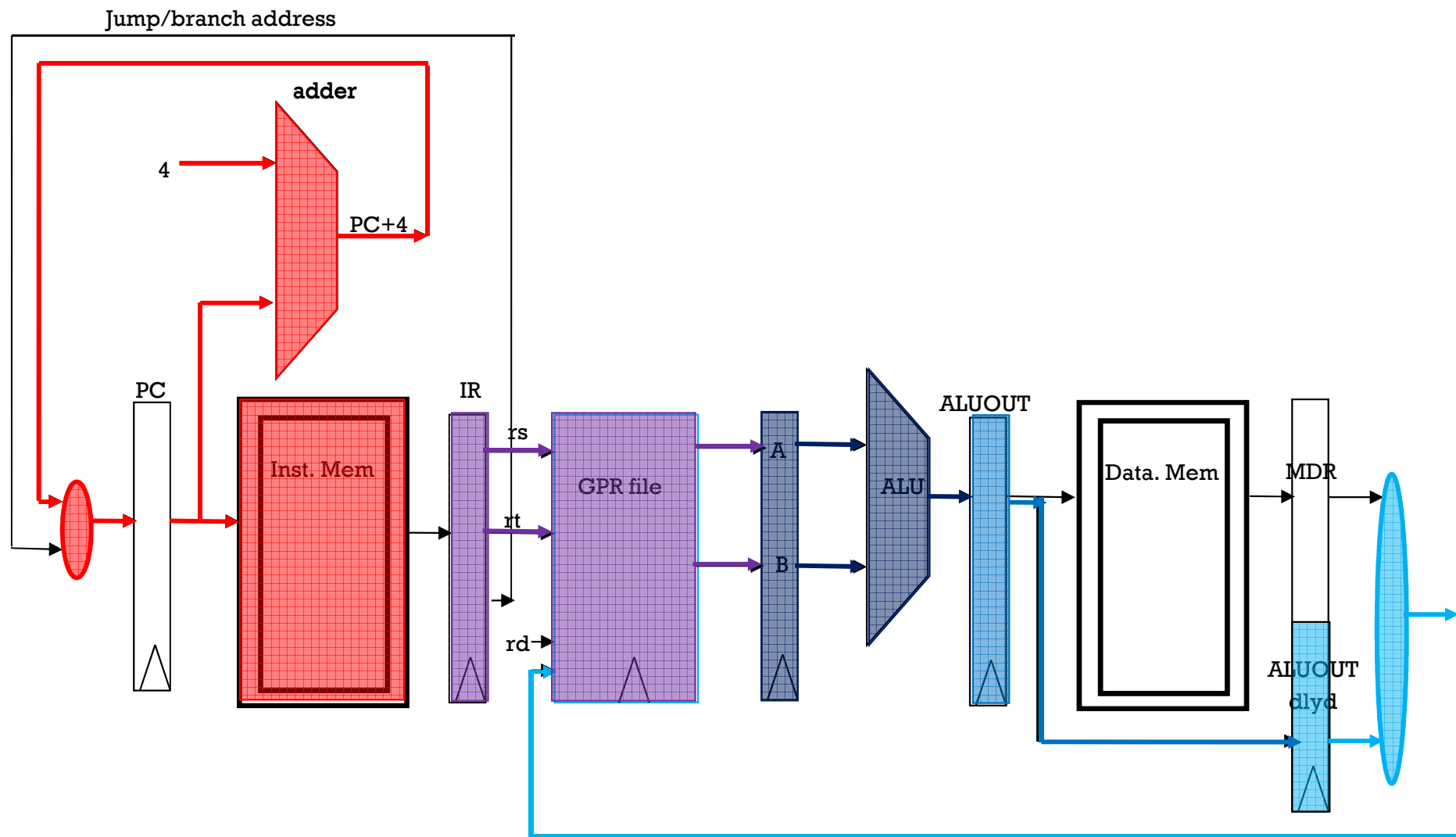

IF – Inst. Fetch

IR = Imem[PC]

PC = PC+4

ID – Inst. Dec.

A = rs , B = rt

(& decode control signals)

EX– Execute

ALUOUT = A op B

MEM


In Rtype – wait 1 ck

WB – write back

Rd = ALUOUT

42

Performing Rtype inst.

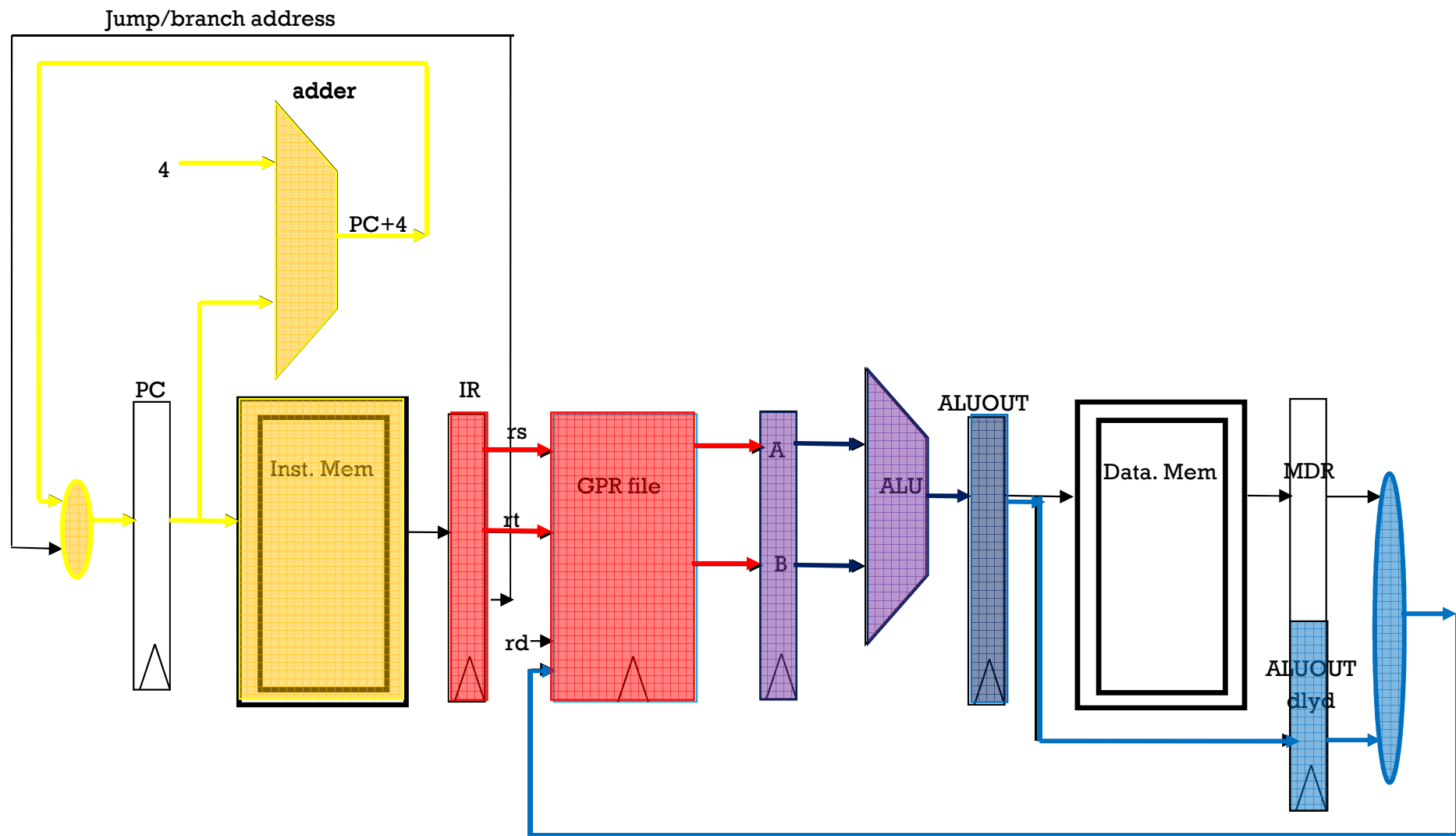

IF – Inst. Fetch

**IR = Imem[PC]
PC = PC+4**


ID – Inst. Dec.
A = rs , B = rt
(& decode control signals)

EX– Execute
ALUOUT = A op B

MEM
In Rtype – wait 1 ck

WB – write back
Rd = ALUOUT

Performing Rtype inst.

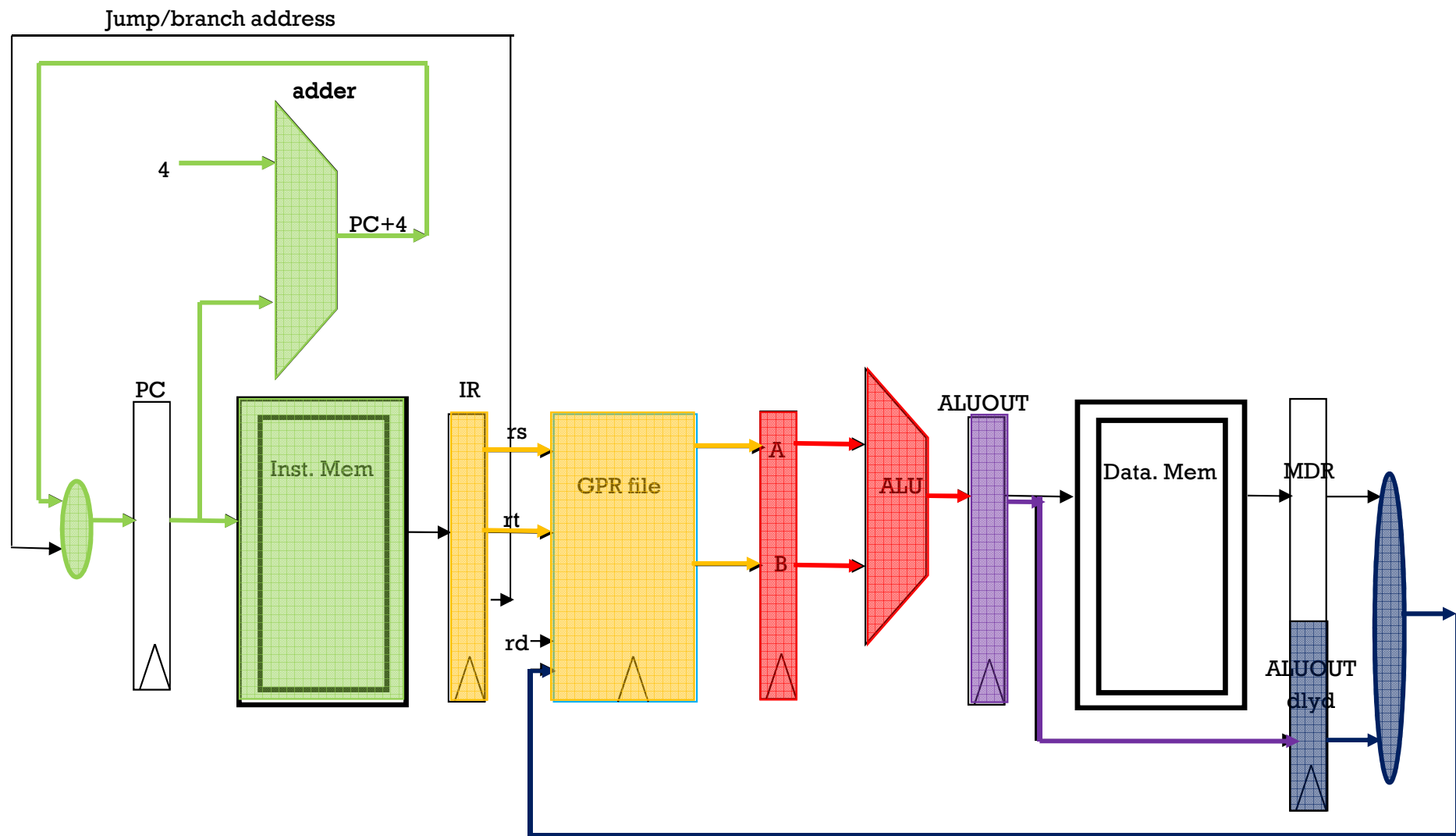

IF – Inst. Fetch

**IR = Imem[PC]
PC = PC+4**

ID – Inst. Dec.
A = rs , B = rt

(& decode
control signals)

EX– Execute

ALUOUT = A op B


MEM

**In Rtype –
wait 1 ck**

WB – write back

Rd = ALUOUT

Performing Rtype inst.

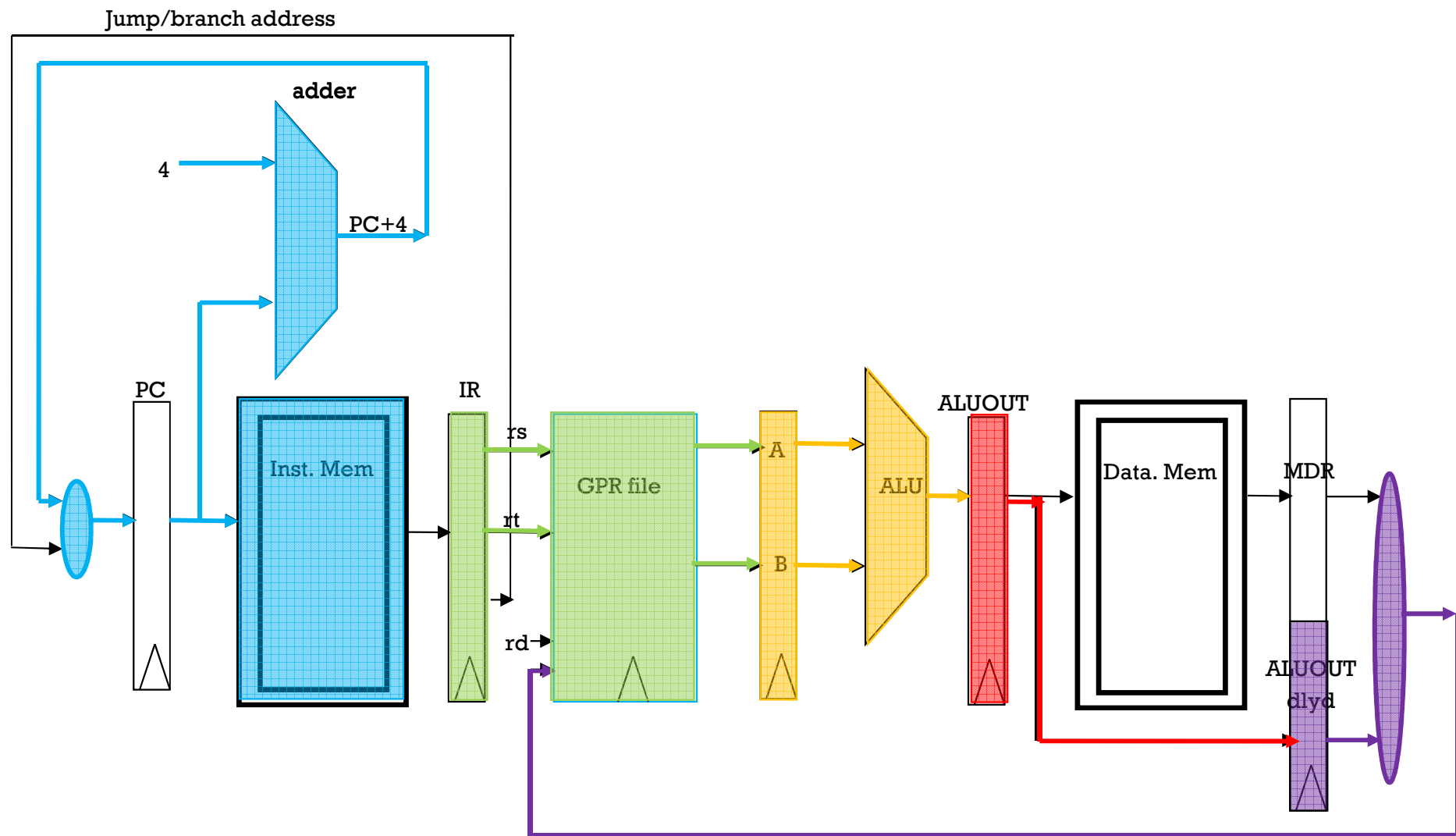

IF – Inst. Fetch

**IR = Imem[PC]
PC = PC+4**

ID – Inst. Dec.
A = rs , B = rt

(& decode
control signals)

EX– Execute

ALUOUT = A op B

MEM


**In Rtype –
wait 1 ck**

WB – write back

Rd = ALUOUT

45

Performing Rtype inst.

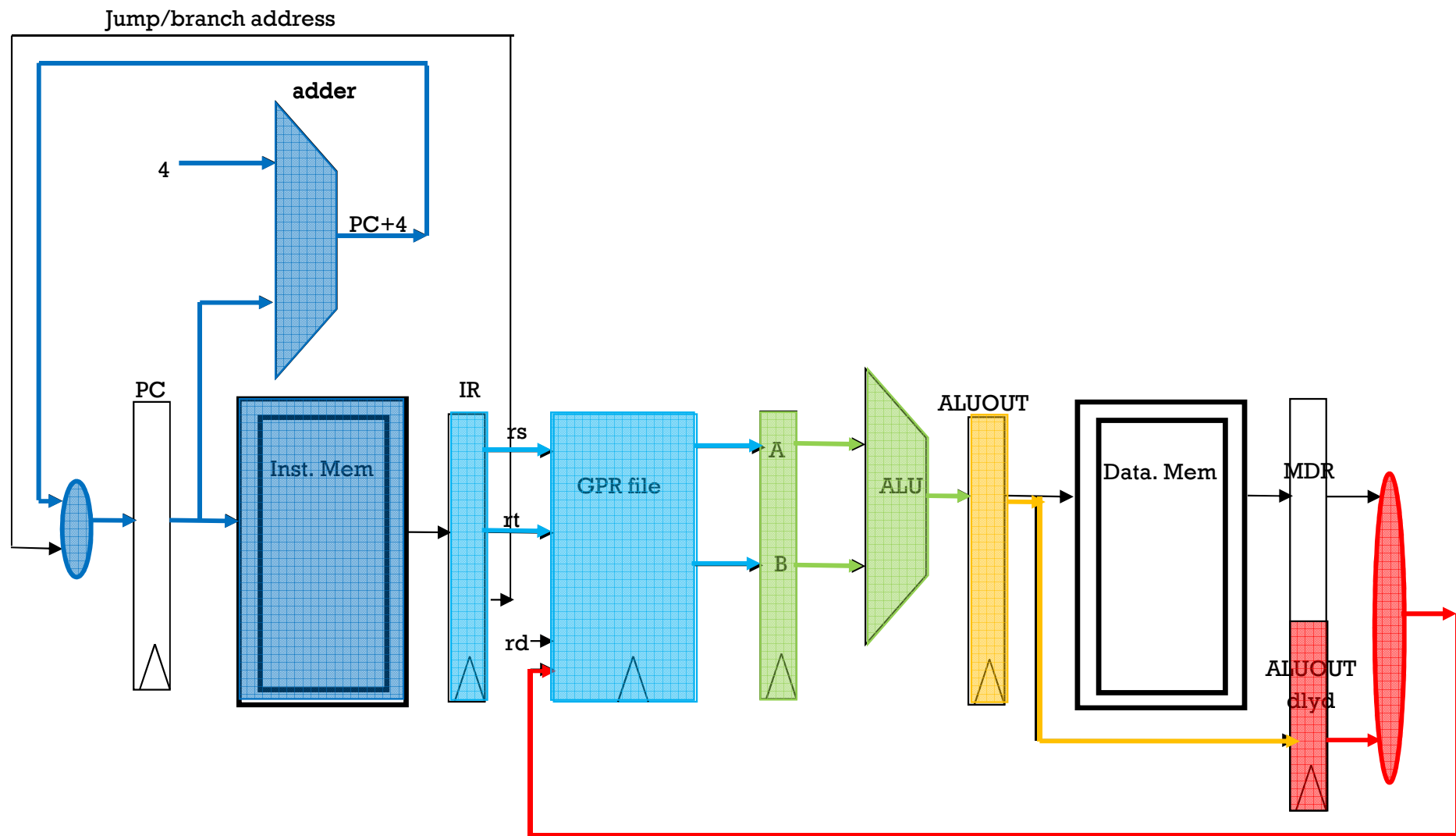

IF – Inst. Fetch

**IR = Imem[PC]
PC = PC+4**

ID – Inst. Dec.

A = rs , B = rt

(& decode
control signals)

EX– Execute

ALUOUT = A op B


MEM

**In Rtype –
wait 1 ck**


WB – write back

Rd = ALUOUT


Pipelining timing representation

 


Pipelining timing representation

 

 
If we rotate that, we
see the same
picture we saw in
the previous slides.



 
If we rotate that, we
see the same
picture we saw in
the previous slides.



 
If we rotate that, we
see the same
picture we saw in
the previous slides.



 
If we rotate that, we see the same picture we saw in the previous slides.



 
If we rotate that, we see the same picture we saw in the previous slides.



 
If we rotate that, we see the same picture we saw in the previous slides.



 
If we rotate that, we see the same picture we saw in the previous slides.



 If we rotate that, we see the same picture we saw in the previous slides.



 
If we rotate that, we see the same picture we saw in the previous slides.




The diagram illustrates the execution of five instructions (I1 to I5) through the stages of a 5-stage pipeline (IF, ID, EX, DM, WB). The instructions are represented by colored bars: I1 (red), I2 (yellow), I3 (green), I4 (blue), and I5 (purple). The diagram shows the progression of each instruction through the stages, with a final empty bar at the bottom.

Instruction	IF	ID	EX	DM	WB
I1					
I2					
I3					
I4					
I5					

 If we rotate that, we see the same picture we saw in the previous slides.




Pipelining timing representation

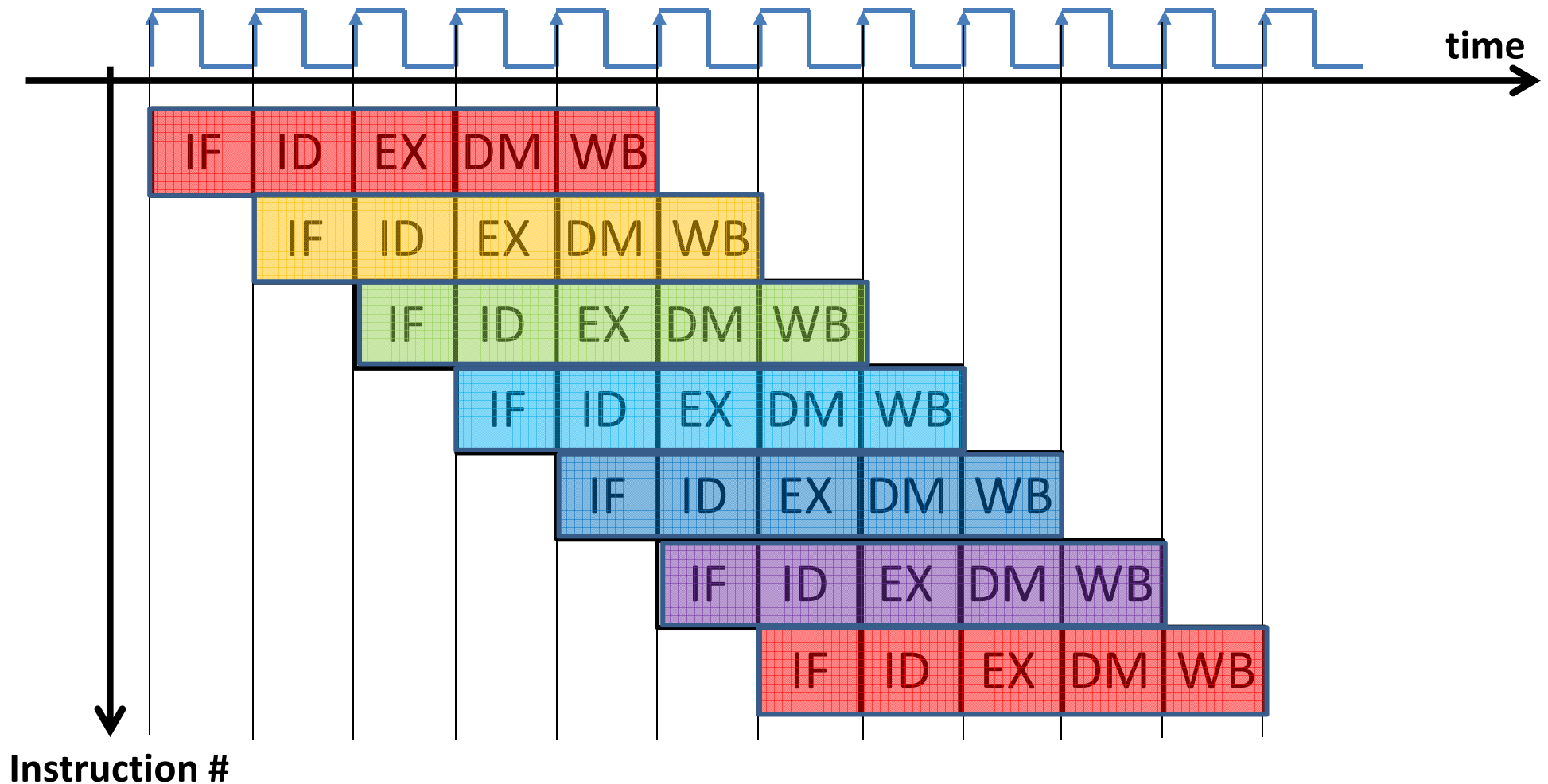

From now and on, we will use this scheme to describe what happens in the CPU.

HW2 – the Fetch Unit

The Fetch Unit

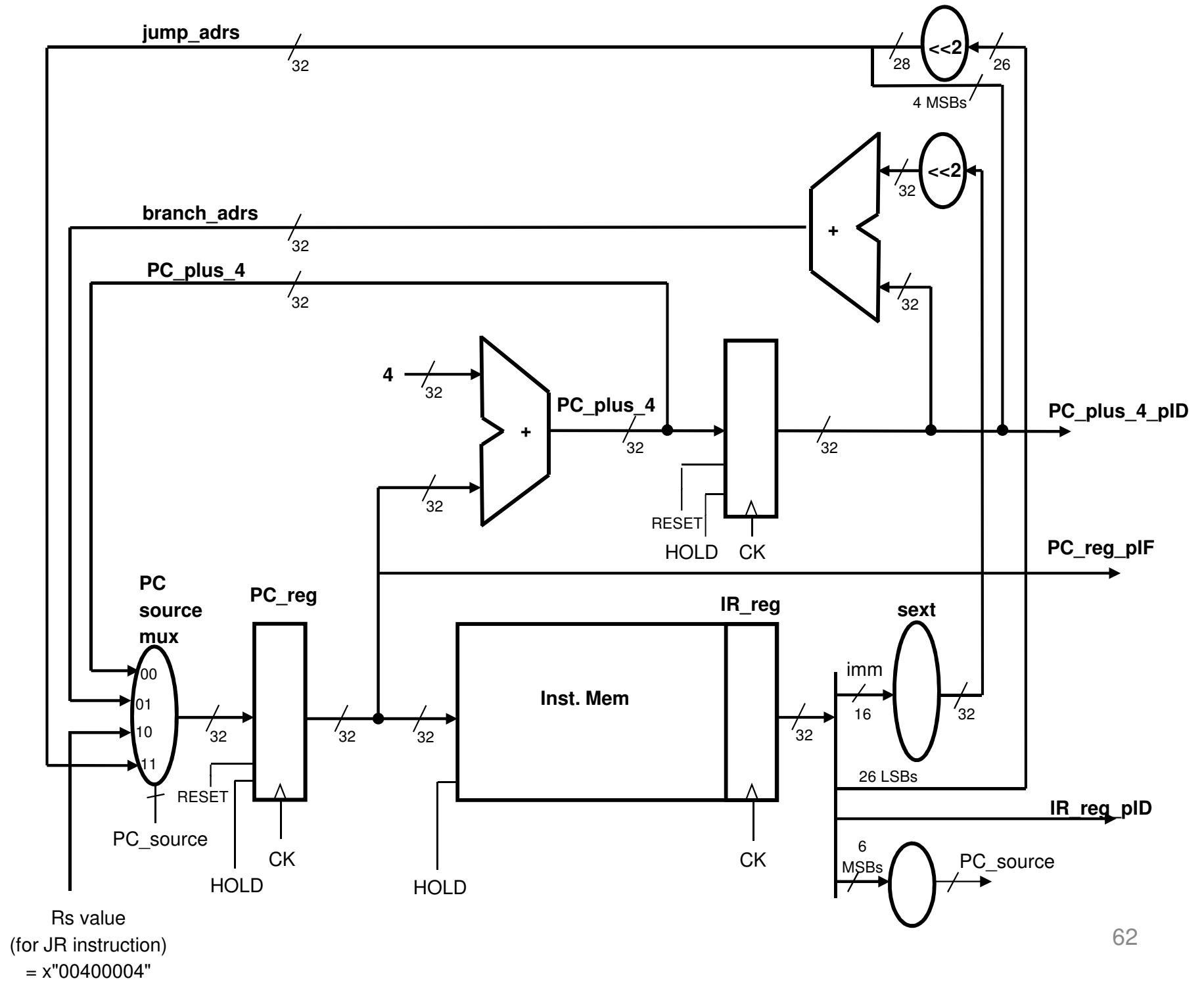


Names & definition of signals inside the Fetch Unit:

You must use these exact signal names in your design.

- **PC_reg** – a 32 bit register. **Reset** should force PC_reg= 0x400000
- **PC_plus_4** – a 32 bit signal that has the PC_reg value + 4.
- **PC_plus_4_pID** – a registered version of the PC_plus_4 to be used in the ID phase.
This is why we added _pID at the end of that signal name.
- **branch_adrs** – a 32 bit signal which is made of PC_plus_4_pID + sext(imm)<<2.
This is the address to be loaded into the PC when a successful branch is performed.
Imm signal is made of the lower 16 bits of IR_reg (see IR_reg in #8 below).
- **jump_adrs** – a 32 bit signal made of PC_plus_4_pID[31:28] & IR[25:0] & b“00”, i.e.,
the jump address in words multiplied by 4. This is the address to be loaded into the PC
when a jump or a jal instruction is performed.
- **jr_adrs** – a 32 bit signal made of the Rs value in a JR instruction.
Since we do not have a GPR file, we set the Rs value to x“00400004”.
In the complete CPU this will be the address to be loaded into the PC when inst. is jr.
- **PC_source** – a 2 bit signal. When “00”, PC_reg is loaded with PC_plus_4. When “01” it
is loaded with branch_adrs, when “10” with jr_adrs, when “11” with the jump_adrs.
- **IR_reg** – a 32 bit register that has the instruction we read from the IMem. This register is
part of the IMem (The IMem is an already designed component we use in the Fetch Unit).
- **imm** – the 16 LSBs of IR_reg
- **sext_imm** – sign extension of imm to 32 bits
- **opcode** – the 6 MSBs of IR_reg. We should determine the PC_source by the instruction opcode
(j,jal-11, beq,bne-01,jr -10, any other instruction-00).
- **HOLD** – This signal is meant to freeze all registers when it is “1”. Very important !!

The Simulation project

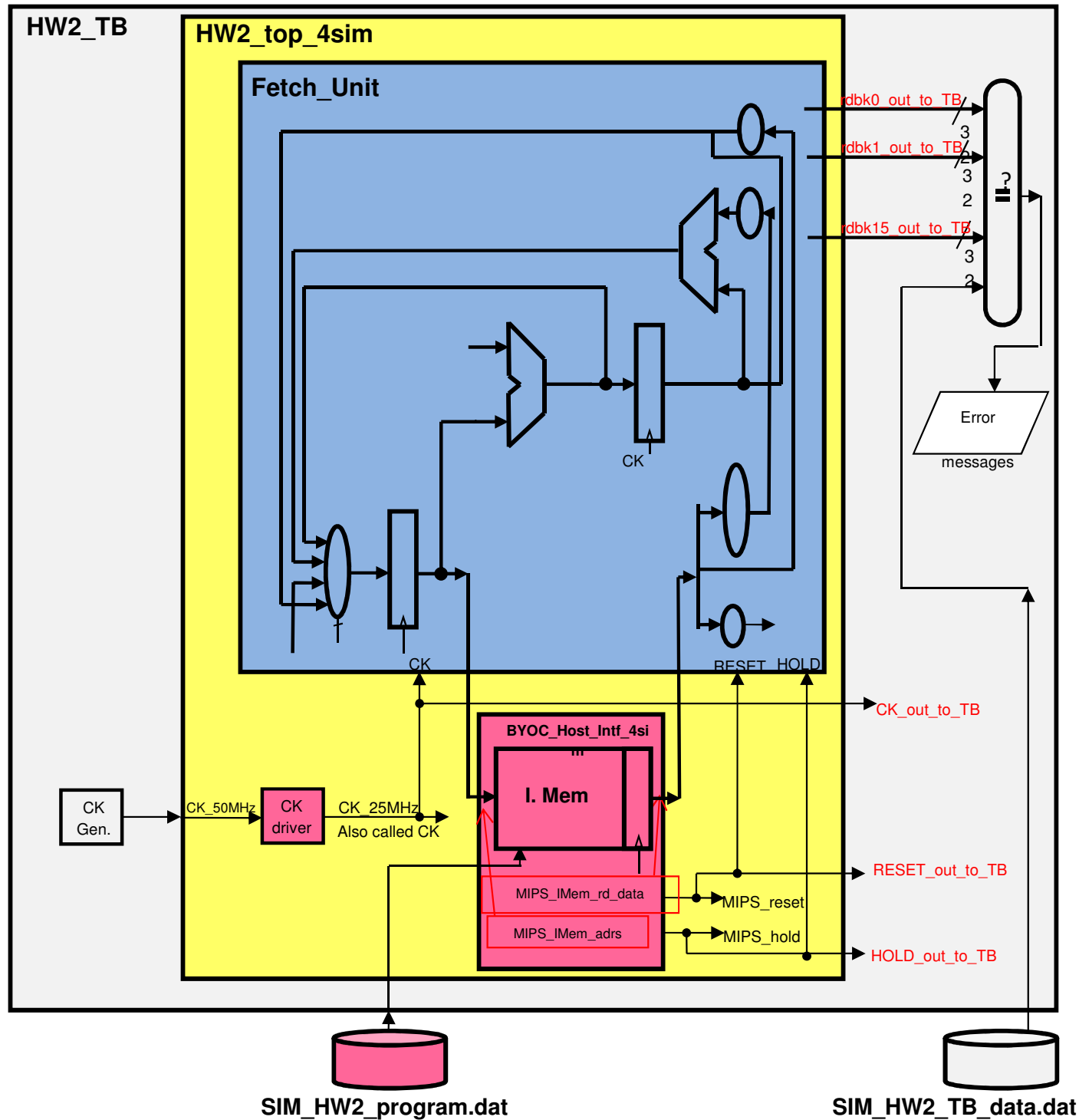

The files we require to have in order to run the simulation are:

Group #1 – The design files

1. **HW2_top_4sim.vhd** – The pre-prepared top file connecting the Fetc_Unit, clock_driver & BYOC_host intf
2. **Fetch_Unit.vhd** - your design implementing figure 1

Group #2 – The infrastructure files [pre-prepared] The same for HW2, HW4, HW5, HW6.

3. **BYOC_clock_driver_4sim.vhd** – component dividing the CK from 50MHz to 25MHz
4. **BYOC_Host_Intf_4sim.vhd** – component having the IMem (& creates reset & hold)

Group #3 – The simulation files [different for each HW]


3. **SIM_HW2_TB.vhd** - The TB vhd file prepared in advance
4. **SIM_HW2_TB_data.dat** - The data file read by the TB during simulation for comparison
5. **SIM_HW2_program.dat** - The program file for simulation.
6. **SIM_HW2_filenames.vhd** - The actual path information of the two dat files.

We prepared an “empty” **Fetch_Unit.empty** file in which we already did the following:

- Defined the I/O pins of the Fetch_Unit_4sim design
- Defined all necessary internal signal inside the Fetch_Unit_4sim design
- Connected other signals, e.g., signals to be outputted to the TB & rdbk signals

You have to rename it to Fetch_Unit.vhd and write the equations describing the logic circuitry of Figure 1!


The Simulation project

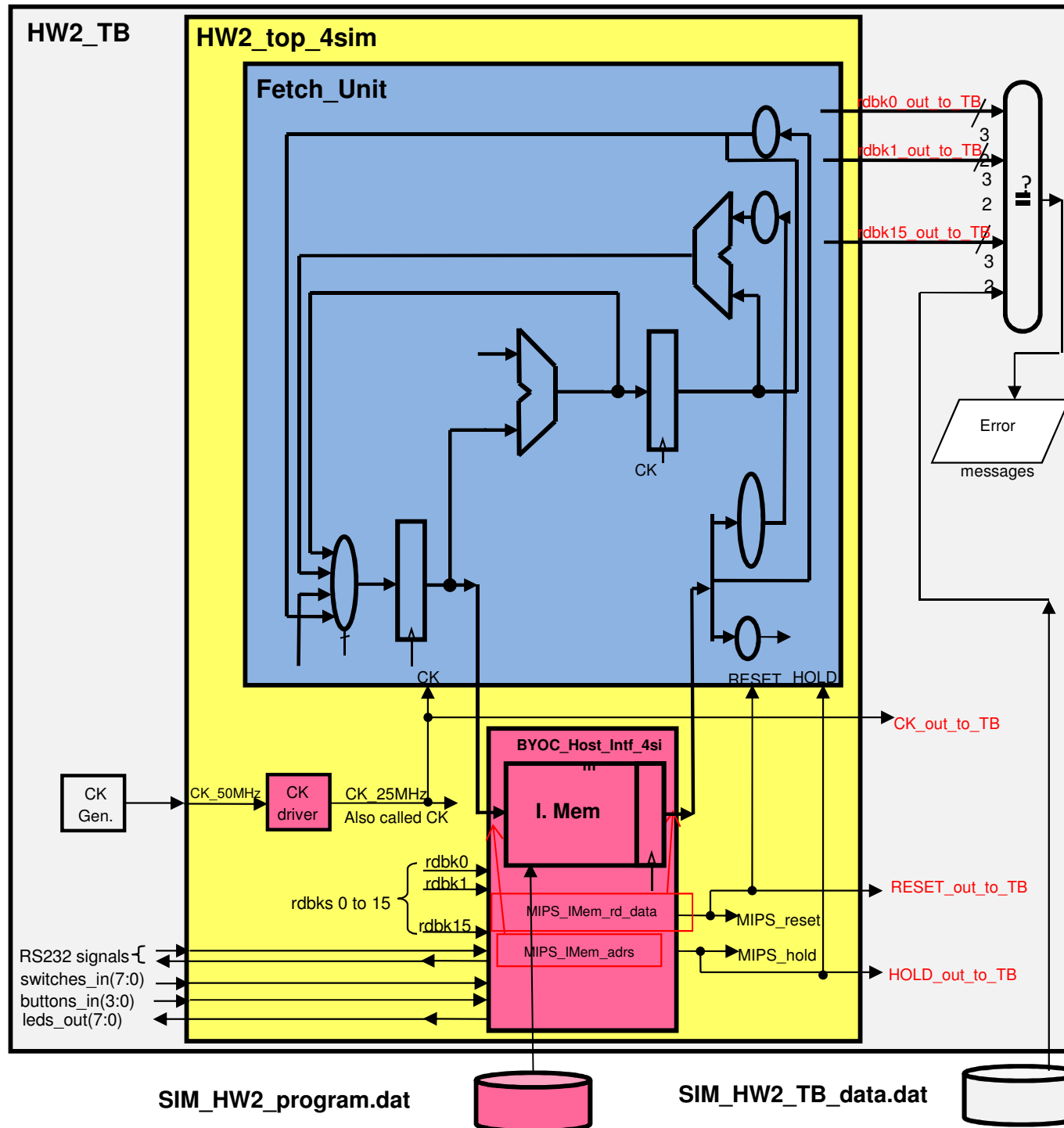

Simulation report

- You should submit a zip file of your entire simulation & implementation project. Your zip file should have two directories **Simulation & Implementation**.
In the **Simulation** one you'll have 3 sub-directories:
Src_4sim – here you put all of the *.vhd sources and the *.dat file (used by the TB)
Sim – here you should have the Fetch_unit_4sim project created by the simulator
Docs – Here you put your simulation report. With your ID numbers (names-opt.)
- Run the simulation to 5500 nS.
- In the DOC file you need to attach with screen captures describing the simulation you made. All signals mentioned in section 1a above should be presented in the screen capture. Show at least the 1st 10 ck cycle following the end of the reset pulse and make the values of all signals readable.
- In that doc file you need to answer the questions appearing in the HW2 doc.

The Implementation project

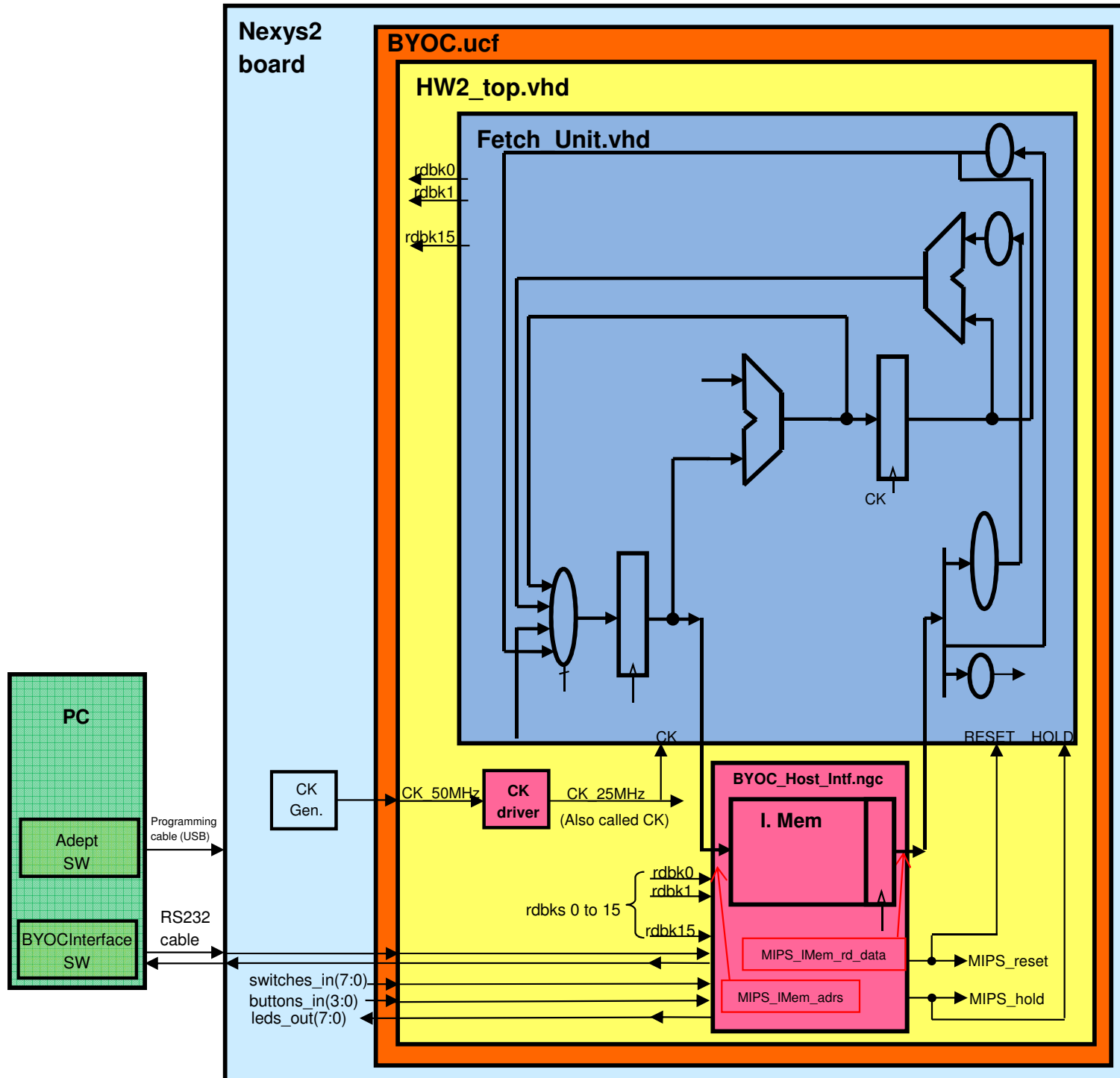

So the files we require to have in order to run the implementation are:

Group #1 – The design files

1. **HW2_top.vhd** – The top file after renaming and removal of all signals outputted to the TB
1. **Fetch_Unit.vhd** - your design implementing figure 1

Group #2 – The infrastructure files

3. **BYOC_clock_driver.vhd** – A CK divider from 50MHz to 25MHz that has a **BUFG** driver inside
3. **BYOC_Host_Intf.ngc** – The pre-compiled component including the IMem and creating the reset & hold signals and the infrastructure interfacing to the PC which is required to run the implemented design.

Group #3 – The implementation files


5. **BYOC.ucf** - The file listing which signals are connected to which FPGA pins in the Nexys2 board.

A reminder: We connected the rdbk signals as follows:

rdbk0	=>	PC_reg,
rdbk1	=>	PC_plus_4,
rdbk2	=>	branch_adrs,
rdbk3	=>	jr_adrs,
rdbk4	=>	jump_adrs,
rdbk5	=>	PC_plus_4_pID,
rdbk6	=>	IR_reg.
rdbk7	=>	PC_source (bits 1:0),
rdbk8	=>	RESET (bit 0),
rdbk9	=>	output of PC_mux (32 bit signal).,
rdbk10 - 15	=>	0x00000000

- **We run ISE and get a bit file**
- **Load the design using the Adept SW**
- **Load the IMem via the BYOCIntf SW**
- **Then use it also to apply a single ck and check the rdbk signals**

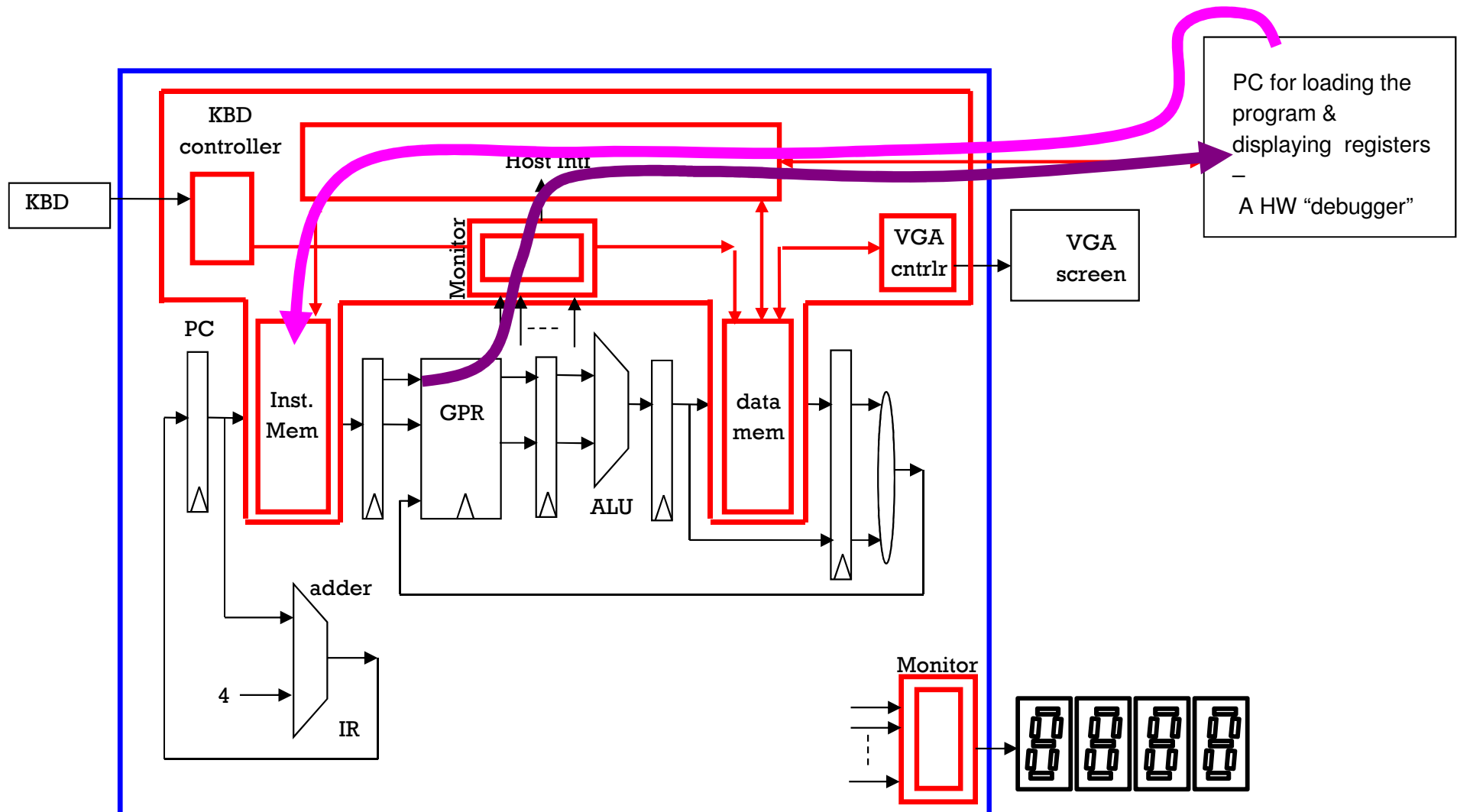- Load the IMem via the BYOCIntf SW
- Then use it also to apply a single ck and check the rdbk signals




Now it is your turn!

**Thanks for
listening!**

Backup slides

 If we rotate that, we see the same picture we saw in the previous slides.



The pipelined MIPS


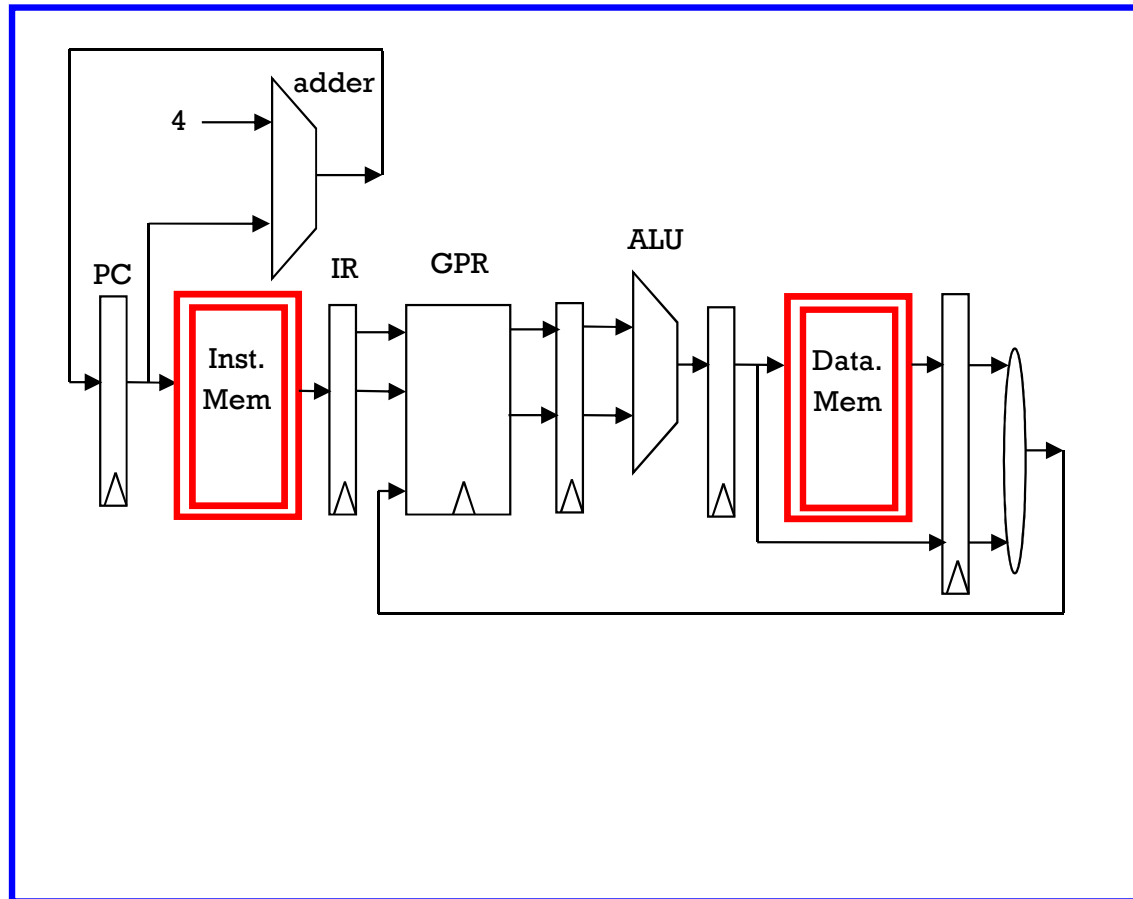


Fig. 3 – The pipeline processor

The pipelined MIPS

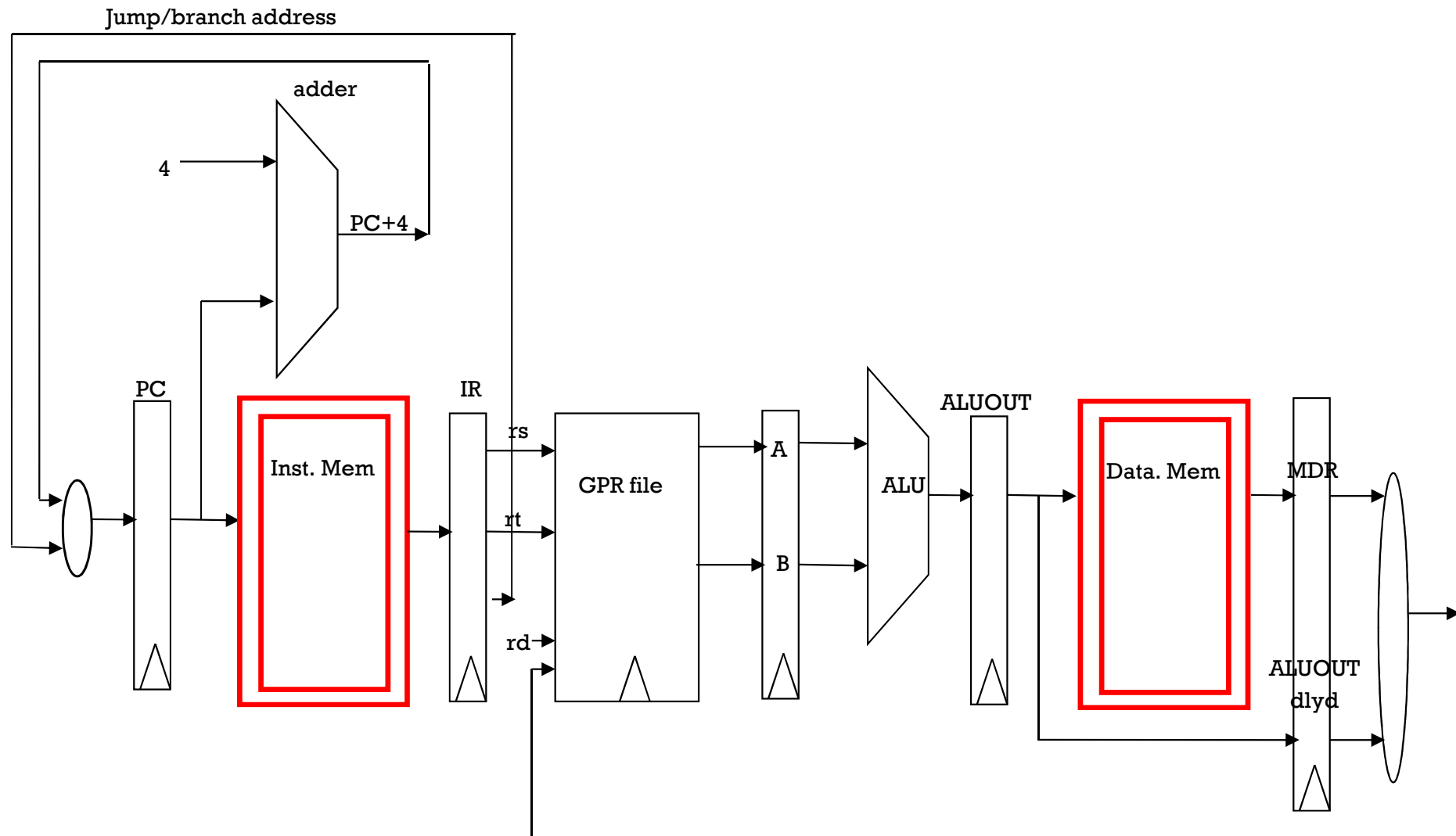

The pipelined processor with support

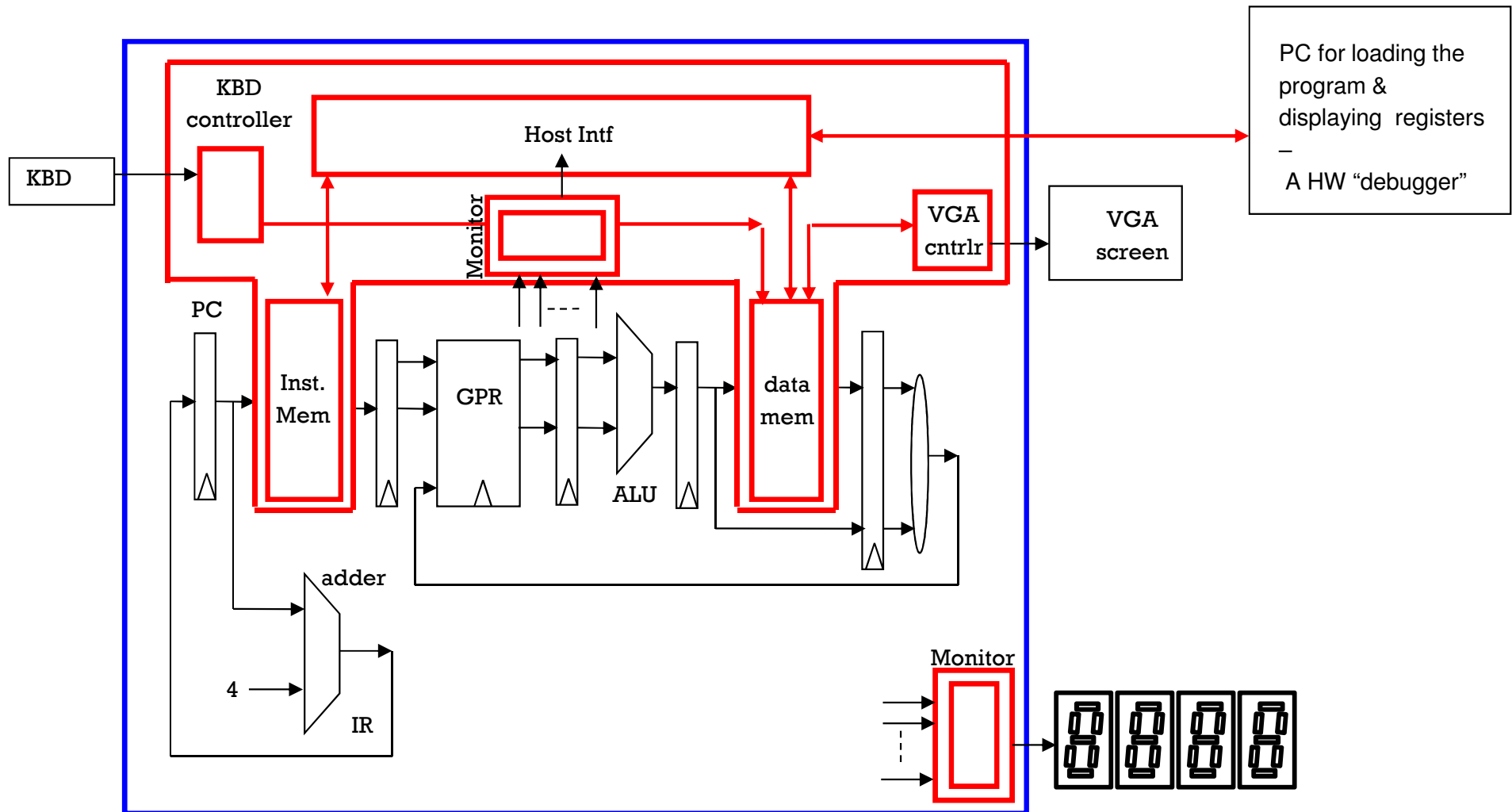


Fig. 4 – The processor & course infrastructure

The VGA screen

A word, 32 bits, is 32 BW pixels. Bit 0 is on the left.

